




Two stage opamp

Professor: Paul C.-P. Chao

Two stage opamp

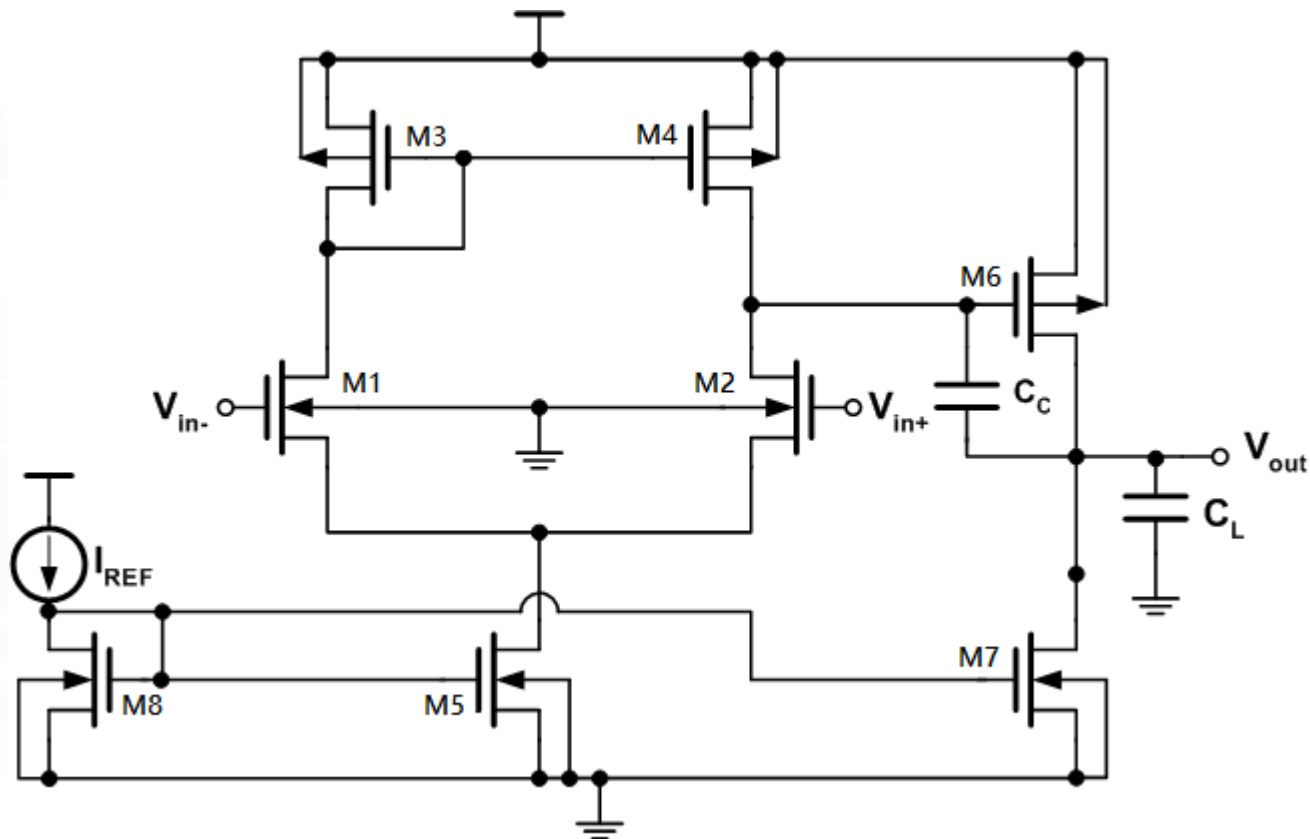- $V_{dd}=1.8V$, $V_{in+}=V_{in-}=0.9V$, $C_L=4pF$



Design Specification

Parameter	Value
DC Gain	>60dB
Phase Margin	>60 deg
Unit Gain Frequency	>10M Hz
Common mode rejection ratio (CMRR)	>60dB
Input Common Mode Range (ICMR)	>1V
Output Swing	>1V
Slew Rate	>10V/us

- 作業上傳到E3, 繳交以下檔案, 檔名: hw3_學號
- 報告 (.pdf) (ex:hw3_0560030.pdf)
 1. 每個規格需符合, 並附上模擬結果
 2. 解釋設計方法
- Spice file (.sp) (ex:hw3_0560030.sp)

MOS





```
***** MOS *****
.option post accurate method=gear
.option probe
.lib 'cic018.1' TT
.temp 27

* Main Circuit
MN D G S B N_18 L=1u W=1u

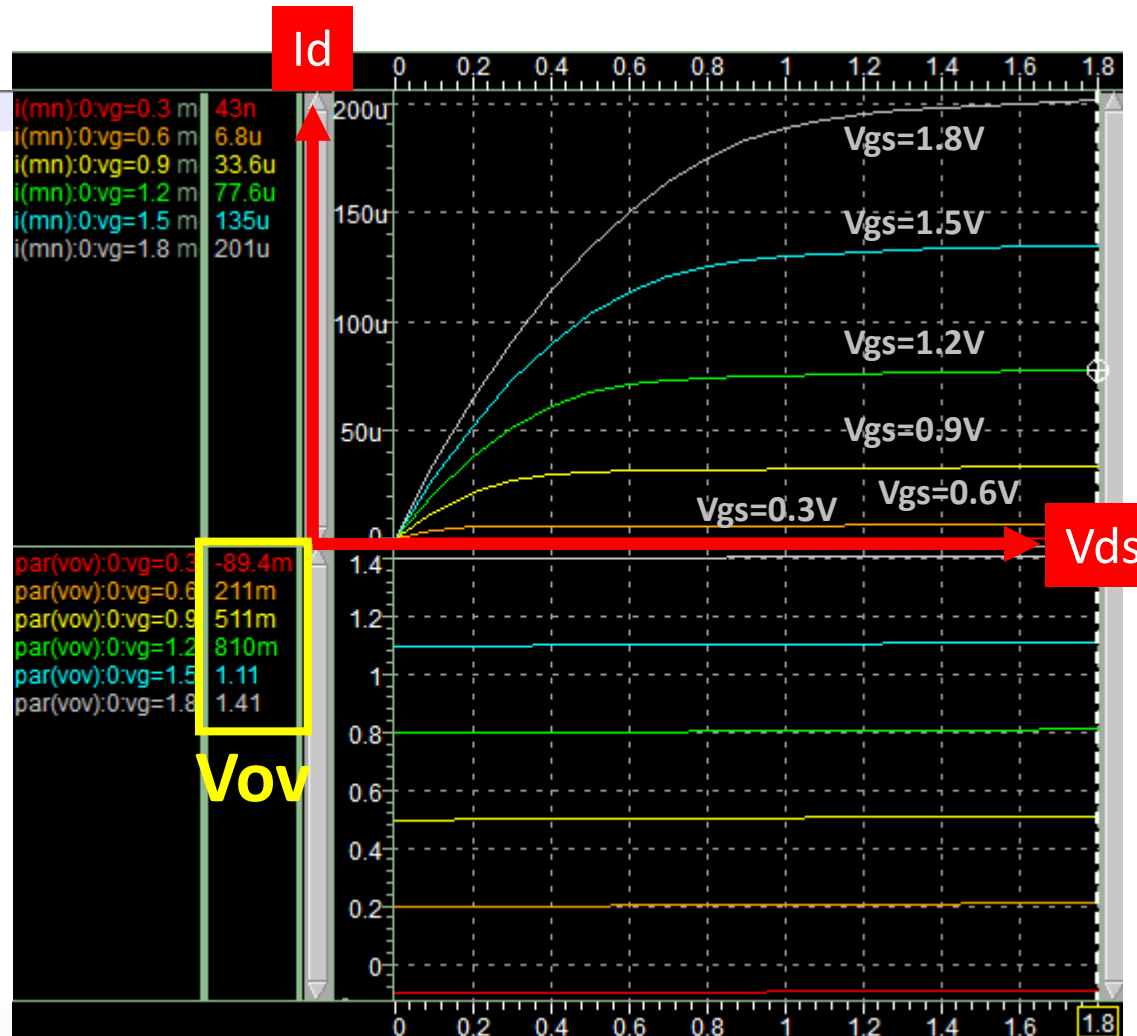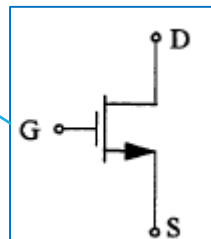Vd d gnd DC=1.8
Vg g gnd DC=0.9
Vs s gnd DC=0
Vb b gnd DC=0




* Simulation Commands
.op
.dc vd 0 1.8 0.1 sweep vg 0.3 1.8 0.3
.probe DC V(*)
.print DC I(MN)
.probe vth = lv9(MN)
.probe vov = par('lx2(MN)-lv9(MN)')
.end
```



MOS



➤ Calculate by Excel

B6		:				=B2*2/B3*B5/(B4^2)
	A	B	C	D		
1	算W					
2	Id	76 (uA)				
3	uCox	240 (uA/V2)				
4	vov=vgs-vth	0.8 (V)				
5	L	1 (u)				
6	W	0.989583 (um)				
7						
8						
9						
10	算uCox					
11	Id	76 (uA)				
12	vov=vgs-vth	0.8 (V)				
13	W	1 (u)				
14	L	1 (u)				
15	uCox	237.5 (uA/V2)				

Operation in the *saturation* region:

■ Conditions:

$$(1) v_{GS} \geq V_t \Leftrightarrow v_{OV} \geq 0$$

$$(2) v_{GD} \leq V_t \Leftrightarrow v_{DS} \geq v_{GS} - V_t \Leftrightarrow v_{DS} \geq v_{OV}$$

■ *i-v* Characteristics:

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

Threshold voltage:

$$V_t = V_{t0} + \gamma (\sqrt{2\phi_f + |V_{SB}|} - \sqrt{2\phi_f})$$

Overdrive voltage:

$$v_{OV} = v_{GS} - V_t$$

$$v_{GS} = V_t + v_{OV}$$

Process parameters:

$$C_{ox} = \epsilon_{ox} / t_{ox} \quad (\text{F/m}^2)$$

$$k'_n = \mu_n C_{ox} \quad (\text{A/V}^2)$$

$$V'_A = (V_A / L) \quad (\text{V/m})$$

$$\lambda = (1 / V_A) \quad (\text{V}^{-1})$$

$$\gamma = \sqrt{2qN_A \epsilon_s} / C_{ox} \quad (\text{V}^{1/2})$$

Constants:

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

$$\epsilon_{ox} = 3.9\epsilon_0 = 3.45 \times 10^{-11} \text{ F/m}$$

$$\epsilon_s = 11.7\epsilon_0 = 1.04 \times 10^{-10} \text{ F/m}$$

$$q = 1.602 \times 10^{-19} \text{ C}$$

Hspice netlist

➤ Circuit description and testbench

```

1 ***** two stage opamp *****
2 ***** model/lib *****
3 .lib 'cic018.1' TT
4 ***** options *****
5 .option post accurate method=gear
6 .option probe
7 .temp 27
8 .global vdd gnd
9 ***** Source *****
10 Vdd      Vdd      gnd      DC=1.8
11 Iref     vdd      g11
12 Vinp     vinp     gnd      dc=0.9 ac=1
13 Vinn     vinn     gnd      dc=0.9
14
15 * Main Circuit
16 M1       N_18 1=     w=     m=
17 M2       N_18 1=     w=     m=
18 M3       P_18 1=     w=     m=
19 M4       P_18 1=     w=     m=
20 M5       N_18 1=     w=     m=
21 M6       P_18 1=     w=     m=
22 M7       N_18 1=     w=     m=
23 M8       N_18 1=     w=     m=
24 CC v12 vout
25 CL vout gnd 4p

```

```

27 ***** analysis *****
28 .op
29 .ac dec 10 10 1G
30 .probe vdb(vout) vp(vout)
31 .meas AC Gain10Hz FIND vdb(vout) AT 10
32 .meas ac Unit_gain when vdb(vout)=0
33 .meas ac Phase_mar FIND vp(vout) when vdb(vout)=0
34
35 **SLEW RATE**
36
37
38
39
40
41
42
43 **ICMR**
44
45
46
47 **OUTPUT VOLTAGE SWING**
48
49
50
51
52
53
54
55
56 **CMRR**
57
58
59
60
61
62
63 .end

```

.Measure

(10). MEASURE Statement : AVG, RMS, MIN, MAX, & P-P

● Syntax :

```
.MEASURE DC|AC|TRAN result FUNC out_var <FROM=val1> <TO=val2>  
+  
    <Optimization Option>
```

- **result_var** : Name Given the Measured Value in HSPICE Output
- **FUNC** : **AVG** ----- Average **MAX** ----- Maximun **PP** ---- Peak-to-Peak
 MIN ----- Minimum **RMS** ----- Root Mean Square
- **out_var** : Name of the Output Variable to be Measured
- **<Optimization Option>**: <GOAL=val> <MINVAL=val> <WEIGHT=val>

● Example:

```
.meas TRAN minval        MIN v(1,2)    from=25ns to=50ns  
.meas TRAN tot_power    AVG power    from=25ns to=50ns  
.meas TRAN rms_power    RMS power
```

.Measure

(11). MEASURE Statement : Find & When Function

● Syntax :


```
.measure DC|AC|TRAN result WHEN ... <Optimization Option>  
.measure DC|AC|TRAN result FIND out_var1 WHEN ...<Optimization Option>  
.measure DC|AC|TRAN result_var FIND out_var1 AT=val <Optimization Option>
```

- **result** : Name Given the Measured Value in HSPICE Output
- **WHEN ...** : WHEN out_var2=val|out_var3 <TD=time_delay>
+ <CROSS=n|LAST> <RISE=r_n|LAST> <FALL=f_n|LAST>
- **<Optimization Option>** : <GOAL=val> <MINVAL=val> <WEIGHT=val>

● Example:

```
.meas TRAN fifth WHEN v(osc_out)=2.5V rise=5  
.meas TRAN result FIND v(out) WHEN v(in)=2.5V rise=1  
.meas TRAN vmin FIND v(out) AT=30ns
```


AC analysis

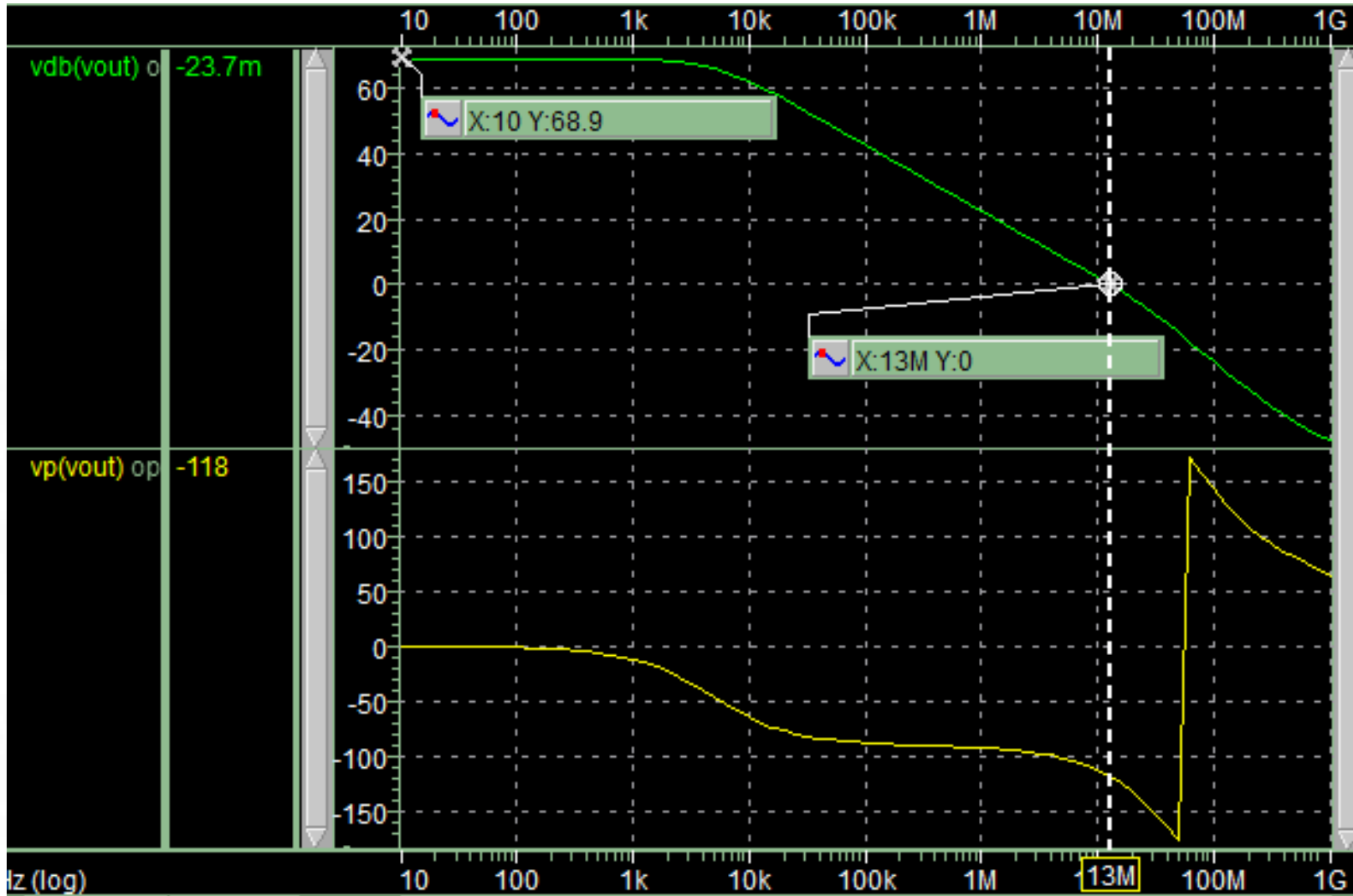

.Measure

● Unity-gain Freq, Phase margin, & DC gain(db/M):

```
.meas AC unitfreq      WHEN vdb(out)=0  FALL=1
.meas AC phase        FIND  vp(out)      WHEN vdb(out)=0
.meas AC 'gain(db)'    MAX    vdb(out)
.meas AC 'gain(mag)'   MAX    vm(out)
```

➤ Analysis command

```
.ac dec 10 10 1G
.probe vdb(vout) vp(vout)
.meas ac Gain10Hz FIND vdb(vout) AT 10
.meas ac Unit_gain when vdb(vout)=0
.meas ac Phase_mar FIND vp(vout) when vdb(vout)=0
```

➤ Lis file

```
***** two stage opamp *****

*****  ac analysis tnom= 25.000 temp= 27.000 ***
gain10hz= 6.8925E+01
unit_gain= 1.2983E+07
phase_mar= -1.1773E+02
```

CMRR

$$\text{CMRR} = \frac{A_d}{A_{cm}}$$

$$\begin{aligned} \text{CMRR} &= 20 \log_{10} \left(\frac{A_d}{A_{cm}} \right) \text{ dB} \\ &= 20 \log |A_d| - 20 \log |A_{cm}| \end{aligned}$$

➤ SPICE – 求 A_{cm}


Vcm vcm gnd dc=0.9 ac=1

Vinp vinp vcm dc=0

Vinn vinn vcm dc=0

.ac dec 10 10 1G


.probe vdb(vout)

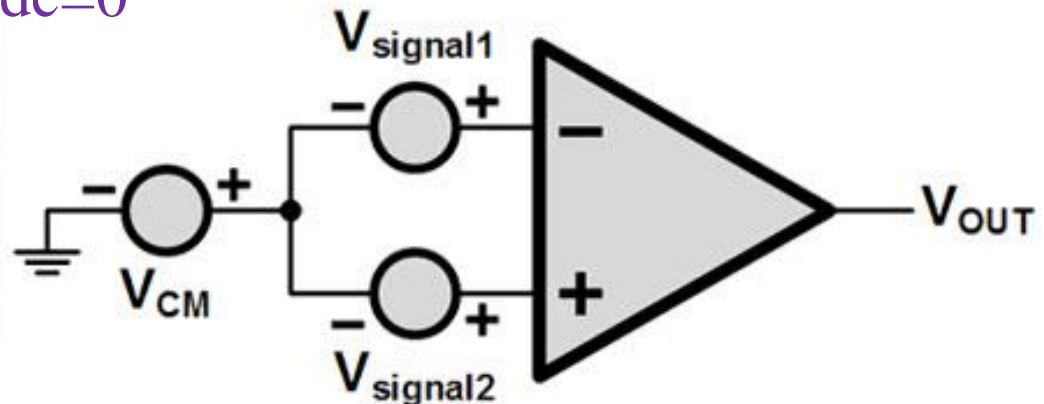

CMRR



$$\text{CMRR} = 20 \log_{10} \left(\frac{A_d}{A_{cm}} \right) \text{ dB} = 20 \log |A_d| - 20 \log |A_{cm}|$$
$$= 68.9 \text{ dB} - (-2.58 \text{ dB}) = 71.48 \text{ dB}$$

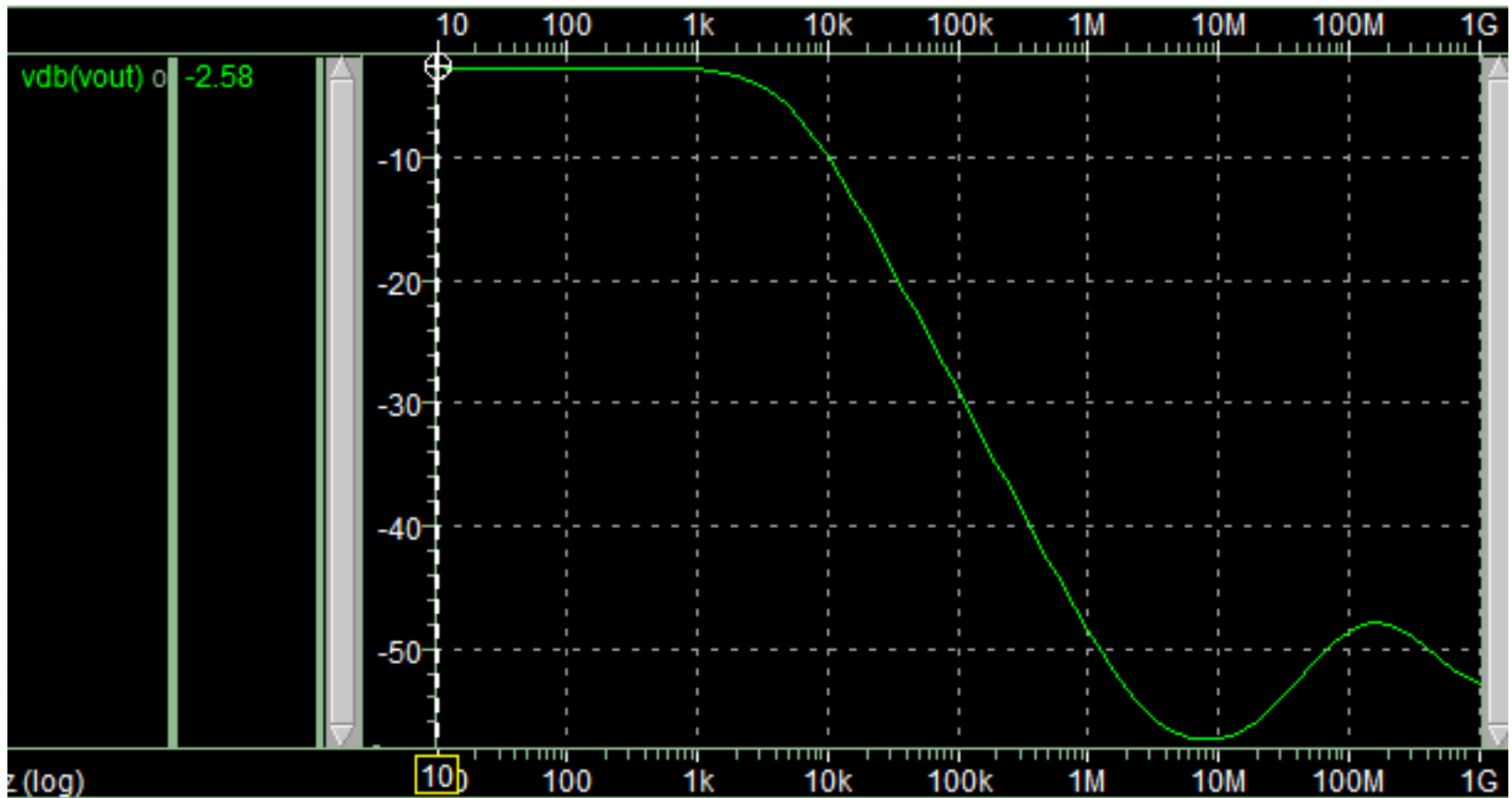


➤ SPICE

Vinp vinp gnd dc=0.9

M1 node_D **vout** node_S node_B N_18 l=?u w=?u m=?

.dc vinp 0 1.8 1m


.probe V(vout) V(vinp)

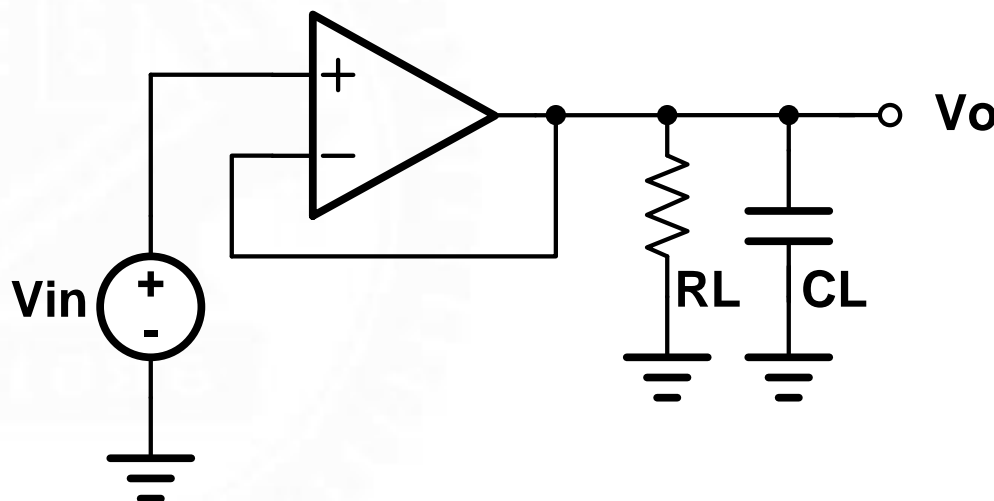

ICMR



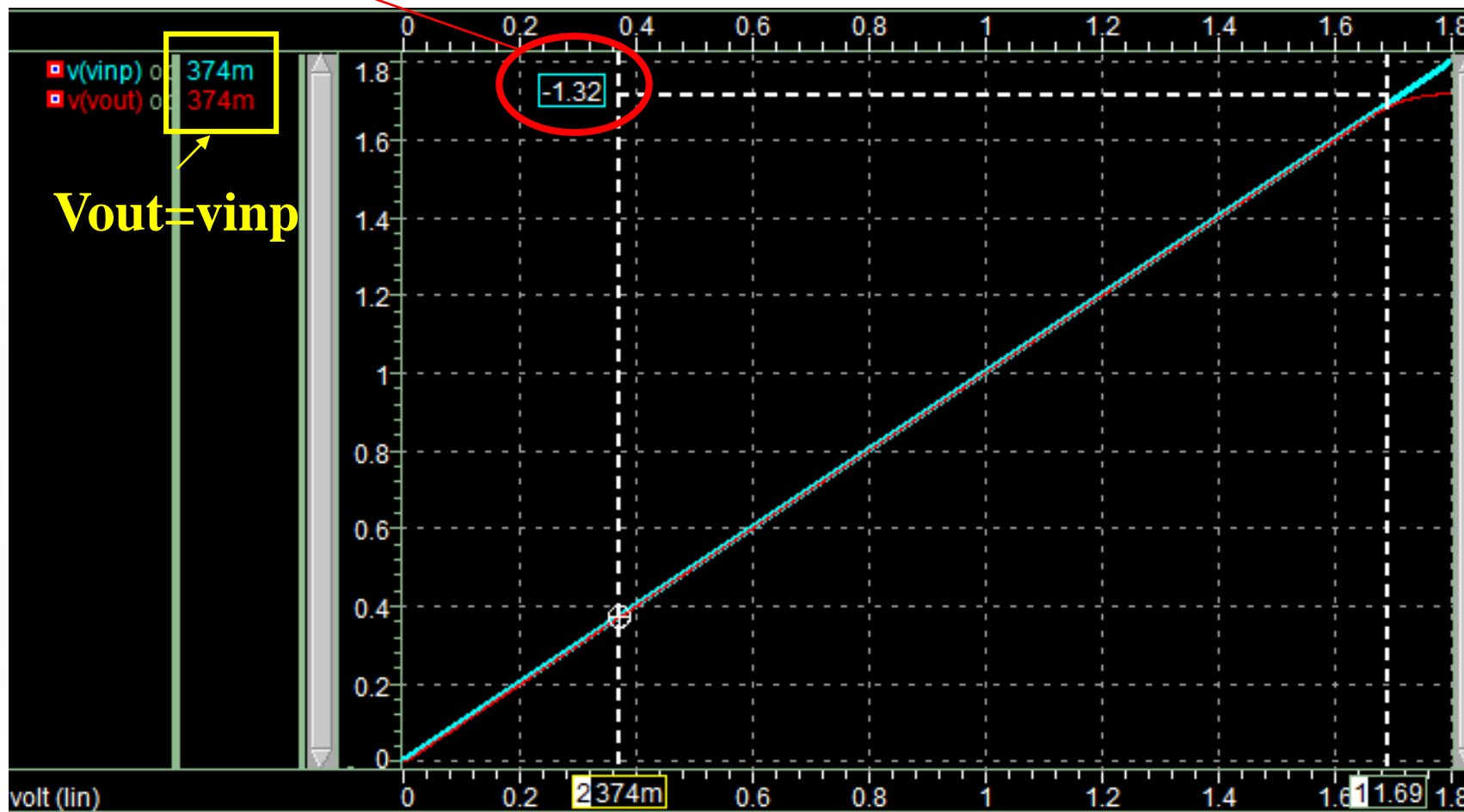- 觀察輸出 V_{out} 能夠隨著輸入 V_{in} 改變的電壓範圍
- $ICMR = 1.32V$



Output Swing

➤ SPICE

vinp vinn gnd dc=0.9


R1 VIN vinn ?k

R2 vinn vout ?k

VIN VIN gnd dc=0.9


.dc VIN 0 1.8 1m

.probe V(vout) V(VIN)

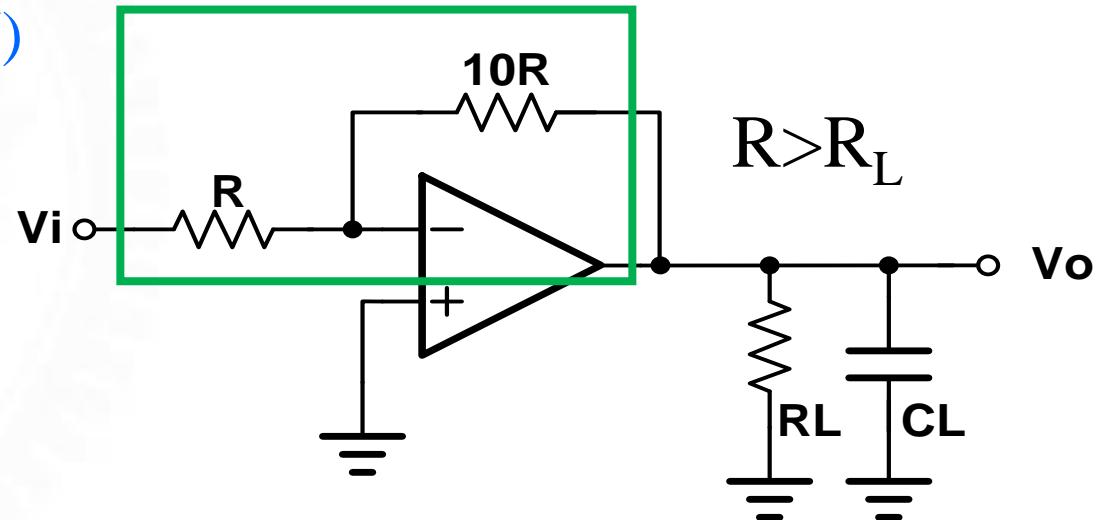

Output Swing

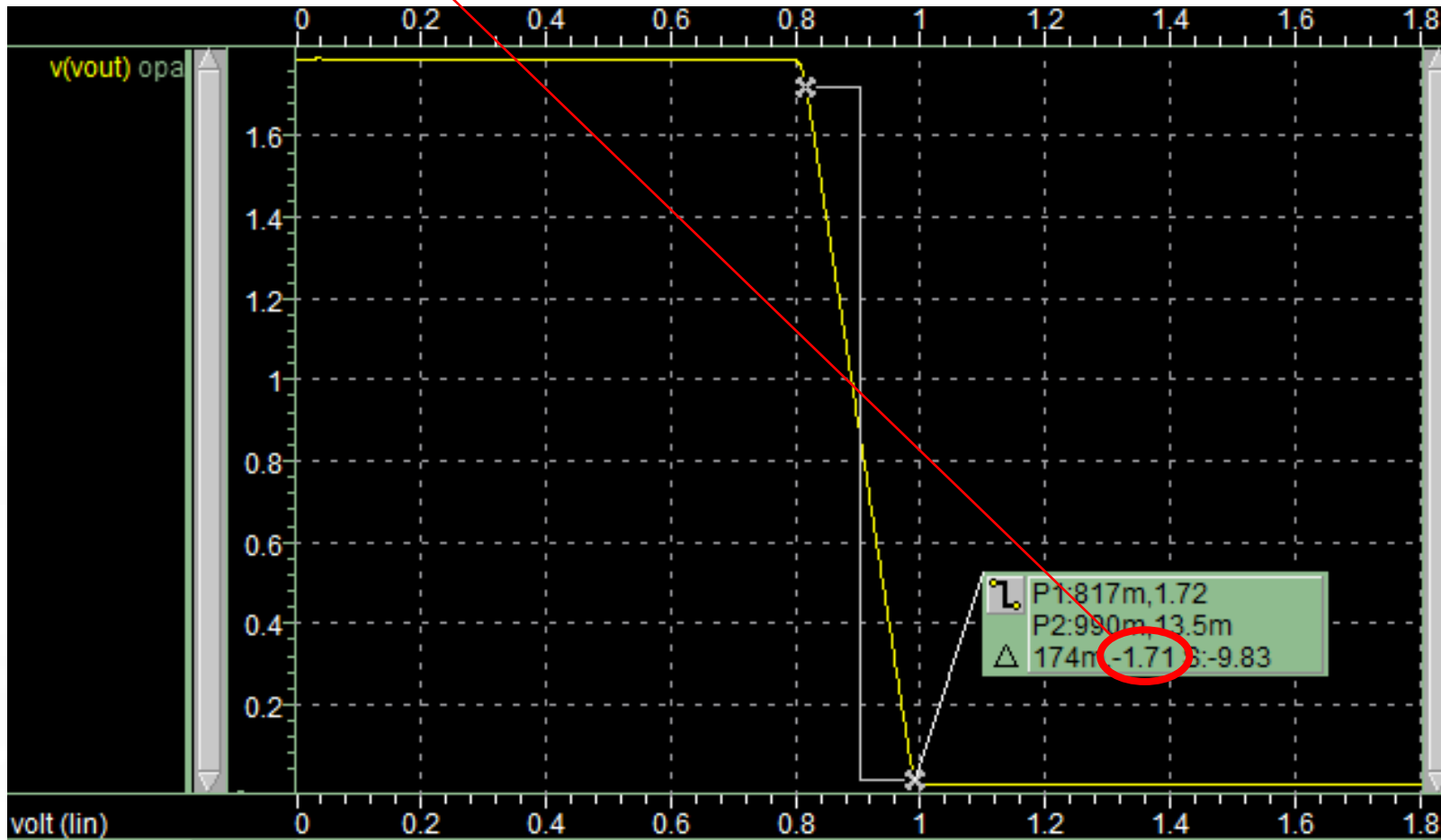
- 觀察輸出 V_{out} 能夠隨著輸入 V_{IN} 變化的電壓範圍
- Output Swing = 1.71V



Slew Rate

➤ SPICE
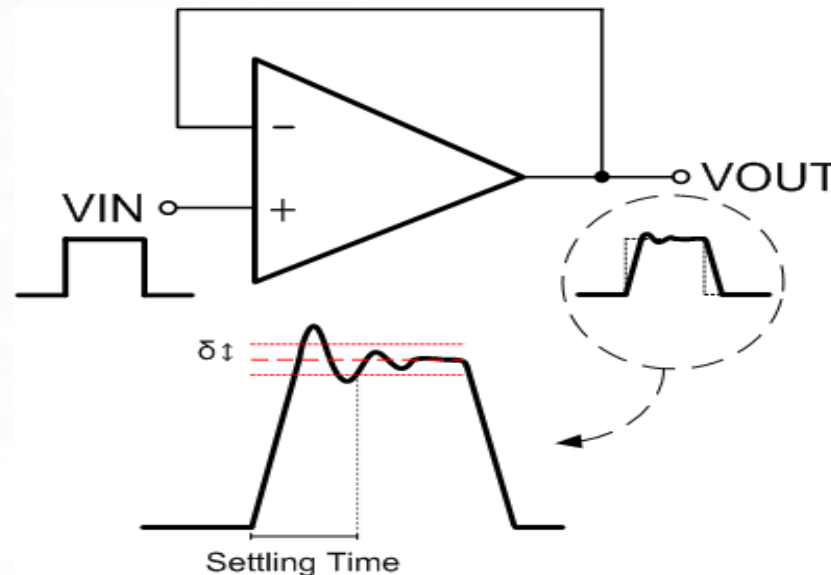
```
vinp vinp gnd pulse(0v 1.8v Tdelay Trise Tfall Tduty Tperiod)
M1 node_D vout node_S node_B N_18 l=?u w=?u m=?
.tran 1p ??
.probe V(vout) V(vinp)
.meas Tran Up_Slew-Rate DERIV V(vout) AT=??
```




Slew Rate

- Slew Rate = 11.7V/us

```
***** two stage opamp *****
```

```
***** transient analysis tnom= 25.000
```

```
up_slew-rate= 1.1172E+07
```

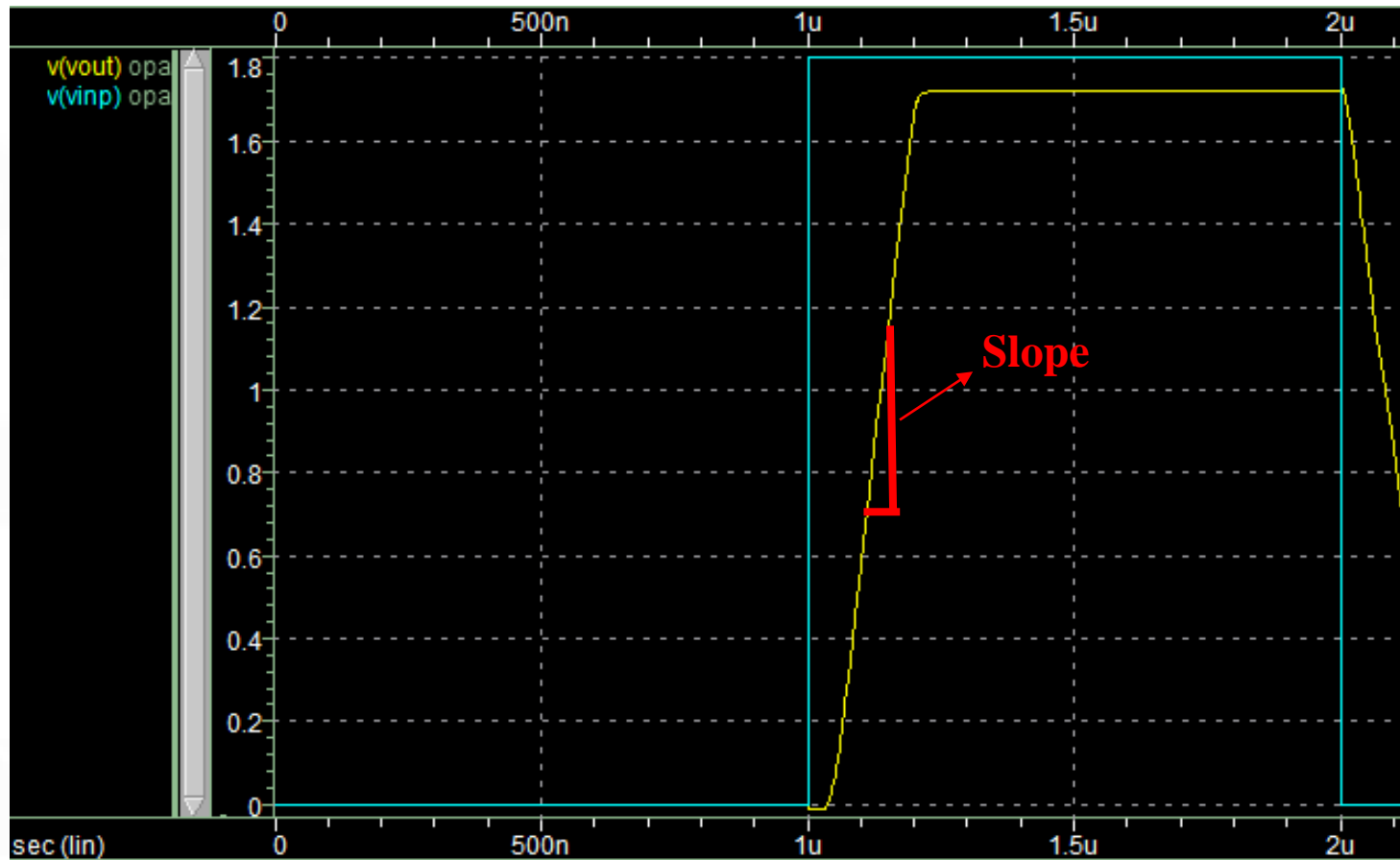

課堂練習 - Two stage opamp

- $V_{dd}=1.8V$, $V_{in+}=V_{in-}=0.9V$, $C_L=4pF$

Parameter	Value
Gain	>40dB
Phase Margin	>50 deg
Unit Gain Frequency	>1M Hz
CMRR	>50dB
ICMR	>1V
Output Swing	>1V
Slew Rate	>1V/us

