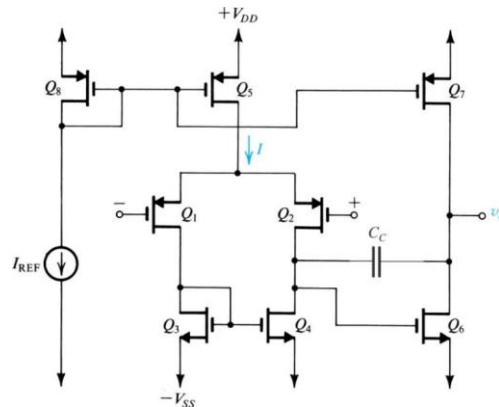


Quiz 1 on Oct 26<sup>th</sup> :

True (v) or False (x) (5 pts, 1 pt for each question):


( x ): The allowable input range of a 2-stage op as below is

$$-V_{SS} + V_{OV3} - |V_{tp}| \leq V_{ICM} \leq V_{DD} - |V_{tp}| - |V_{OV1}| - |V_{OV5}|.$$



( v ): The overall gain of the 2-stage as above is  $g_{m2}(r_{o2} \parallel r_{o4})g_{m6}(r_{o2} \parallel r_{o4})$ .

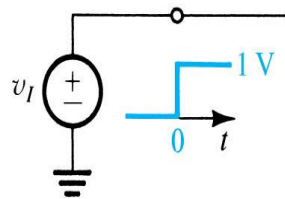( x ): With a large signal applied to the 2-stage op as shown below, Q1 in the first figure will be turned off initially in the transient period.



( v ) In the transient period defined in the previous question, the current drawn from the output node is exactly  $I$ , as denoted in the first figure, which is the current provide by Q3, a saturated current source.

( x ): Lower Vov increases bandwidth and gain of an op.