

## HW7

## 14.12

**14.12** If the closed-loop amplifier in Fig. 14.5 exhibits a phase shift of  $-3^\circ$  for  $\omega$  around  $\omega_0$ , then the loop-gain expression in Eq. (14.11) becomes

$$L(j\omega) = \frac{(1 + R_2/R_1)e^{-j\phi}}{3 + j(\omega CR - 1/\omega CR)}$$

where

$$\phi = \frac{3\pi}{180} = \pi/60$$

Oscillation will occur at the frequency  $\omega_0$  for which the phase angle of  $L(j\omega)$  is  $0^\circ$ :

$$-\phi = \tan^{-1} \frac{1}{3} \left( \omega_0 CR - \frac{1}{\omega_0 CR} \right)$$

$$\omega_0 CR - \frac{1}{\omega_0 CR} = -3 \tan 3^\circ = -0.157$$

$$\Rightarrow \omega_0^2 + \frac{0.157}{CR} \omega_0 - \frac{1}{(CR)^2} = 0$$

$$\Rightarrow \omega_0 = \frac{0.925}{CR}$$

## 14.15

**14.15** First we design the circuit to operate at 10 kHz.

$$\omega_0 = \frac{1}{CR}$$

$$2\pi \times 10 \times 10^3 = \frac{1}{CR}$$

$$\Rightarrow CR = 0.159 \times 10^{-4} \text{ s}$$

For  $R = 10 \text{ k}\Omega$ , we have

$$C = \frac{0.159 \times 10^{-4}}{10 \times 10^3} = 1.59 \text{ nF}$$

Now, refer to Eq. (14.11). If the closed-loop amplifier has an excess phase lag of  $5.7^\circ$ , then the gain will be  $\left(1 + \frac{R_2}{R_1}\right)e^{-j5.7^\circ}$ . Oscillations will occur at the frequency  $\omega_{01}$  at which the phase angle of the denominator is  $-5.7^\circ$ , that is,

$$\tan^{-1} \frac{1}{3} \left( \omega_{01} CR - \frac{1}{\omega_{01} CR} \right) = -5.7^\circ$$

$$\omega_{01} CR - \frac{1}{\omega_{01} CR} = 3 \tan(-5.7^\circ) = -0.3$$

$$\Rightarrow \omega_{01}^2 + \frac{0.3}{CR} \omega_{01} - \frac{1}{(CR)^2} = 0$$

$$\Rightarrow \omega_{01} = \frac{0.86}{CR}$$

That is, the frequency of oscillation is reduced by 14% to

$$f_{01} = 0.86f_0 = 8.6 \text{ kHz}$$

To restore operation to  $f_0 = 10 \text{ kHz}$ , we modify the shunt resistor  $R$  to  $R_x$ , as indicated in Fig. 1.

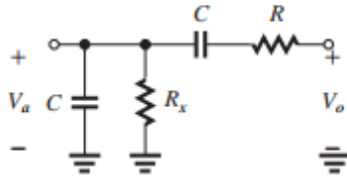


Figure 1

We now require the feedback RC circuit to have a phase shift of  $-(-5.7^\circ) = +5.7^\circ$  at  $f = 10 \text{ kHz}$ . The transfer function of the RC circuit can be found as follows:

$$\begin{aligned} \frac{V_a}{V_o} &= \frac{Z_p}{Z_p + Z_s} \\ &= \frac{1}{1 + Z_s Y_p} \\ &= \frac{1}{1 + \left(R + \frac{1}{sC}\right) \left(\frac{1}{R_x} + sC\right)} \\ &= \frac{1}{\left(2 + \frac{R}{R_x}\right) + sCR + \frac{1}{sCR_x}} \end{aligned}$$

For  $s = j\omega$ , we have

$$\frac{V_a}{V_o} = \frac{1}{\left(2 + \frac{R}{R_x}\right) + j\left(\omega CR - \frac{1}{\omega CR_x}\right)}$$

At  $\omega = \omega_0$ , the phase angle of  $\frac{V_a}{V_o}$  must be  $+5.7^\circ$  or equivalently, the phase angle of the denominator must be  $-5.7^\circ$ . Thus,

$$\tan^{-1} \frac{\omega_0 CR - \frac{1}{\omega_0 CR_x}}{2 + \frac{R}{R_x}} = -5.7^\circ$$

$$\begin{aligned} \omega_0 CR - \frac{1}{\omega_0 CR_x} &= \left(2 + \frac{R}{R_x}\right) \tan(-5.7^\circ) \\ &= \left(2 + \frac{R}{R_x}\right) \times -0.0998 \end{aligned}$$

Now,  $\omega_0 CR = 1$ , thus

$$1 - \frac{R}{R_x} = -0.0998 \left(2 + \frac{R}{R_x}\right)$$

$$1 + 2 \times 0.0998 = \frac{R}{R_x} (1 - 0.0998) \Rightarrow \frac{R}{R_x} = 1.33$$

$$\Rightarrow R_x = 0.75 R = 7.5 \text{ k}\Omega$$

At  $\omega = \omega_0$  and for  $R_x = 7.5 \text{ k}\Omega$

$$\begin{aligned} \frac{V_a}{V_o}(\omega_0) &= \frac{1}{\left(2 + \frac{10}{7.5}\right) + j\left(1 - \frac{10}{7.5}\right)} \\ &= \frac{1}{3.33 - j0.33} \end{aligned}$$

$$\left| \frac{V_a}{V_o}(\omega_0) \right| = \frac{1}{\sqrt{(3.33)^2 + (0.33)^2}} = \frac{1}{3.35}$$

Thus the magnitude of the gain of the amplifier must be 3.35 V/V. Thus,  $R_2/R_1$  must be changed to

$$\frac{R_2}{R_1} = 2.35$$

## 14.18

**14.18** Figure 1 shows the circuit with the additional resistance  $R$  included. The loop has been broken at the output of the op amp. The analysis will determine  $V_o/V_x$  and equate it to unity, which is the condition for sustained oscillations.

To begin, observe that the voltage  $V_1$  is related to  $V_o$  by

$$\frac{V_o}{V_1} = -\frac{R_f}{R} \quad (1)$$

Also, the current  $I_1$  is given by

$$I_1 = \frac{V_1}{R} \quad (2)$$

We now proceed to determine the various currents and voltages of the RC network as follows:

$$\begin{aligned} V_2 &= V_1 + \frac{1}{sC} I_1 \\ &= V_1 + \frac{1}{sC} \frac{V_1}{R} = V_1 \left( 1 + \frac{1}{sCR} \right) \\ I_2 &= \frac{V_2}{R} = \frac{V_1}{R} \left( 1 + \frac{1}{sCR} \right) \\ I_3 &= I_1 + I_2 = \frac{V_1}{R} + \frac{V_1}{R} \left( 1 + \frac{1}{sCR} \right) \\ &= \frac{V_1}{R} \left( 2 + \frac{1}{sCR} \right) \\ V_3 &= V_2 + \frac{I_3}{sC} \\ &= V_1 \left( 1 + \frac{1}{sCR} \right) + \frac{V_1}{sCR} \left( 2 + \frac{1}{sCR} \right) \\ &= V_1 \left( 1 + \frac{3}{sCR} + \frac{1}{s^2 C^2 R^2} \right) \\ I_4 &= \frac{V_3}{R} = \frac{V_1}{R} \left( 1 + \frac{3}{sCR} + \frac{1}{s^2 C^2 R^2} \right) \end{aligned}$$

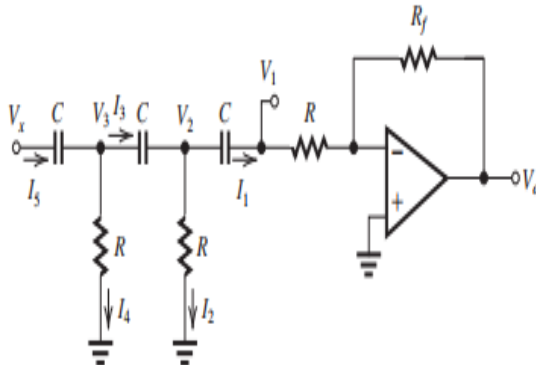


Figure 1

$$\begin{aligned} I_5 &= I_3 + I_4 \\ &= \frac{V_1}{R} \left( 2 + \frac{1}{sCR} \right) + \frac{V_1}{R} \left( 1 + \frac{3}{sCR} + \frac{1}{s^2 C^2 R^2} \right) \\ &= \frac{V_1}{R} \left( 3 + \frac{4}{sCR} + \frac{1}{s^2 C^2 R^2} \right) \\ V_x &= V_3 + \frac{I_5}{sC} \\ &= V_1 \left( 1 + \frac{3}{sCR} + \frac{1}{s^2 C^2 R^2} \right) \\ &\quad + \frac{V_1}{sCR} \left( 3 + \frac{4}{sCR} + \frac{1}{s^2 C^2 R^2} \right) \\ &= V_1 \left( 1 + \frac{6}{sCR} + \frac{5}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3} \right) \end{aligned}$$

Now, by replacing  $V_1$  by the value from Eq. (1), we obtain

$$V_x = -V_o \frac{R}{R_f} \left( 1 + \frac{6}{sCR} + \frac{5}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3} \right)$$

For sustained oscillations  $V_o = V_x$ , thus

$$-\frac{R_f}{R} = 1 + \frac{6}{sCR} + \frac{5}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3}$$

For  $s = j\omega$ , we have

$$\begin{aligned} -\frac{R_f}{R} &= 1 + \frac{6}{j\omega CR} - \frac{5}{\omega^2 C^2 R^2} - \frac{1}{j\omega^3 C^3 R^3} \\ &= \left( 1 - \frac{5}{\omega^2 C^2 R^2} \right) - j \left( \frac{6}{\omega CR} - \frac{1}{\omega^3 C^3 R^3} \right) \end{aligned}$$

Thus, oscillation will occur at the frequency that renders the imaginary part of the RHS zero:

$$\begin{aligned} \frac{6}{\omega_0 CR} &= \frac{1}{\omega_0^3 C^3 R^3} : \\ \Rightarrow \omega_0 &= \frac{1}{\sqrt{6}CR} \end{aligned}$$

At this frequency, the real part of the RHS must be equal to  $(-R_f/R)$ :

$$-\frac{R_f}{R} = 1 - \frac{5}{1/6} = -29$$

Thus,

$$R_f = 29R$$

which is the minimum required value for  $R_f$  to obtain sustained oscillations. Numerical values:

$$f_0 = \frac{1}{2\pi\sqrt{6} \times 16 \times 10^{-9} \times 10 \times 10^3}$$

$$= 406 \text{ Hz}$$

$$R_f = 290 \text{ k}\Omega$$

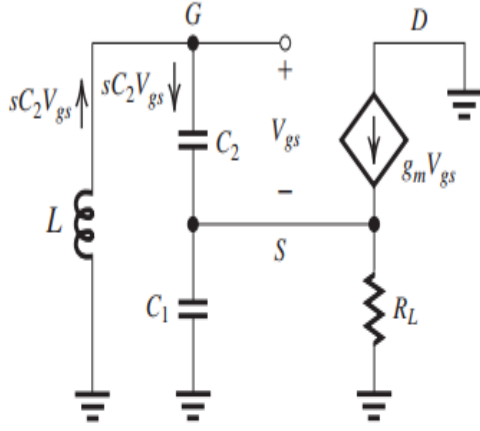


Figure 1

Figure 1 shows the equivalent circuit together with some of the analysis. The voltage at the gate,  $V_g$ , can be expressed as

$$V_g = -s^2 LC_2 V_{gs} \quad (1)$$

The voltage at the source,  $V_s$ , can be expressed as

$$V_s = V_g - V_{gs}$$

Thus,

$$V_s = -s^2 LC_2 V_{gs} - V_{gs} \quad (2)$$

A node equation at S provides

$$sC_2 V_{gs} + g_m V_{gs} = \left( \frac{1}{R_L} + sC_1 \right) V_s$$

Substituting for  $V_s$  from Eq. (2), we obtain

$$sC_2 V_{gs} + g_m V_{gs} = - \left( \frac{1}{R_L} + sC_1 \right) (s^2 LC_2 + 1) V_{gs}$$

Dividing by  $V_{gs}$  and collecting terms, we obtain

$$s^3 LC_1 C_2 + s^2 \frac{LC_2}{R_L} + s(C_1 + C_2) + \left( g_m + \frac{1}{R_L} \right) = 0$$

For  $s = j\omega$ , we have

$$j\omega[-\omega^2 LC_1 C_2 + (C_1 + C_2)] + \left( g_m + \frac{1}{R_L} - \omega^2 \frac{LC_2}{R_L} \right) = 0 \quad (3)$$

This is the equation that governs the operation of the oscillator circuit. The frequency of oscillation  $\omega_0$  is the value of  $\omega$  at which the imaginary part is zero, thus

$$\begin{aligned} \omega_0^2 &= 1 / \left[ L \left( \frac{C_1 C_2}{C_1 + C_2} \right) \right] \\ \Rightarrow \omega_0 &= 1 / \sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)} \end{aligned} \quad (4)$$

The condition for sustained oscillations can be found by equating the real part of Eq. (3) to zero and making use of (4), thus

$$\begin{aligned} g_m + \frac{1}{R_L} &= \left( \frac{C_1 + C_2}{C_1} \right) \left( \frac{1}{R_L} \right) \\ \Rightarrow g_m R_L &= \frac{C_2}{C_1} \end{aligned}$$

To ensure that oscillations start, we use

$$g_m R_L > \frac{C_2}{C_1}$$

## 14.27

$$\mathbf{14.27} \quad \omega_0 = 20 \text{ Grad/s} = 20 \times 10^9 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$20 \times 10^9 = \frac{1}{\sqrt{5 \times 10^{-9} \times C}}$$

$$\Rightarrow C = 0.5 \text{ pF}$$

$$R_p = \omega_0 L Q$$

$$= 20 \times 10^9 \times 5 \times 10^{-9} \times 10$$

$$= 1000 \, \Omega = 1 \text{ k}\Omega$$

$$r_o \parallel R_p = 5 \parallel 1 = \frac{5}{6} \text{ k}\Omega$$

$$g_{m|_{\min}} = \frac{1}{\frac{5}{6} \times 10^3} = 1.2 \text{ mA/V}$$

## 14.28

**14.28** From Exercise 14.13, we have

$$L = 0.52 \text{ H}$$

$$C_s = 0.012 \text{ pF}$$

$$C_p = 4 \text{ pF}$$

$$C_{\text{eq}} = \frac{C_s \left( C_p + \frac{C_1 C_2}{C_1 + C_2} \right)}{C_s + C_p + \frac{C_1 C_2}{C_1 + C_2}}$$

$$C_2 = 10 \text{ pF} \quad C_1 = 1 \text{ to } 10 \text{ pF}$$

$$C_L = \frac{0.012 \left( 4 + \frac{10 \times 1}{10 + 1} \right)}{\left( 0.012 + 4 + \frac{10}{11} \right)} = 0.01197 \text{ pF}$$

$$C_H = \frac{0.012 \left( 4 + \frac{10 \times 10}{10 + 10} \right)}{\left( 0.012 + 4 + \frac{100}{20} \right)} = 0.01198 \text{ pF}$$

$$\therefore f_{0H} = \frac{1}{2\pi [0.52 \times 0.01197 \times 10^{-12}]^{1/2}}$$

$$= 2.0173 \text{ MHz}$$

$$f_{0L} = \left[ 2\pi (0.52 \times 0.01198 \times 10^{-12})^{1/2} \right]^{-1}$$

$$= 2.0165 \text{ MHz}$$

$$\text{Difference} = 800 \text{ Hz}$$

## HW8

14.30

14.30

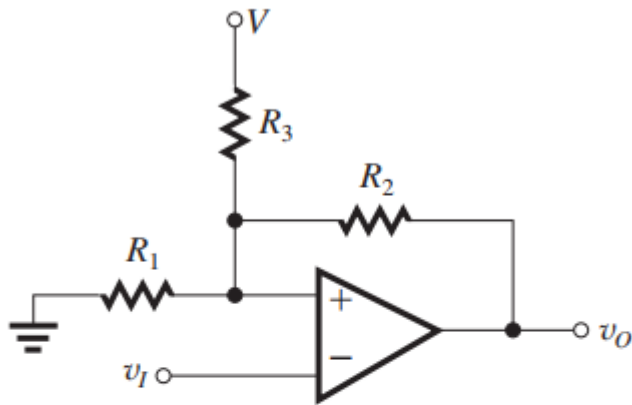


Figure 1

(a) Refer to Fig. 1. With  $v_O = L_+$ , the voltage at the op amp positive input terminal will be  $V_{TH}$ . Now, writing a node equation at the op amp positive input terminal, we have

$$\frac{V_{TH}}{R_1} = \frac{V - V_{TH}}{R_3} + \frac{L_+ - V_{TH}}{R_2}$$

$$V_{TH} \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{L_+}{R_2} + \frac{V}{R_3}$$

$$\Rightarrow V_{TH} = \left( \frac{L_+}{R_2} + \frac{V}{R_3} \right) (R_1 \parallel R_2 \parallel R_3)$$

Similarly, we can obtain

$$V_{TL} = \left( \frac{L_-}{R_2} + \frac{V}{R_3} \right) (R_1 \parallel R_2 \parallel R_3)$$

(b)  $L_+ = -L_- = 10 \text{ V}$ ,  $V = 15 \text{ V}$ ,  $R_1 = 10 \text{ k}\Omega$

$$V_{TH} = 5.1 = \left( \frac{10}{R_2} + \frac{15}{R_3} \right) (R_1 \parallel R_2 \parallel R_3)$$

$$\frac{5.1}{R_1} + \frac{5.1}{R_2} + \frac{5.1}{R_3} = \frac{10}{R_2} + \frac{15}{R_3}$$

$$0.51 = \frac{4.9}{R_2} + \frac{9.9}{R_3} \quad (1)$$

$$V_{TL} = 4.9 = \left( \frac{-10}{R_2} + \frac{15}{R_3} \right) (R_1 \parallel R_2 \parallel R_3)$$

$$\frac{4.9}{R_1} + \frac{4.9}{R_2} + \frac{4.9}{R_3} = -\frac{10}{R_2} + \frac{15}{R_3}$$

$$0.49 = \frac{-14.9}{R_2} + \frac{10.1}{R_3} \quad (2)$$

Multiplying Eq. (1) by  $\left( \frac{14.9}{4.9} \right)$ , we obtain

$$1.55 = \frac{-14.9}{R_2} + \frac{30.1}{R_3} \quad (3)$$

Adding (2) and (3) gives

$$2.04 = \frac{40.2}{R_3}$$

$$\Rightarrow R_3 = 19.7 \text{ k}\Omega$$


Substituting in Eq. (1), we obtain

$$0.51 = \frac{4.9}{R_2} + \frac{9.9}{19.7}$$

$$\Rightarrow R_2 = \frac{4.9}{0.0076} = 656.7 \text{ k}\Omega$$

14.36

14.36

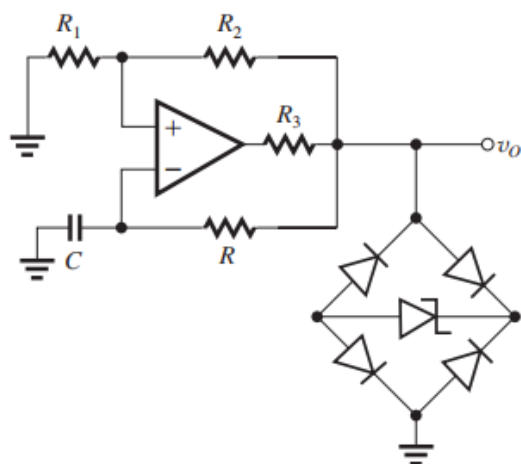

$$\beta = 0.462$$

For  $V_D = 0.7 \text{ V}$  and  $V_O = \pm 5 \text{ V}$ , we have

$$V_Z = 5 - 2V_D$$

$$V_Z = 3.6 \text{ V}$$

$$T = 2\tau \ln\left(\frac{1+\beta}{1-\beta}\right)$$

$$10^{-3} = 2\tau \ln\left(\frac{1.462}{1-0.462}\right) \Rightarrow \tau = 0.5 \text{ ms}$$


$$\tau = RC \Rightarrow R = \tau/C = 50 \text{ k}\Omega$$

$$\text{Thresholds} = \pm 0.462 \times 5 = \pm 2.31 \text{ V}$$

Average current in  $R$  in  $\frac{1}{2}$  cycle:

$$I \cong \frac{1}{R} \left( \frac{5 - 2.31 + 2.31 + 5}{2} \right)$$
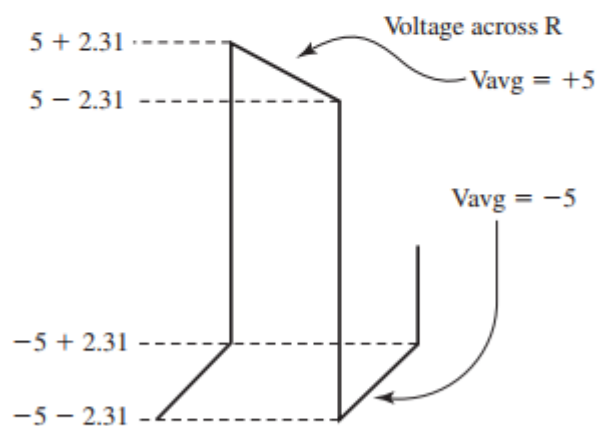
$$= \frac{5}{R} = \frac{5}{50 \text{ k}\Omega} = 0.1 \text{ mA}$$



$$R_1 + R_2 = \frac{5 \text{ V}}{0.1 \text{ mA}} = 50 \text{ k}\Omega$$

$$\frac{R_1}{R_1 + R_2} = 0.462 \rightarrow R_1 = 50 (0.462)$$

$$= 23.1 \text{ k}\Omega$$

$$\therefore R_2 = 26.9 \text{ k}\Omega$$

$$1 = \frac{13 - 5}{R_3} - 0.1 - 0.1$$

$$R_3 = \frac{8}{1.2}$$

$$= 6.67 \text{ k}\Omega$$



#### 14.40

**14.40** Choose  $C_1 = 1 \text{ nF}$  and  $C_2 = 0.1 \text{ nF}$ :

$$R_1 = R_2 = 100 \text{ k}\Omega \Rightarrow \beta \equiv \frac{1}{2}$$

$$T = C_1 R_3 \ln \left( \frac{0.7 + 13}{0.5 \times (-13) + 13} \right)$$

$$10^{-4} = 10^{-9} R_3 \ln \left( \frac{13.7}{13(0.5)} \right)$$

$$R_3 = 134.1 \text{ k}\Omega$$

Need  $R_4 \gg R_1 \Rightarrow$  choose  $R_4 = 470 \text{ k}\Omega$

The trigger pulse must be sufficiently large to lower the voltage at node  $C$  from  $\beta L_+$  to  $V_D$ , that is, from  $+6.5 \text{ V}$  to  $+0.7 \text{ V}$ ; thus it must be at least  $5.8 \text{ V}$ .

For recovery we have

$$v_B = 13 - (13 - \beta L_-) e^{-t/\tau}$$

$$= 13 - 19.5 e^{-t/\tau} = 0.7$$

$$\therefore t_{\text{recovery}} = -\tau \ln \left( \frac{12.3}{19.5} \right)$$

$$= - (134.1 \times 10^3) (10^{-9}) (-0.4608)$$

$$= 61.8 \text{ }\mu\text{s}$$