

Exercise 11-1

Ex: 11.1 To allow for v_O to reach $-V_{CC} + V_{CEsat} = -15 + 0.2 = -14.8$ V, with Q_1 just cutting off (i.e. $i_{E1} = 0$),

$$I = \frac{14.8 \text{ V}}{R_L} = \frac{14.8}{1 \text{ k}\Omega} = 14.8 \text{ mA}$$

The value of R can now be found from

$$I = \frac{V_R}{R} = \frac{V_{CC} - V_D}{R}$$

$$14.8 = \frac{15 - 0.7}{R}$$

$$\Rightarrow R = \frac{14.3}{14.8} = 0.97 \text{ k}\Omega$$

The resulting output signal swing will be -14.8 V to $+14.8$ V. The minimum current in $Q_1 = 0$. The maximum current in $Q_1 = 14.8 + 14.8 = 29.6$ mA

Ex: 11.2 At $v_O = -10$ V, we have

$$i_L = \frac{-10}{1} = -10 \text{ mA}$$

$$i_{E1} = I + i_L = 14.8 - 10 = 4.8 \text{ mA}$$

$$v_{BE1} = 0.6 + 0.025 \ln\left(\frac{4.8}{1}\right)$$

$$= 0.64 \text{ V}$$

$$v_I = v_O + v_{BE1}$$

$$= -10 + 0.64 = -9.36 \text{ V}$$

At $v_O = 0$ V, we have

$$i_L = 0 \text{ mA}$$

$$i_{E1} = I = 14.8 \text{ mA}$$

$$v_{BE1} = 0.6 + 0.025 \ln\left(\frac{14.8}{1}\right)$$

$$= 0.67 \text{ V}$$

$$v_I = v_O + v_{BE1}$$

$$= 0 + 0.67 = 0.67 \text{ V}$$

At $v_O = 10$ V

$$i_L = \frac{10}{1} = 10 \text{ mA}$$

$$i_{E1} = I + i_L = 14.8 + 10 = 24.8 \text{ mA}$$

$$v_{BE1} = 0.6 + 0.025 \ln\left(\frac{24.8}{1}\right)$$

$$= 0.68 \text{ V}$$

$$v_I = v_O + v_{BE1}$$

$$= 10 + 0.68 = 10.68 \text{ V}$$

At $v_O = -10$ V, we have

$$i_{E1} = 4.8 \text{ mA}$$

$$r_{e1} = \frac{25 \text{ mV}}{4.8 \text{ mA}} = 5.2 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + r_{e1}} = \frac{1}{1 + 0.0052} = 0.995 \text{ V/V}$$

At $v_O = 0$ V,

$$i_{E1} = 14.8 \text{ mA}$$

$$r_{e1} = \frac{25 \text{ mV}}{14.8 \text{ mA}} = 1.7 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + r_{e1}} = \frac{1}{1 + 0.0017} = 0.998 \text{ V/V}$$

At $v_O = +10$ V,

$$i_{E1} = 24.8 \text{ mA}$$

$$r_{e1} = \frac{25 \text{ mV}}{24.8 \text{ mA}} = 1.0 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + r_{e1}} = \frac{1}{1 + 0.001} = 0.999 \text{ V/V}$$

Ex: 11.3

$$\text{a. } P_L = \frac{(\hat{V}_o/\sqrt{2})^2}{R_L} = \frac{(8/\sqrt{2})^2}{100} = 0.32 \text{ W}$$

$$P_S = 2V_{CC} \times I = 2 \times 10 \times 100 \times 10^{-3}$$

$$= 2 \text{ W}$$

$$\text{Efficiency } \eta = \frac{P_L}{P_S} \times 100$$

$$= \frac{0.32}{2} \times 100$$

$$= 16\%$$

$$\text{Ex: 11.4 (a) } P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

$$= \frac{1}{2} \frac{(4.5)^2}{4} = 2.53 \text{ W}$$

$$\text{(b) } P_{S+} = P_{S-} = V_{CC} \times \frac{1}{\pi} \frac{\hat{V}_o}{R_L}$$

$$= 6 \times \frac{1}{\pi} \times \frac{4.5}{4} = 2.15 \text{ W}$$

$$\text{(c) } \eta = \frac{P_L}{P_S} \times 100 = \frac{2.53}{2 \times 2.15} \times 100$$

$$= 59\%$$

$$\text{(d) Peak input currents} = \frac{1}{\beta + 1} \frac{\hat{V}_o}{R_L}$$

$$= \frac{1}{51} \times \frac{4.5}{4}$$

$$= 22.1 \text{ mA}$$

(e) Using Eq. (11.22), we obtain

$$P_{DN\max} = P_{DP\max} = \frac{V_{CC}^2}{\pi^2 R_L}$$

$$= \frac{6^2}{\pi^2 \times 4} = 0.91 \text{ W}$$

Exercise 11-2

Ex: 11.5 (a) The quiescent power dissipated in each transistor = $I_Q \times V_{CC}$

Total power dissipated in the two transistors

$$= 2I_Q \times V_{CC}$$

$$= 2 \times 2 \times 10^{-3} \times 15$$

$$= 60 \text{ mW}$$

(b) I_Q is increased to 10 mA

At $v_O = 0$, we have $i_N = i_P = 10 \text{ mA}$

From Eq. (11.31), we obtain

$$R_{\text{out}} = \frac{V_T}{i_P + i_N} = \frac{25}{10 + 10} = 1.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 1.25}$$

$$\frac{v_o}{v_i} = 0.988 \text{ at } v_O = 0 \text{ V}$$

At $v_O = 10 \text{ V}$, we have

$$i_L = \frac{10 \text{ V}}{100 \Omega} = 0.1 \text{ A} = 100 \text{ mA}$$

Use Eq. (11.27) to calculate i_N :

$$i_N^2 - i_N i_L - I_Q^2 = 0$$

$$i_N^2 - 100 i_N - 10^2 = 0$$

$$\Rightarrow i_N = 101.0 \text{ mA}$$

Using Eq. (11.26), we obtain

$$i_P = \frac{I_Q^2}{i_N} \simeq 1 \text{ mA}$$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{101.0 + 1} \simeq 0.2451 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 0.2451} \simeq 1$$

$$\% \text{ change} = \frac{1 - 0.988}{1} \times 100 = 1.2\%$$

In Example 11.3, $I_Q = 2 \text{ mA}$, and for $v_O = 0$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{2 + 2} = 6.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 6.25} = 0.94$$

$$v_O = 10 \text{ V}$$

$$i_L = \frac{10 \text{ V}}{100 \Omega} = 100 \text{ mA}$$

Again calculate i_N (for $I_Q = 2 \text{ mA}$) using Eq. (11.27) ($i_N = 100.04 \text{ mA}$):

$$i_P = \frac{I_Q^2}{i_N} = \frac{2^2}{100.04} = 0.04 \text{ mA}$$

$$R_{\text{out}} = \frac{V_T}{i_N + i_P} = \frac{25}{100.04 + 0.04} = 0.25 \Omega$$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} \simeq 1$$

$$\% \text{ Change} = \frac{1 - 0.94}{1} \times 100 = 6\%$$

For $I_Q = 10 \text{ mA}$, change is 1.2%

For $I_Q = 2 \text{ mA}$, change is 6%

(c) The quiescent power dissipated in each transistor = $I_Q \times V_{CC}$

$$\text{Total power dissipated} = 2 \times 10 \times 10^{-3} \times 15 = 300 \text{ mW}$$

Ex: 11.6 From Example 11.4, we have $V_{CC} = 15 \text{ V}$,

$$R_L = 100 \Omega$$

Q_N and Q_P matched and $I_S = 10^{-13} \text{ A}$ and $\beta = 50$, $I_{\text{Bias}} = 3 \text{ mA}$

$$\text{For } v_O = 10 \text{ V, we have } i_L = \frac{10}{100} = 0.1 \text{ A}$$


As a first approximation, $i_N \simeq 0.1 \text{ A}$,

$$i_P = 0, i_{BN} \simeq \frac{0.1 \text{ A}}{50 + 1} \simeq 2 \text{ mA}$$

$$i_D = I_{\text{Bias}} - i_{BN} = 3 - 2 = 1 \text{ mA}$$

$$V_{BB} = 2V_T \ln \left(\frac{10^{-3}}{\frac{1}{3} \times 10^{-13}} \right) \quad (1)$$

This $\frac{1}{3}$ is because biasing diodes have $\frac{1}{3}$ area of the output devices.

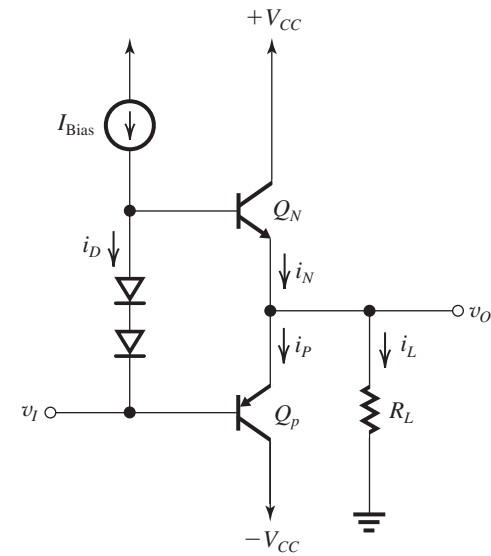

Exercise 11-3

But $V_{BB} = V_{BEN} + V_{BEP}$

$$\begin{aligned} &= V_T \ln\left(\frac{i_N}{I_S}\right) + V_T \ln\left(\frac{i_N - i_L}{I_S}\right) \\ &= V_T \ln\left[\frac{i_N (i_N - i_L)}{I_S^2}\right] \end{aligned} \quad (2)$$

Equating Eqs. 1 and 2, we obtain

$$\begin{aligned} 2V_T \ln\left(\frac{10^{-3}}{\frac{1}{3} \times 10^{-13}}\right) &= V_T \ln\left[\frac{i_N (i_N - i_L)}{I_S^2}\right] \\ \left(\frac{10^{-3}}{\frac{1}{3} \times 10^{-13}}\right)^2 &= \frac{i_N (i_N - 0.1)}{(10^{-13})^2} \end{aligned}$$

$$i_N (i_N - 0.1) = 9 \times 10^{-6}$$

If i_N is in mA, then

$$i_N (i_N - 100) = 9$$

$$i_N^2 - 100 i_N - 9 = 0$$

$$\Rightarrow i_N = 100.1 \text{ mA}$$

$$i_P = i_N - i_L = 0.1 \text{ mA}$$

$$\text{For } v_O = -10 \text{ V and } i_L = \frac{-10}{100} = -0.1 \text{ A}$$

$$= -100 \text{ mA:}$$

As a first approximation assume $i_P \cong 100 \text{ mA}$,

$i_N \cong 0$. Since $i_N = 0$, current through diodes
= 3 mA

$$\therefore V_{BB} = 2V_T \ln\left(\frac{3 \times 10^{-3}}{\frac{1}{3} \times 10^{-13}}\right) \quad (3)$$

$$\begin{aligned} \text{But } V_{BB} &= V_T \ln\left(\frac{i_N}{10^{-13}}\right) + V_T \ln\left(\frac{i_P}{10^{-13}}\right) \\ &= V_T \ln\left(\frac{i_P + i_L}{10^{-13}}\right) + V_T \ln\left(\frac{i_P}{10^{-13}}\right) \end{aligned} \quad (4)$$

Here $i_L = -0.1 \text{ A}$

Equating Eqs. (3) and (4), we obtain

$$\begin{aligned} 2V_T \ln\left(\frac{3 \times 10^{-3}}{\frac{1}{3} \times 10^{-13}}\right) &= \\ V_T \ln\left(\frac{i_P - 0.1}{10^{-13}}\right) + V_T \ln\left(\frac{i_P}{10^{-13}}\right) \\ \left(\frac{3 \times 10^{-3}}{\frac{1}{3} \times 10^{-13}}\right)^2 &= \frac{i_P (i_P - 0.1)}{(10^{-13})^2} \\ i_P (i_P - 0.1) &= 81 \times 10^{-6} \end{aligned}$$

Expressing currents in mA, we have

$$i_P (i_P - 100) = 81$$

$$i_P^2 - 100 i_P - 81 = 0$$

$$\Rightarrow i_P = 100.8 \text{ mA}$$

$$i_N = i_P + i_L = 0.8 \text{ mA}$$

Ex: 11.7 $\Delta I_C = g_m \times 2 \text{ mV} / ^\circ\text{C} \times 5 ^\circ\text{C}$, mA

where g_m is in mA/mV

$$g_m = \frac{10 \text{ mA}}{25 \text{ mV}} = 0.4 \text{ mA/mV}$$

$$\text{Thus, } \Delta I_C = 0.4 \times 2 \times 5 = 4 \text{ mA}$$

Ex: 11.8 Refer to Fig. 11.15.

(a) To obtain a terminal voltage of 1.2 V, and since β_1 is very large, it follows that

$$V_{R1} = V_{R2} = 0.6 \text{ V.}$$

Thus $I_{C1} = 1 \text{ mA}$

$$I_R = \frac{1.2 \text{ V}}{R_1 + R_2} = \frac{1.2}{2.4} = 0.5 \text{ mA}$$

$$\text{Thus, } I = I_{C1} + I_R = 1.5 \text{ mA}$$

(b) For $\Delta V_{BB} = +50 \text{ mV}$:

$$V_{BB} = 1.25 \text{ V } I_R = \frac{1.25}{2.4} = 0.52 \text{ mA}$$

$$V_{BE} = \frac{1.25}{2} = 0.625 \text{ V}$$

$$\begin{aligned} I_{C1} &= 1 \times e^{\Delta V_{BE}/V_T} = e^{0.025/0.025} \\ &= 2.72 \text{ mA} \end{aligned}$$

$$I = 2.72 + 0.52 = 3.24 \text{ mA}$$

For $\Delta V_{BB} = +100 \text{ mV}$, we have

$$V_{BB} = 1.3 \text{ V, } I_R = \frac{1.3}{2.4} = 0.54 \text{ mA}$$

$$V_{BE} = \frac{1.3}{2} = 0.65 \text{ V}$$

$$\begin{aligned} I_{C1} &= 1 \times e^{\Delta V_{BE}/V_T} = 1 \times e^{0.05/0.025} \\ &= 7.39 \text{ mA} \end{aligned}$$

$$I = 7.39 + 0.54 = 7.93 \text{ mA}$$

For $\Delta V_{BB} = +200 \text{ mV}$:

$$V_{BB} = 1.4 \text{ V, } I_R = \frac{1.4}{2.4} = 0.58 \text{ mA}$$

$$V_{BE} = 0.7 \text{ V}$$

$$I_{C1} = 1 \times e^{0.1/0.025} = 54.60 \text{ mA}$$

$$I = 54.60 + 0.58 = 55.18 \text{ mA}$$

Exercise 11-4

For $\Delta V_{BB} = -50$ mV:

$$V_{BB} = 1.15 \text{ V}, \quad I_R = \frac{1.15}{2.4} = 0.48 \text{ mA}$$

$$V_{BE} = \frac{1.15}{2} = 0.575$$

$$I_{C1} = 1 \times e^{-0.025/0.025} = 0.37 \text{ mA}$$

$$I = 0.48 + 0.37 = 0.85 \text{ mA}$$

For $\Delta V_{BB} = -100$ mV:

$$V_{BB} = 1.1 \text{ V}, \quad I_R = \frac{1.1}{2.4} = 0.46 \text{ mA}$$

$$V_{BE} = 0.55 \text{ V}$$

$$I_{C1} = 1 \times e^{-0.05/0.025} = 0.13 \text{ mA}$$

$$I = 0.46 + 0.13 = 0.59 \text{ mA}$$

For $\Delta V_{BB} = -200$ mV:

$$V_{BB} = 1.0 \text{ V}, \quad I_R = \frac{1}{2.4} = 0.417 \text{ mA}$$


$$V_{BE} = 0.5 \text{ V}$$

$$I_{C1} = 1 \times e^{-0.1/0.025} = 0.018 \text{ mA}$$

$$I = 0.43 \text{ mA}$$

Ex: 11.9 (a) From symmetry we see that all transistors will conduct equal currents and have equal V_{BE} 's. Thus,

$$v_O = 0 \text{ V}$$

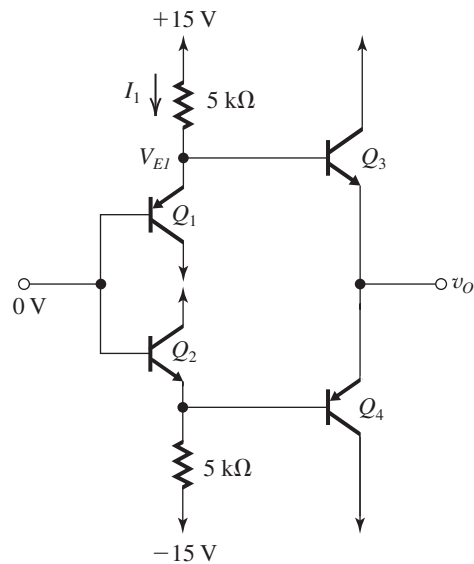

If $V_{BE} \simeq 0.7$ V, then

$$V_{E1} = 0.7 \text{ V and } I_1 = \frac{15 - 0.7}{5} = 2.86 \text{ mA}$$

If we neglect I_{B3} , then

$$I_{C1} \simeq 2.86 \text{ mA}$$

At this current, $|V_{BE}|$ is given by

$$|V_{BE}| = 0.025 \ln \left(\frac{2.86 \times 10^{-3}}{3.3 \times 10^{-14}} \right) \simeq 0.63 \text{ V}$$

Thus $V_{E1} = 0.63$ V and $I_1 = 2.87$ mA

No more iterations are required and

$$i_{C1} = i_{C2} = i_{C3} = i_{C4} \simeq 2.87 \text{ mA}$$

(b) For $v_I = +10$ V:


To start the iterations, let $V_{BE1} \simeq 0.7$ V

Thus,

$$V_{E1} = 10.7 \text{ V}$$

and
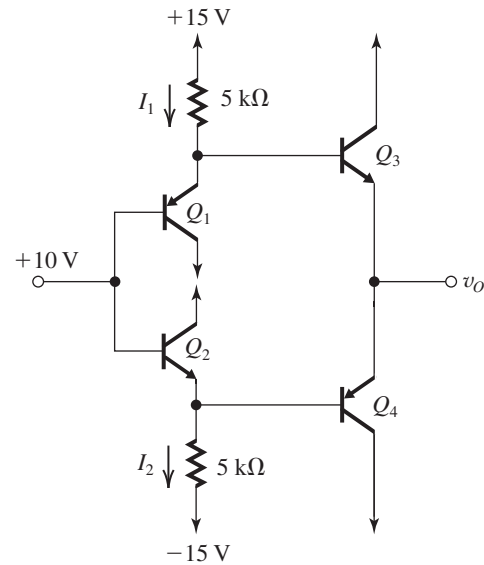
$$I_1 = \frac{15 - 10.7}{5} = 0.86 \text{ mA}$$



Neglecting I_{B3} , we obtain

$$I_{C1} \simeq I_{E1} \simeq I_1 = 0.86 \text{ mA}$$

But at this current

$$\begin{aligned} |V_{BE1}| &= V_T \ln \left(\frac{I_{C1}}{I_S} \right) \\ &= 0.025 \ln \left(\frac{0.86 \times 10^{-3}}{3.3 \times 10^{-14}} \right) \\ &= 0.6 \text{ V} \end{aligned}$$

Thus, $V_{E1} = +10.6$ V and $I_1 = 0.88$ mA. No further iterations are required and $I_{C1} \simeq 0.88$ mA.

To find I_{C2} , we use an identical procedure:

$$V_{BE2} \simeq 0.7 \text{ V}$$

$$V_{E2} = 10 - 0.7 = +9.3 \text{ V}$$

$$I_2 = \frac{9.3 - (-15)}{5} = 4.86 \text{ mA}$$

Exercise 11-5

$$V_{BE2} = 0.025 \ln \left(\frac{4.86 \times 10^{-3}}{3.3 \times 10^{-14}} \right)$$

$$= 0.643 \text{ V}$$

$$V_{E2} = 10 - 0.643 = +9.357$$

$$I_2 = 4.87 \text{ mA}$$

$$I_{C2} \simeq 4.87 \text{ mA}$$

Finally,

$$I_{C3} = I_{C4} = 3.3 \times 10^{-14} e^{V_{BE}/V_T}$$

where

$$V_{BE} = \frac{V_{E1} - V_{E2}}{2} = 0.62 \text{ V}$$

$$\text{Thus, } I_{C3} = I_{C4} = 1.95 \text{ mA}$$

The symmetry of the circuit enables us to find the values for $v_I = -10 \text{ V}$ as follows:

$$I_{C1} = 4.87 \text{ mA} \quad I_{C2} = 0.88 \text{ mA}$$

$$I_{C3} = I_{C4} = 1.95 \text{ mA}$$

$$\text{For } v_I = +10 \text{ V, we have } v_O = V_{E1} - V_{BE3}$$

$$= 10.6 - 0.62 = +9.98 \text{ V}$$

$$\text{For } v_I = -10 \text{ V, we have } v_O = V_{E1} - V_{BE3}$$

$$= -9.357 - 0.62 = -9.98 \text{ V}$$


(c) For $v_I = +10 \text{ V}$, we have

$$v_O \simeq 10 \text{ V}$$

$$I_L \simeq 100 \text{ mA}$$

$$I_{C3} \simeq 100 \text{ mA}$$
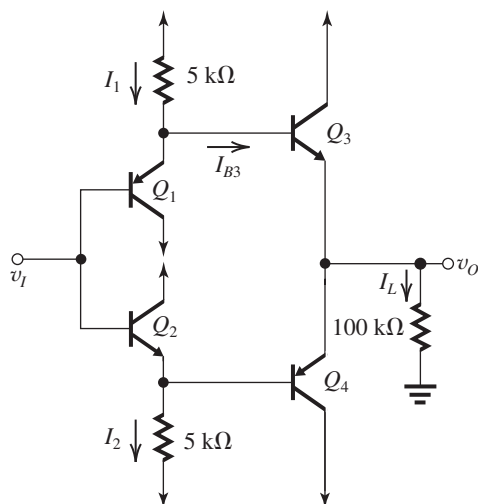
$$I_{B3} = \frac{100}{201} \simeq 0.5 \text{ mA}$$



Assuming that $|V_{BE1}|$ has not changed much from 0.6 V, then

$$V_{E1} \simeq 10.6 \text{ V}$$

$$I_1 = \frac{15 - 10.6}{5} = 0.88 \text{ mA}$$

$$I_{E1} = I_1 - I_{B3} = 0.88 - 0.5 = 0.38 \text{ mA}$$

$$I_{C1} \simeq 0.38 \text{ mA}$$

$$|V_{BE1}| = 0.025 \ln \left(\frac{0.38 \times 10^{-3}}{3.3 \times 10^{-14}} \right)$$

$$= 0.58 \text{ V}$$

$$V_{E1} = 10.58 \text{ V}$$

$$I_1 = \frac{15 - 10.58}{5} = 0.88 \text{ mA}$$

$$\text{Thus, } I_{C1} \simeq 0.38 \text{ mA}$$

Now for Q_2 we have

$$V_{BE2} = 0.643 \text{ V}$$

$$V_{E2} = 10 - 0.643 = 9.357$$

$$I_2 = 4.87 \text{ mA}$$

$$I_{B4} \simeq 0$$

$$I_{C2} \simeq 4.87 \text{ mA (as in (b))}$$

Assuming that $I_{C3} \simeq 100 \text{ mA}$, we have

$$V_{BE3} = 0.025 \ln \left(\frac{100 \times 10^{-3}}{3.3 \times 10^{-14}} \right)$$

$$= 0.72 \text{ V}$$

$$\text{Thus, } v_O = V_{E1} - V_{BE3}$$

$$= 10.58 - 0.72 = +9.86 \text{ V}$$

$$|V_{BE4}| = v_O - V_{E2}$$

$$9.86 - 9.36 = 0.5 \text{ V}$$

$$\text{Thus, } I_{C4} = 3.3 \times 10^{-14} e^{0.5/0.025}$$

$$\simeq 0.02 \text{ mA}$$

From symmetry we find the values for the case

$v_I = -10 \text{ V}$ as:

$$I_{C1} = 4.87 \text{ mA}, \quad I_{C2} = 0.38 \text{ mA}$$

$$I_{C3} = 0.02 \text{ mA}, \quad I_{C4} = 100 \text{ mA}$$

$$v_O = -9.86 \text{ V}.$$

Ex: 11.10 For Q_1 :


$$i_{C1} = I_{SP} e^{v_{EB}/V_T}$$

$$\frac{i_C}{\beta_N + 1} = I_{SP} e^{v_{EB}/V_T}$$

$$i_C \simeq \beta_N I_{SP} e^{v_{EB}/V_T}$$

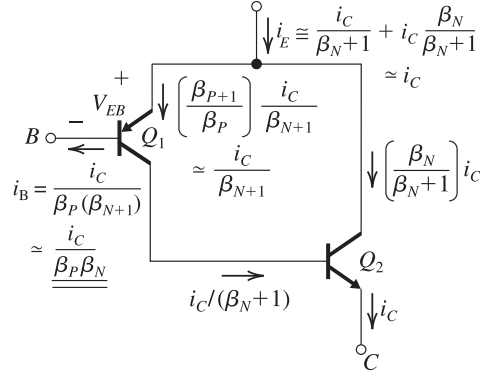Exercise 11-6

Thus, effective scale current = $\beta_N I_{SP}$



(b) Effective current gain $\equiv \frac{i_C}{i_B} = \beta_P \beta_N$

$$= 20 \times 50 = 1000$$

$$100 \times 10^{-3} = 50 \times 10^{-14} e^{v_{EB}/0.025}$$

$$v_{EB} = 0.025 \ln(2 \times 10^{11})$$

$$= 0.651 \text{ V}$$

Ex: 11.11 See Figure 11.21

When $V_{BE5} = 150 \times 10^{-3} \times R_{E1}$, then $I_{CS} = I_{Bias}$

$$= 2 \text{ mA}$$

$$V_{BE5} = V_T \ln\left(\frac{I_{CS}}{I_S}\right)$$

$$= 25 \times 10^{-3} \ln\left(\frac{2 \times 10^{-3}}{10^{-14}}\right)$$

$$= 0.651 \text{ V}$$

$$150 \times 10^{-3} R_{E1} = 0.651$$

$$R_{E1} = 4.34 \Omega$$

If peak output current = 100 mA

$$V_{BE5} = R_{E1} \times 100 \text{ mA} = 4.34 \times 100 \times 10^{-3}$$

$$= 0.434 \text{ V}$$

$$i_{CS} = I_S e^{V_{BE5}/V_T}$$

$$= 10^{-14} e^{0.434/25 \times 10^{-3}}$$

$$\simeq 0.35 \mu\text{A}$$

Ex: 11.12 Using Eq. (11.43), we obtain

$$I_Q = I_{Bias} \frac{(W/L)_n}{(W/L)_1}$$

$$1 = 0.2 \frac{(W/L)_n}{(W/L)_P}$$

$$\frac{(W/L)_n}{(W/L)_1} = 5$$

$$Q_1: I_{Bias} = \frac{1}{2} k'_n \left(\frac{W}{L}\right)_1 (V_{GS} - V_m)^2$$

$$0.2 = \frac{1}{2} \times 0.250 \left(\frac{W}{L}\right)_1 (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = 40$$

$$Q_2: I_{Bias} = \frac{1}{2} k'_p \left(\frac{W}{L}\right)_2 (V_{GS} - |V_t|)^2$$

$$0.2 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_2 \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_2 = 100$$

$$Q_N: I_Q = \frac{1}{2} k'_n \left(\frac{W}{L}\right)_N (V_{GS} - V_t)^2$$

$$1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_n 0.2^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_n = 200$$

$$Q_P: I_Q = \frac{1}{2} k'_p \left(\frac{W}{L}\right)_p (V_{GS} - |V_t|)^2$$

$$1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_p \times 0.2^2$$

$$\left(\frac{W}{L}\right)_p = 500$$

$$\text{Now } V_{GG} = V_{GS1} + V_{GS2}$$

$$= (V_{ov1} + V_t) + (V_{ov2} + |V_t|)$$

$$= (0.2 + 0.5) + (0.2 + 0.5)$$

$$= 1.4 \text{ V}$$

Ex: 11.13 $I_N = i_{Lmax} = 10 \text{ mA}$

$$\therefore 10 = \frac{1}{2} k'_n \left(\frac{W}{L}\right)_n V_{OV}^2$$

$$10 = \frac{1}{2} \times 0.250 \times 200 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.63 \text{ V}$$

Using equation 11.46, we obtain

$$v_{Omax} = V_{DD} - V_{OV}|_{Bias} - V_m - V_{OVN}$$

$$= 2.5 - 0.2 - 0.5 - 0.63$$

$$= 1.17 \text{ V}$$

Ex: 11.14 New values of W/L are

$$\left(\frac{W}{L}\right)_P = \frac{2000}{2} = 1000$$

$$\left(\frac{W}{L}\right)_N = \frac{800}{2} = 400$$

Exercise 11-7

$$I_Q = \frac{1}{2} k'_p \left(\frac{W}{L} \right)_p V_{OV}^2$$

$$1 \times 10^{-3} = \frac{1}{2} \times 0.1 \times 10^{-3} \times 1000 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.14 \text{ V}$$

Gain error

$$= -\frac{V_{OV}}{4\mu I_Q R_L} = -\frac{0.14}{4 \times 10 \times 1 \times 10^{-3} \times 100}$$

$$= -0.035$$

$$\text{Gain error} = -0.035 \times 100 = -3.5\%$$

$$g_{mn} = g_{mp} = \frac{2I_Q}{V_{OV}} = \frac{2 \times 1 \times 10^{-3}}{0.14}$$

$$= 14.14 \text{ mA/V}$$

$$R_{out} = \frac{1}{\mu(g_{mp} + g_{mn})}$$

$$= \frac{1}{10 \times (14.14 + 14.14) \times 10^{-3}}$$

$$\simeq 3.5 \Omega$$

Ex: 11.15 Total current into node $B = \frac{2v_i}{R_3} + \frac{v_o}{R_2}$


Thus

$$\left(\frac{2v_i}{R_3} + \frac{v_o}{R_2} \right) R = -\frac{v_o}{A}$$

$$\Rightarrow v_o \left(\frac{1}{A} + \frac{R}{R_2} \right) = -\frac{2R}{R_3} v_i$$

$$\frac{v_o}{v_i} = \frac{-\frac{2R}{R_3}}{\frac{1}{A} + \frac{R}{R_2}}$$
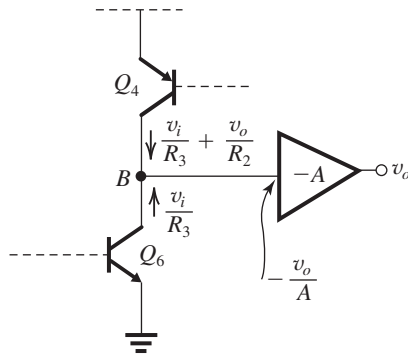
$$= \frac{-2R_2/R_3}{1 + (R_2/AR)} \quad \text{Q.E.D.}$$



For $AR \gg R_2$, we have

$$\frac{v_o}{v_i} \simeq -\frac{2R_2}{R_3}$$

Ex: 11.16 From Fig. 11.31 we see that for $P_{\text{dissipation}}$ to be less than 2.9 W, a maximum supply voltage of 20V is called for. The 20-V-supply curve intersects the 3% distortion line at a point for which the output power is 4.2 W. Since

$$P_L = \frac{(\hat{V}_o/\sqrt{2})^2}{R_L}$$

$$\text{we have } \hat{V}_o = \sqrt{4.2 \times 2 \times 8} = 8.2 \text{ V}$$

or 16.4 V peak-to-peak

Ex: 11.17 Voltage gain = 2 K

$$\text{where } K = \frac{R_4}{R_3} = 1 + \frac{R_2}{R_1} = 1.5$$

Thus, $A_v = 3 \text{ V/V}$

Input resistance = $R_3 = 10 \text{ k}\Omega$

Peak-to-Peak $v_o = 3 \times 20 = 60 \text{ V}$

$$\text{Peak load current} = \frac{30 \text{ V}}{8 \Omega} = 3.75 \text{ A}$$

$$P_L = \frac{(30/\sqrt{2})^2}{8} = 56.25 \text{ W}$$

Ex: 11.18 See Fig. 1.



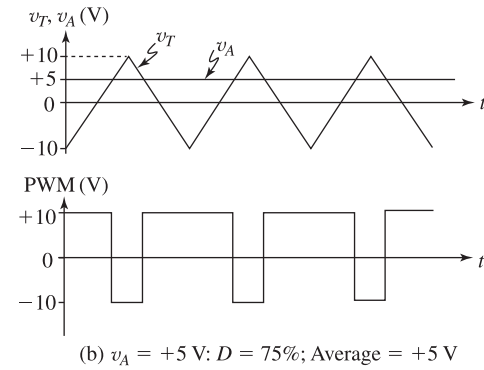
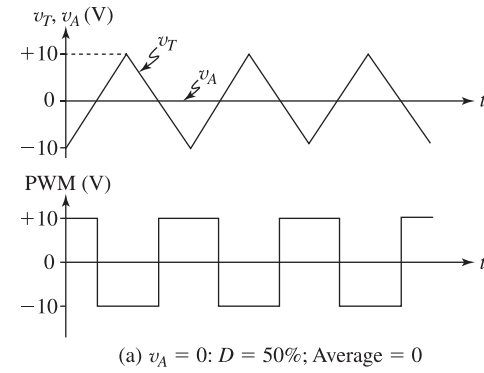


Figure 1 continued


Exercise 11-8

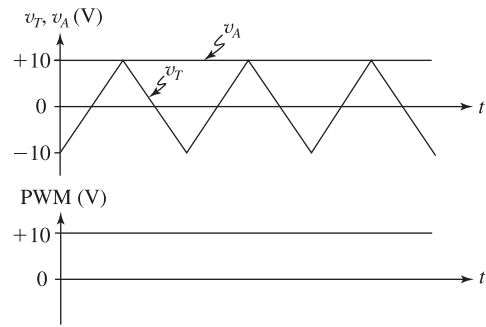

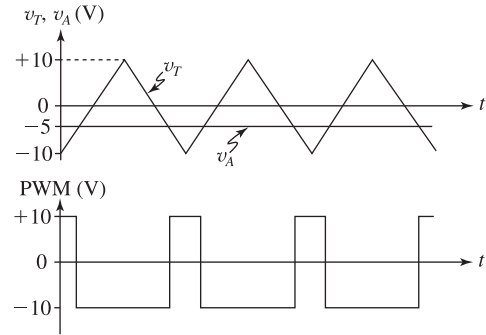(c) $v_A = +10\text{ V}$; $D = 100\%$; Average = $+10\text{ V}$



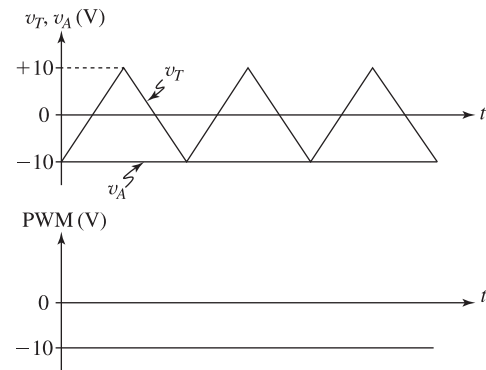(d) $v_A = -5\text{ V}$; $D = 25\%$; Average = -5 V



(e) $v_A = -10\text{ V}$; $D = 0\%$; Average = -10 V

Figure 1

Ex: 11.19

$f_s = 10 \times$ highest frequency in audio signal

$$= 10 \times 20 = 200\text{ kHz}$$

Since f_s is a decade higher than f_p , the gain will have fallen by 40 dB. Thus the PWM component at f_s will be attenuated by 40 dB.

Ex: 11.20 Maximum peak amplitude = V_{DD}

$$\text{Maximum power delivered to } R_L = \frac{(V_{DD}/\sqrt{2})^2}{R_L}$$

$$= \frac{V_{DD}^2}{2R_L}$$

For $V_{DD} = 35\text{ V}$ and $R_L = 8\ \Omega$:

Peak amplitude = 35 V

$$\text{Maximum power} = \frac{35^2}{2 \times 8} = 76.6\text{ W}$$

Power delivered by power supplies

$$= \frac{P_L}{\eta} = \frac{76.6}{0.9} = 85.1\text{ W}$$

Ex: 11.21 $T_J - T_A = \theta_{JA} P_D$

$$200 - 25 = \theta_{JA} \times 50$$

$$\theta_{JA} = \frac{175}{50} = 3.5^\circ\text{C/W}$$

But, $\theta_{JA} = \theta_{JC} + \theta_{CS} + \theta_{SA}$

$$3.5 = 1.4 + 0.6 + \theta_{SA}$$

$$\Rightarrow \theta_{SA} = 1.5^\circ\text{C/W}$$

$$T_J - T_C = \theta_{JC} \times P_D$$

$$T_C = T_J - \theta_{JC} \times P_D$$

$$= 200 - 1.4 \times 50$$

$$= 130^\circ\text{C}$$

$$\begin{aligned} 11.1 \quad I &= \frac{0 - (-V_{CC}) - V_D}{R} \\ &= \frac{10 - 0.7}{1} = 9.3 \text{ mA} \end{aligned}$$

Upper limit on $v_O = V_{CC} - V_{CEsat}$

$$= 10 - 0.3 = 9.7 \text{ V}$$

Corresponding input $= 9.7 + 0.7 = 10.4 \text{ V}$

Lower limit on $v_O = -IR_L = -9.3 \times 1$

$$= -9.3 \text{ V}$$

Corresponding input $= -9.3 + 0.7 = -8.6 \text{ V}$

If the EBJ area of Q_3 is twice as large as that of Q_2 , then

$$I = \frac{1}{2} \times 9.3 = 4.65 \text{ mA}$$

There will be no change in v_{Omax} and in the corresponding value of v_I . However, v_{Omin} will now become

$$v_{Omin} = -IR_L$$

$$= -4.65 \times 1 = -4.65 \text{ V}$$

and the corresponding value of v_I will be

$$v_I = -4.65 + 0.7 = -3.95 \text{ V}$$

If the EBJ area of Q_3 is made half as big as that of Q_2 , then

$$I = 4 \times 9.3 = 18.6 \text{ mA}$$

There will be no change in v_{Omax} and in the corresponding value of v_I . However, v_{Omin} will now become


$$v_{Omin} = -V_{CC} + V_{CEsat}$$

$$= -10 + 0.3 = -9.7 \text{ V}$$

and the corresponding value of v_I will be

$$v_I = -9.7 + 0.7 = -9 \text{ V}$$

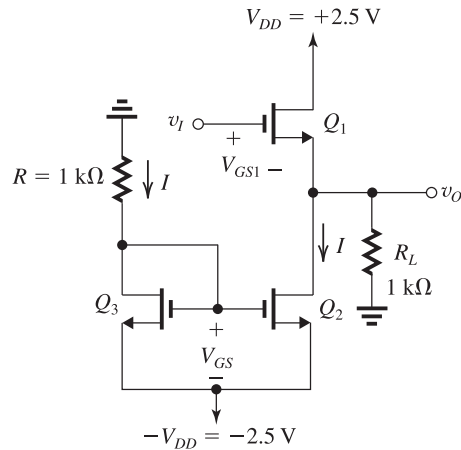11.2 First we determine the bias current I as follows:



$$I = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

But

$$V_{GS} = 2.5 - IR = 2.5 - I$$

Thus

$$I = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (2.5 - I - V_t)^2$$

$$= \frac{1}{2} \times 20 (2.5 - I - 0.5)^2$$

$$I = 10(2 - I)^2$$

$$\Rightarrow I^2 - 4.1I + 4 = 0$$

$$I = 1.6 \text{ mA and } V_{GS} = 0.9 \text{ V}$$

The upper limit on v_O is determined by Q_1 leaving the saturation region (and entering the triode region). This occurs when v_I exceeds V_{DD} by V_t volts:

$$v_{Imax} = 2.5 + 0.5 = 3 \text{ V}$$

To obtain the corresponding value of v_O , we must find the corresponding value of V_{GS1} , as follows:

$$v_O = v_I - V_{GS1}$$

$$i_L = \frac{v_O}{R_L} = \frac{v_I - V_{GS1}}{R_L} = \frac{v_I - V_{GS1}}{1}$$

$$i_L = 3 - V_{GS1}$$

$$i_{D1} = i_L + I = 3 - V_{GS1} + 1.6$$

$$= 4.6 - V_{GS1}$$

But,

$$i_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS1} - V_t)^2$$

$$4.6 - V_{GS1} = \frac{1}{2} \times 20 (V_{GS1} - 0.5)^2$$

$$\Rightarrow V_{GS1}^2 - 0.9V_{GS1} - 0.21 = 0$$

$$V_{GS1} = 1.09 \text{ V}$$

$$v_{Omax} = v_{Imax} - V_{GS1}$$

$$= 3 - 1.09 = +1.91 \text{ V}$$

The lower limit of v_O is determined either by Q_1 cutting off,

$$v_O = -IR_L = -1.6 \times 1 = -1.6 \text{ V}$$

or by Q_2 leaving saturation,

$$v_O = -V_{DD} + V_{OV2}$$

where

$$V_{OV2} = V_{GS2} - V_t = 0.9 - 0.5 = 0.4 \text{ V}$$

Thus,

$$v_O = -2.5 + 0.4 = -2.1 \text{ V}$$

We observe that Q_1 will cut off before Q_2 leaves saturation, thus

$$v_{Omin} = -1.6 \text{ V}$$

and the corresponding value of v_I will be

$$\begin{aligned} v_{Imin} &= v_{Omin} + V_t \\ &= -1.6 + 0.5 = -1.1 \text{ V} \end{aligned}$$

11.3 Refer to Fig. 11.2. For a load resistance of 100Ω and v_O ranging between -5 V and $+5 \text{ V}$, the maximum current through Q_1 is

$$\begin{aligned} I + \frac{5}{0.1} &= I + 50, \text{ mA and the minimum current} \\ \text{is } I - \frac{5}{0.1} &= I - 50, \text{ mA.} \end{aligned}$$

For a current ratio of 15, we have

$$\frac{I + 50}{I - 50} = 15$$

$$\Rightarrow I = 57.1 \text{ mA}$$

$$R = \frac{9.3 \text{ V}}{57.1 \text{ mA}} = 163 \Omega$$

The incremental voltage gain is $A_v = \frac{R_L}{R_L + r_{e1}}$

For $R_L = 100 \Omega$;

At $v_O = +5 \text{ V}$, $i_{E1} = 57.1 + 50 = 107.1 \text{ mA}$

$$r_{e1} = \frac{25}{107.1} = 0.233 \Omega$$

$$A_v = \frac{100}{100 + 0.233} = 0.998 \text{ V/V}$$

At $v_O = 0 \text{ V}$, $i_{E1} = 57.1 \text{ mA}$

$$r_{e1} = \frac{25}{57.1} = 0.438 \Omega$$

$$A_v = \frac{100}{100.438} = 0.996 \text{ V/V}$$

At $v_O = -5 \text{ V}$, $i_{E1} = 57.1 - 50 = 7.1 \text{ mA}$

$$r_{e1} = \frac{25}{7.1} = 3.52 \Omega$$

$$A_v = \frac{100}{103.52} = 0.966 \text{ V/V}$$


Thus the incremental gain changes by $0.998 - 0.966 = 0.032$ or about 3% over the range of v_O .

11.4 Refer to Fig. 11.2. With $V_{CC} = +5 \text{ V}$, the upper limit on v_O is 4.7 V , which is greater than the required value of $+3 \text{ V}$. To obtain a lower limit of -3 V , we select I so that

$$IR_L = 3$$

$$\Rightarrow I = 3 \text{ mA}$$

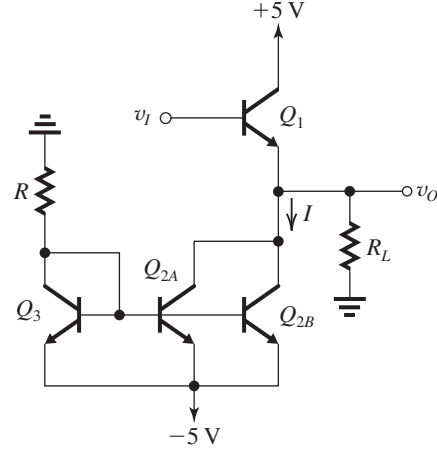Since we are provided with four devices, we can minimize the total supply current by paralleling two devices to form Q_2 as shown below.



The resulting supply current will be $3 \times \frac{I}{2}$ rather than $2I$ which is the value obtained in the circuit of Fig. 11.2. Then the supply current is 4.5 mA . The value of R is found from


$$R = \frac{4.3 \text{ V}}{1.5 \text{ mA}} = 2.87 \text{ k}\Omega$$

In a practical design we would select a standard value for R that results in I somewhat larger than 3 mA . Say, $R = 2.7 \text{ k}\Omega$. In this case $I = 3.2 \text{ mA}$.

Power from negative supply $= 3 \times 1.6 \times 5 = 24 \text{ mW}$.

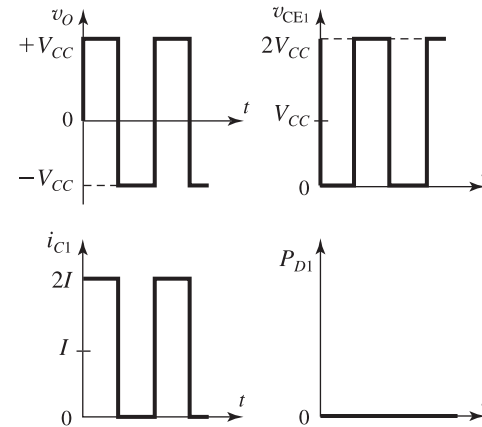
11.5 Refer to Figs. 11.2 and 11.4.

For v_O being a square wave of $\pm V_{CC}$ levels:



$P_{D1}|_{\text{average}} = 0$. For the corresponding sine wave curve [Fig. 11.4], we have $P_{D1}|_{\text{avg}} = \frac{1}{2} V_{CC} I$.

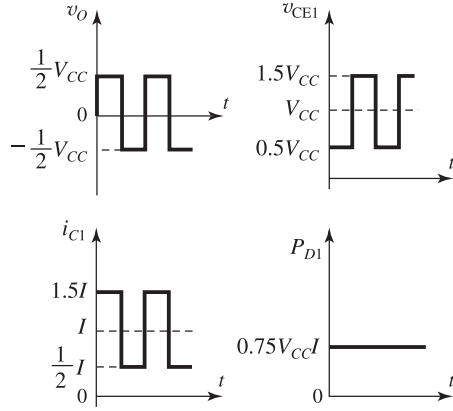For v_O being a square wave of $\pm V_{CC}/2$ levels:



$$P_{D1}|_{\text{average}} = 0.75V_{CC}I$$

For a sine-wave output of $V_{CC}/2$ peak amplitude:

$$v_O = \frac{1}{2} V_{CC} \sin \theta$$

$$i_{C1} = I + \frac{\frac{1}{2}V_{CC}}{R_L} \sin \theta = I + \frac{1}{2}I \sin \theta$$

$$v_{CE1} = V_{CC} - \frac{1}{2}V_{CC} \sin \theta$$

$$P_{D1} = \left(V_{CC} - \frac{1}{2}V_{CC} \sin \theta \right) \left(I + \frac{1}{2}I \sin \theta \right)$$

$$= V_{CC}I - \frac{1}{4}V_{CC}I \sin^2 \theta$$

$$= V_{CC}I - \frac{1}{4}V_{CC}I \times \frac{1}{2} (1 - \cos 2\theta)$$

$$= \frac{7}{8}V_{CC}I + \frac{1}{8}V_{CC}I \cos 2\theta$$

$$P_{D1}|_{\text{average}} = \frac{7}{8}V_{CC}I$$

11.6 In all cases, the average voltage across Q_2 is equal to V_{CC} . Thus, since Q_2 conducts a constant current I , its average power dissipation is $V_{CC}I$.

11.7 The minimum required value of V_{CC} is

$$V_{CC} = \hat{V}$$

and the minimum required value of I is

$$I = \frac{\hat{V}}{R_L}$$

From Eq. (11.10),


$$\eta = \frac{1}{4} \left(\frac{\hat{V}_o}{IR_L} \right) \left(\frac{\hat{V}_o}{V_{CC}} \right)$$

$$= \frac{1}{4} \left(\frac{\hat{V}}{\hat{V}} \right) \left(\frac{\hat{V}}{\hat{V}} \right) = 0.25$$

or 25%

11.8 Refer to Figs. 11.6 and 11.7. A 10% loss in peak amplitude is obtained when the amplitude of the input signal is 5 V.

11.9

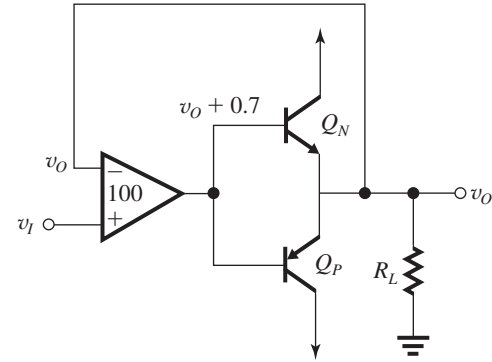

With v_I sufficiently positive so that Q_N is conducting, the situation shown obtains. Then,

$$(v_I - v_O) \times 100 = v_O + 0.7$$

$$\Rightarrow v_O = \frac{1}{1.01} (v_I - 0.007)$$

This relationship applies for $v_I \geq 0.007$.


Similarly, for v_I sufficiently negative so that Q_P conducts, the voltage at the output of the amplifier becomes $v_O - 0.7$, thus

$$(v_I - v_O) \times 100 = v_O - 0.7$$

$$\Rightarrow v_O = \frac{1}{1.01} (v_I + 0.007)$$


This relationship applies for $v_I \leq -0.007$.

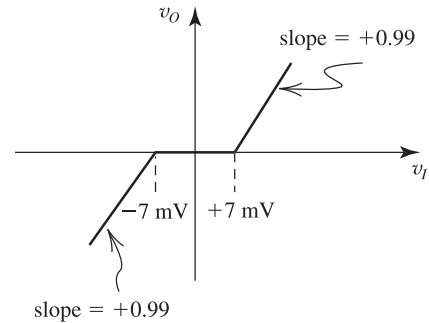The result is the transfer characteristic



Without the feedback arrangement, the deadband becomes ± 700 mV and the slope change a little (to nearly $+1$ V/V).

11.10

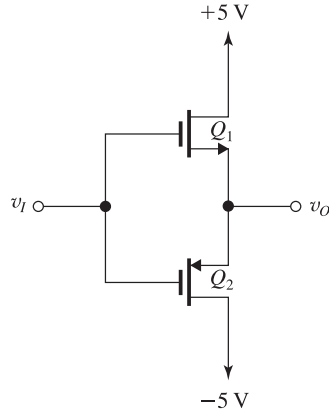

Devices have $|V_t| = 0.5$ V

$$\mu C_{ox} \frac{W}{L} = 2 \text{ mA/V}^2$$

For $R_L = \infty$, the current is normally zero, so

$$V_{GS} = V_t$$

$$\therefore v_O = v_I - V_{GS1} = 5 - 0.5 = 4.5 \text{ V}$$


The peak output voltage will be 4.5 V

$$\sin \theta = \frac{0.5}{5} \Rightarrow \theta = 5.74^\circ$$

$$\text{Crossover interval} = 4\theta = 22.968$$

$$= \frac{22.96}{360} \times 100$$

$$= 6.4\%$$

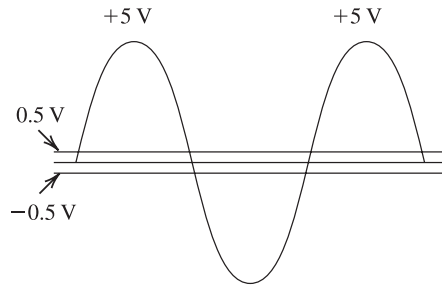


For $v_I = 5$ V, $v_O = 2.5$ V:

$$\therefore V_{GS} = 5 - 2.5 = 2.5 \text{ V}$$

$$i_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$
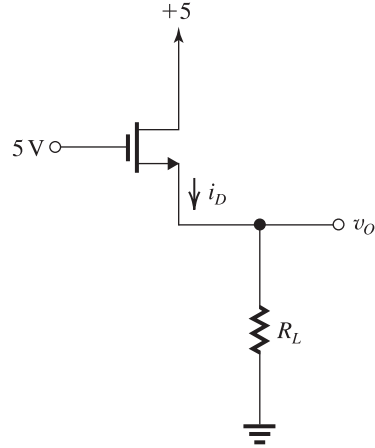
$$= \frac{1}{2} \times 2 \times (2.5 - 0.5)^2$$



$$i_D = 4 \text{ mA and } R_L = \frac{2.5 \text{ V}}{4 \text{ mA}} = 625 \Omega$$

11.11 For $V_{CC} = 10$ V and $R_L = 8 \Omega$, the maximum sine-wave output power occurs when

$$\hat{V}_o = V_{CC} \text{ and is } P_{L\max} = \frac{1}{2} \frac{V_{CC}^2}{R_L}$$

$$= \frac{1}{2} \times \frac{100}{8} = 6.25 \text{ W}$$

Correspondingly,

$$P_{S+} = P_{S-} = \frac{1}{\pi} \frac{\hat{V}_o}{R_L} V_{CC}$$

$$= \frac{1}{\pi} \times \frac{10}{8} \times 10 = 3.98 \text{ W}$$

for a total supply power of

$$P_S = 2 \times 3.98 = 7.96 \text{ W}$$

The power conversion efficiency η is

$$\eta = \frac{P_L}{P_S} \times 100 = \frac{6.25}{7.96} \times 100 = 78.5\%$$

For $\hat{V}_o = 5$ V,

$$P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L} = \frac{1}{2} \times \frac{25}{8} = 1.56 \text{ W}$$

$$P_{S+} = P_{S-} = \frac{1}{\pi} \frac{\hat{V}_o}{R_L} V_{CC}$$

$$= \frac{1}{\pi} \times \frac{5}{8} \times 10 = 2 \text{ W}$$

$$P_S = 4 \text{ W}$$

$$\eta = \frac{1.56}{4} \times 100 = 39\%$$

Thus, the efficiency reduces to half its maximum value.

$$\mathbf{11.12} \quad P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

$$50 = \frac{1}{2} \frac{\hat{V}_o^2}{8}$$

$$\Rightarrow \hat{V}_o = 28.3 \text{ V}$$

$$V_{CC} = 28.3 + 4 = 32.3 \rightarrow 33 \text{ V}$$

$$\text{Peak current from each supply} = \frac{\hat{V}_o}{R_L} = \frac{28.3}{8}$$

$$= 3.54 \text{ A}$$

$$P_{S+} = P_{S-} = \frac{1}{\pi} \times 3.54 \times 33 = 37.2 \text{ W}$$

Thus,

$$P_S = 2 \times 37.2 = 74.4 \text{ W}$$

$$\eta = \frac{P_L}{P_S} = \frac{50}{74.4} = 67.2\%$$

Using Eq. (11.22), we obtain

$$P_{DN\max} = P_{DP\max} = \frac{V_{CC}^2}{\pi^2 R_L} = \frac{33^2}{\pi^2 \times 8} = 13.8 \text{ W}$$

$$\mathbf{11.13} \quad V_{CC} = 10 \text{ V}$$

For maximum η ,

$$\hat{V}_o = V_{CC} = 10 \text{ V}$$

The output voltage that results in maximum device dissipation is given by Eq. (11.20),

$$\hat{V}_o = \frac{2}{\pi} V_{CC}$$

$$= \frac{2}{\pi} \times 10 = 6.37 \text{ V}$$

If operation is always at full output voltage, $\eta = 78.5\%$ and thus

$$\begin{aligned} P_{\text{dissipation}} &= (1 - \eta) P_S \\ &= (1 - \eta) \frac{P_L}{\eta} = \frac{1 - 0.785}{0.785} P_L = 0.274 P_L \end{aligned}$$

$$P_{\text{dissipation/device}} = \frac{1}{2} \times 0.274 P_L = 0.137 P_L$$

For a rated device dissipation of 2 W, and using a factor of 2 safety margin,

$$P_{\text{dissipation/device}} = 1 \text{ W}$$

$$= 0.137 P_L$$

$$\Rightarrow P_L = 7.3 \text{ W}$$

$$7.3 = \frac{1}{2} \times \frac{100}{R_L}$$

$$\Rightarrow R_L = 6.85 \Omega \text{ (i.e. } R_L \geq 6.85 \Omega \text{)}$$

The corresponding output power (i.e., greatest possible output power) is 7.3 W.

$$\text{If operation is allowed at } \hat{V}_o = \frac{1}{2} V_{CC} = 5 \text{ V,}$$

$$\eta = \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}} \text{ (Eq. 11.15)}$$

$$= \frac{\pi}{4} \times \frac{1}{2} = 0.393$$

$$P_{\text{dissipation/device}} = \frac{1}{2} \frac{1 - \eta}{\eta} P_L = 0.772 P_L$$

$$1 = 0.772 P_L$$

$$\Rightarrow P_L = 1.3 \text{ W}$$

$$= \frac{1}{2} \frac{5^2}{R_L}$$

$$\Rightarrow R_L = 9.62 \Omega \text{ (i.e., } \geq 9.62 \Omega \text{)}$$

$$\mathbf{11.14} \quad P_L = \frac{\hat{V}_o^2}{R_L}$$

$$P_{S+} = P_{S-} = \frac{1}{2} \left(\frac{\hat{V}_o}{R_L} \right) V_{SS}$$

$$P_S = \frac{\hat{V}_o}{R_L} V_{SS}$$

$$\eta = \frac{P_L}{P_S} = \frac{\hat{V}_o^2 / R_L}{\hat{V}_o V_{SS} / R_L} = \frac{\hat{V}_o}{V_{SS}}$$

$$\eta_{\max} = 1 (100\%), \text{ obtained for } \hat{V}_o = V_{SS}$$

$$P_{L\max} = \frac{V_{SS}^2}{R_L}$$

$$P_{\text{dissipation}} = P_S - P_L$$

$$= \frac{\hat{V}_o}{R_L} V_{SS} - \frac{\hat{V}_o^2}{R_L}$$

$$\frac{\partial P_{\text{dissipation}}}{\partial \hat{V}_o} = \frac{V_{SS}}{R_L} - \frac{2\hat{V}_o}{R_L}$$

$$= 0 \text{ for } \hat{V}_o = \frac{V_{SS}}{2}$$

$$\text{Correspondingly, } \eta = \frac{V_{SS}/2}{V_{SS}} = \frac{1}{2} \text{ or } 50\%$$

$$\mathbf{11.15} \quad V_{BB} = 2V_T \ln(I_Q/I_S)$$

$$= 2 \times 0.025 \ln(10^{-3}/10^{-14})$$

$$= 1.266 \text{ V}$$

At $v_I = 0$, $i_N = i_P = I_Q = 1 \text{ mA}$, we have

$$r_{eN} = r_{eP} = \frac{25 \text{ mV}}{1 \text{ mA}} = 25 \Omega$$

$$R_{\text{out}} = r_{eN} \parallel r_{eP} = 12.5 \Omega$$

$$\begin{aligned} A_v &= \frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 12.5} \\ &= 0.889 \text{ V/V} \end{aligned}$$

At $v_O = 10 \text{ V}$, we have

$$i_L = \frac{10}{100} = 0.1 \text{ A} = 100 \text{ mA}$$

To obtain i_N , we use Eq. (11.27):

$$i_N^2 - i_L i_N - I_Q^2 = 0$$

$$i_N^2 - 100 i_N - 1 = 0$$

$$\Rightarrow i_N = 100.01 \text{ mA}$$

$$i_P = i_N - i_L = 0.01 \text{ mA}$$

$$R_{\text{out}} = \frac{V_T}{i_P + i_N} \simeq \frac{25 \text{ mV}}{100 \text{ mA}} = 0.25 \Omega$$

$$A_v = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + 0.25} = 0.998 \text{ V/V}$$

11.16 At $i_L = 0$, we have $i_N = i_P = I_Q$ and

$$R_{\text{out}} = \frac{1}{2} \frac{V_T}{I_Q}$$

Thus,

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}} = \frac{100}{100 + \frac{12.5}{I_Q}} \quad (1)$$

where I_Q is in mA.

For $i_L = 50 \text{ mA}$, we have

$$i_N \simeq 50 \text{ mA and } i_P \simeq 0$$

Thus,

$$R_{\text{out}} \simeq r_{eN} = \frac{V_T}{i_N} = \frac{25 \text{ mV}}{50 \text{ mA}} = 0.5 \Omega$$

$$\frac{v_o}{v_i} = \frac{100}{100 + 0.5} = 0.995 \text{ V/V}$$

To limit the variation to 5%, we use

$$\left. \frac{v_o}{v_i} \right|_{i_L=0} = 0.995 - 0.05 = 0.945 \text{ V/V}$$

Substituting this value in Eq. (1) yields

$$I_Q = 2.15 \text{ mA}$$

$$\mathbf{11.17} \quad A_v = \frac{R_L}{R_L + R_{\text{out}}} \text{ and } R_{\text{out}} = \frac{r_e}{2} = \frac{V_T}{2I_Q}$$

Now $A_v \geq 0.97$ for $R_L \geq 100 \Omega$

$$\therefore 0.97 = \frac{100}{100 + R_{\text{out}}}$$

$$\Rightarrow R_{\text{out}} \simeq 3 \Omega$$

$$R_{\text{out}} = 3 = \frac{V_T}{2I_Q}$$

$$I_Q = \frac{V_T}{6} = \frac{25 \times 10^{-3}}{6} = 4.17 \text{ mA}$$

$$V_{BB} = 2V_{BE} = 2 \left[0.7 + V_T \ln \left(\frac{4.17}{100} \right) \right]$$

$$= 1.24 \text{ V}$$

11.18 The current i_I can be obtained as

$$i_I = \frac{i_N}{\beta_N + 1} - \frac{i_P}{\beta_P + 1} = \frac{i_L}{\beta + 1}$$

where $\beta_N = \beta_P = \beta = 49$

Using values of v_I from the table, one can evaluate R_{in} as

$$R_{\text{in}} = \frac{v_I}{i_I}$$

Using the resistance reflection rule

$$R_{\text{in}} \simeq (\beta + 1)R_L = 50 \times 100$$

$$= 5000 \Omega$$

For large input signal, the two values of R_{in} are somewhat the same. For the small values of v_I , the calculated value in the table is larger.

This table belongs to Problem 11.18.

v_O (V)	i_L (mA)	i_N (mA)	i_P (mA)	v_{BE} (V)	v_{EB} (V)	v_i (V)	v_o/v_I (V/V)	R_{out} (Ω)	v_o/v_i (V/V)	i_I (mA)	R_{in} (Ω)
+10.0	100	100.04	0.04	0.691	0.495	10.1	0.99	0.25	1.00	2	5050
+5.0	50	50.08	0.08	0.673	0.513	5.08	0.98	0.50	1.00	1	5080
+1.0	10	10.39	0.39	0.634	0.552	1.041	0.96	2.32	0.98	0.2	5205
+0.5	5	5.70	0.70	0.619	0.567	0.526	0.95	4.03	0.96	0.1	5260
+0.2	2	3.24	1.24	0.605	0.581	0.212	0.94	5.58	0.95	0.04	5300
+0.1	1	2.56	1.56	0.599	0.587	0.106	0.94	6.07	0.94	0.02	5300
0	0	2	2	0.593	0.593	0	—	6.25	0.94	0	
-0.1	-1	1.56	2.56	0.587	0.599	-0.106	0.94	6.07	0.94	-0.02	5300
-0.2	-2	1.24	3.24	0.581	0.605	-0.212	0.94	5.58	0.95	-0.04	5300
-0.5	-5	0.70	5.70	0.567	0.619	-0.526	0.95	4.03	0.96	-0.1	5260
-1.0	-10	0.39	10.39	0.552	0.634	-1.041	0.96	2.32	0.98	-0.2	5205
-5.0	-50	0.08	50.08	0.513	0.673	-5.08	0.98	0.50	1.00	-1	5080
-10.0	-100	0.04	100.04	0.495	0.691	-10.1	0.99	0.25	1.00	-2	5050

$$11.19 \quad \frac{v_o}{v_i} = \frac{R_L}{R_L + R_{out}} \text{ and}$$

$$R_{out} = \frac{V_T}{i_P + i_N} = \frac{V_T}{I_Q + I_Q} \text{ at } v_O = 0$$

$$(a) \quad \epsilon = 1 - \left. \frac{v_o}{v_i} \right|_{v_O=0}$$

$$= 1 - \frac{R_L}{R_L + R_{out}} = 1 - \frac{R_L}{R_L + \frac{V_T}{2I_Q}} =$$

$$\frac{V_T/2I_Q}{R_L + (V_T/2I_Q)}$$

$$\epsilon = \frac{V_T/2I_Q}{R_L + (V_T/2I_Q)} = \frac{V_T}{2R_L I_Q + V_T}$$

If $2I_Q R_L \gg V_T$, then we have

$$\epsilon \simeq \frac{V_T}{2I_Q R_L} \quad \text{Q.E.D.}$$

$$(b) \quad \text{Quiescent power dissipation} = 2V_{CC}I_Q = P_D$$

$$(c) \quad \epsilon \times \text{Quiescent power dissipation} =$$

$$\frac{V_T}{2I_Q R_L} \times 2V_{CC}I_Q = V_T \times \left(\frac{V_{CC}}{R_L} \right)$$

$$\therefore \epsilon P_D = V_T \left(\frac{V_{CC}}{R_L} \right)$$

$$(d) \quad \epsilon P_D = V_T \frac{V_{CC}}{R_L} = 25 \times 10^{-3} \times \frac{10}{100}$$

$$= 2.5 \text{ mW}$$

$$P_D = \frac{2.5 \times 10^{-3}}{\epsilon}$$

ϵ	P_D (mW)	I_Q (mA)
0.05	50	2.5
0.02	125	6.25
0.01	250	12.5

$$11.20 \quad I_Q = 1 \text{ mA}$$

For output of -1 V , we have

$$i_L = -\frac{1}{100} = -10 \text{ mA}$$

Using Eq. (11.27), we obtain

$$i_N^2 - i_L i_N - I_Q^2 = 0$$

$$i_N^2 + 10i_N - 1 = 0$$

$$i_N = 0.1 \text{ mA}$$

$$i_P = 10.1 \text{ mA}$$

$$\text{Thus } v_{EBP} \text{ increases by } V_T \ln \frac{10.1}{1} = 0.06 \text{ V}$$

and the input step must be -1.06 V .

Largest possible positive output from 6 to 10, i.e., 4 V

Largest negative output from 6 to 0, i.e., 6 V

$$11.21 \quad R_{out} = r_e/2 = 8 \Omega$$

$$\Rightarrow r_e = 16 \Omega$$

$$I_Q = \frac{V_T}{r_e} = \frac{25}{16} = 1.56 \text{ mA}$$

$$\text{Thus, } n = \frac{1.56}{0.2} = 7.8$$

11.22 $I_Q \simeq I_{BIAS} = 1 \text{ mA}$, neglecting the base current of Q_N . More precisely,

$$I_Q = I_{BIAS} - \frac{I_Q}{\beta + 1}$$

$$\Rightarrow I_Q = \frac{I_{BIAS}}{1 + \frac{1}{\beta + 1}} \simeq 0.98 \times 1 = 0.98 \text{ mA}$$

The largest positive output is obtained when all of I_{BIAS} flows into the base of Q_N , resulting in

$$v_O = (\beta_N + 1)I_{BIAS}R_L$$

$$= 51 \times 1 \times 100 \Omega = 5.1 \text{ V}$$

The largest possible negative output voltage is limited by the saturation of Q_P to

$$-10 + V_{ECsat} = -10 \text{ V}$$

To achieve a maximum positive output of 10 V without changing I_{BIAS} , β_N must be

$$10 = (\beta_N + 1) \times 1 \times 10^{-3} \times 100 \Omega$$

$$\Rightarrow \beta_N = 99$$

Alternatively, if β_N is held at 50, I_{BIAS} must be increased so that

$$10 = 51 \times I_{BIAS} \times 10^{-3} \times 100 \Omega$$

$$\Rightarrow I_{BIAS} = 1.96 \text{ mA}$$

for which

$$I_Q = \frac{I_{BIAS}}{1 + \frac{1}{\beta + 1}} = 1.92 \text{ mA}$$

11.23 Figure 1(a) shows the small-signal equivalent circuit of the class AB circuit in Fig. 11.14. Here, each of Q_N and Q_P has been replaced with its hybrid- π model, and the small resistances of the diodes have been neglected. As well, we have not included r_o of each of Q_N and Q_P .

The circuit in Fig. 1(a) can be simplified to that in Fig. 1(b) where

$$r_\pi = r_{\pi N} \parallel r_{\pi P} \quad (1)$$

$$g_m = g_{mN} + g_{mP} \quad (2)$$

This figure belongs to Problem 11.23.

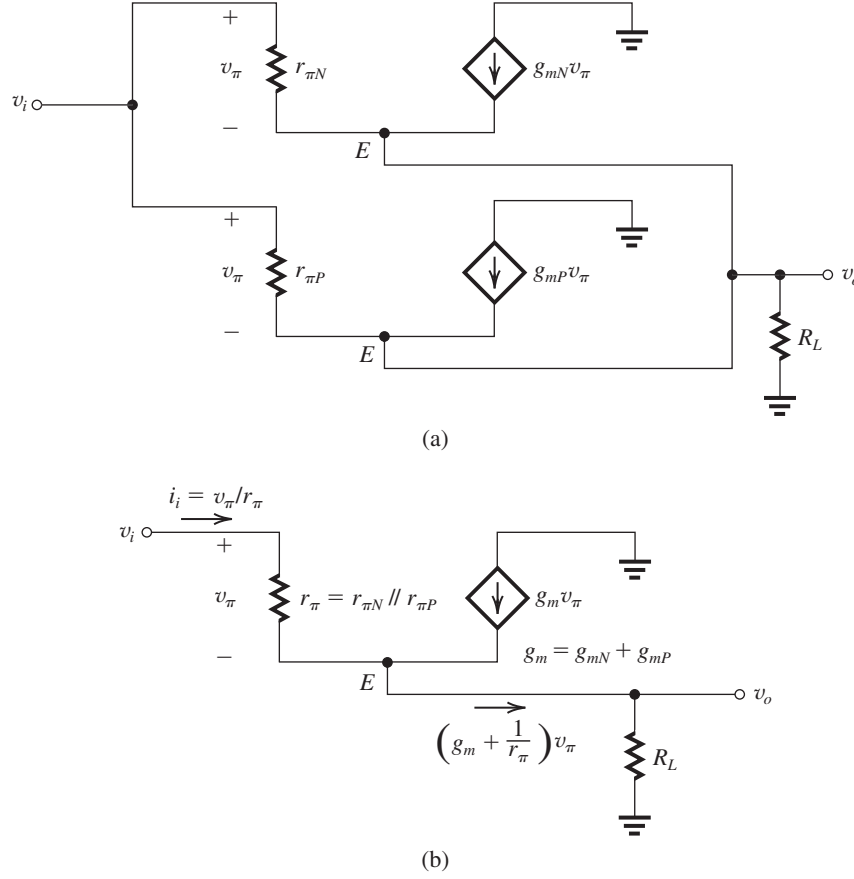


Figure 1

Since $g_m \simeq \frac{1}{r_e}$, then from (2) we obtain

$$\frac{1}{r_e} = \frac{1}{r_{eN}} + \frac{1}{r_{eP}}$$

or, equivalently,

$$r_e = r_{eN} \parallel r_{eP} \quad (3)$$

We observe that the circuit in Fig. 1(b) is the equivalent circuit of an emitter follower with the small-signal parameters r_{π} , g_m , and r_e given in Eqs. (1), (2), and (3). Furthermore, its β is given by

$$\beta = g_m r_{\pi} = (g_{mN} + g_{mP})(r_{\pi N} \parallel r_{\pi P}) \quad (4)$$

For the circuit in Fig. 1(b), we can write

$$v_i = v_{\pi} + v_o \quad (5)$$

$$v_o = \left(g_m + \frac{1}{r_{\pi}} \right) v_{\pi} R_L \quad (6)$$

Equations (5) and (6) can be used to obtain the incremental (or small-signal) gain,

$$\frac{v_o}{v_i} = \frac{\left(g_m + \frac{1}{r_{\pi}} \right) R_L}{\left(g_m + \frac{1}{r_{\pi}} \right) R_L + 1}$$

But,

$$g_m + \frac{1}{r_{\pi}} = \frac{1}{r_e}$$

Thus,

$$\frac{v_o}{v_i} = \frac{R_L / r_e}{R_L / r_e + 1}$$

$$\Rightarrow \frac{v_o}{v_i} = \frac{R_L}{R_L + r_e} = \frac{R_L}{R_L + (r_{eN} \parallel r_{eP})}$$

Q.E.D. (7)

The input resistance is found as follows:

$$R_{in} = \frac{v_i}{i_i} = \frac{v_i}{v_{\pi} / r_{\pi}}$$

Substituting for v_i from (5) together with utilizing (7) gives

$$\begin{aligned} R_{in} &= \frac{v_{\pi} \left[1 + \left(g_m + \frac{1}{r_{\pi}} \right) R_L \right]}{v_{\pi}/r_{\pi}} \\ &= r_{\pi} + (g_m r_{\pi} + 1) R_L \\ &= r_{\pi} + (\beta + 1) R_L \\ &= (\beta + 1)(R_L + r_e) \\ &\simeq \beta[R_L + (r_{eN} \parallel r_{eP})] \quad \text{Q.E.D.} \end{aligned} \quad (8)$$

11.24 Refer to Fig. P11.24. Neglecting the small resistances of D_1 and D_2 , we can write for the voltage gain of the CE amplifier transistor Q_3 ,

$$\frac{v_{c3}}{v_i} = -g_{m3} R_{in} \quad (1)$$

where R_{in} is the input resistance of the class AB circuit, given in the statement of Problem 11.23 as

$$R_{in} \simeq \beta[R_L + (r_{eN} \parallel r_{eP})] \quad (2)$$

where

$$\beta = (g_{mN} + g_{mP})(r_{\pi N} \parallel r_{\pi P}) \quad (3)$$

The voltage gain of the class AB circuit is given in the statement of Problem 11.23 as

$$\frac{v_o}{v_{c3}} = \frac{R_L}{R_L + (r_{eN} \parallel r_{eP})} \quad (4)$$

Now, we can combine (1), (2), and (4) to obtain the voltage gain of the circuit in Fig. P11.24 as

$$\begin{aligned} \frac{v_o}{v_i} &= -g_{m3} \beta [R_L + (r_{eN} \parallel r_{eP})] \frac{R_L}{R_L + (r_{eN} \parallel r_{eP})} \\ \Rightarrow \frac{v_o}{v_i} &= -g_{m3} \beta R_L \end{aligned}$$

where β is given by Eq. (3).

11.25 At 20°C , $I_Q = 1\text{mA} = I_S e^{(0.6/0.025)}$

$$\Rightarrow I_S \text{ (at } 20^\circ\text{C)} = 3.78 \times 10^{-11} \text{ mA}$$

$$\text{At } 70^\circ\text{C}, I_S = 3.78 \times 10^{-11} (1.14)^{50}$$

$$= 2.64 \times 10^{-8} \text{ mA}$$

$$\text{At } 70^\circ\text{C}, V_T = 25 \frac{273 + 70}{273 + 20} = 29.3 \text{ mV}$$

$$\text{Thus, } I_Q \text{ (at } 70^\circ\text{C)} = 2.64 \times 10^{-8} e^{0.6/0.0293}$$

$$= 20.7 \text{ mA}$$

$$\text{Additional current} = 20.7 - 1 = 19.7 \text{ mA}$$

$$\text{Additional power} = 2 \times 20 \times 19.7 = 788 \text{ mW}$$

$$\begin{aligned} \text{Additional temperature rise} &= 10 \times 0.788 \\ &= 7.9^\circ\text{C}, \end{aligned}$$

At 77.9°C :

$$V_T = \frac{25}{293} (273 + 77.9) = 29.9 \text{ mV}$$

$$\begin{aligned} I_Q &= 3.78 \times 10^{-11} \times (1.14)^{57.9} e^{(0.6/0.0299)} \\ &= 37.6 \text{ mA} \end{aligned}$$

etc., etc.

11.26 (a) $V_{BE} = 0.7 \text{ V}$ at 1 mA

At 0.5 mA ,

$$V_{BE} = 0.7 + 0.025 \ln \frac{0.5}{1} = 0.683 \text{ V}$$

$$\text{Thus, } R_1 = \frac{0.683}{0.5} = 1.365 \text{ k}\Omega$$

$$\text{and } R_2 = 1.365 \text{ k}\Omega$$

$$V_{BB} = 2V_{BE} = 1.365 \text{ V}$$

(b) For $I_{\text{bias}} = 2 \text{ mA}$, I_C increases to nearly 1.5 mA for which

$$V_{BE} = 0.7 + 0.025 \ln \frac{1.5}{1} = 0.710 \text{ V}$$

Note that $I_R = \frac{0.710}{1.365} = 0.52 \text{ mA}$ is very nearly equal to the assumed value of 0.50 mA , thus no further iterations are required.

$$V_{BB} = 2V_{BE} = 1.420 \text{ V}$$

(c) For $I_{\text{bias}} = 10 \text{ mA}$, assume that I_R remains constant at 0.5 mA , thus $I_{C1} = 9.5 \text{ mA}$

$$\text{and } V_{BE} = 0.7 + 0.025 \ln \frac{9.5}{1} = 0.756 \text{ V}$$

at which

$$I_R = \frac{0.755}{1.365} = 0.554 \text{ mA}$$

Thus,

$$I_{C1} = 10 - 0.554 = 9.45 \text{ mA}$$

$$\text{and } V_{BE} = 0.7 + 0.025 \ln \frac{9.45}{1} = 0.756 \text{ V}$$

$$\text{Thus, } V_{BB} = 2 \times 0.756 = 1.512 \text{ V}$$

(d) Now for $\beta = 100$,

$$I_{R1} = \frac{0.756}{1.365} = 0.554 \text{ mA}$$

$$I_{R2} = 0.554 + \frac{9.45}{101} = 0.648 \text{ mA}$$

$$I_C = 10 - 0.648 = 9.352 \text{ mA}$$

$$\text{Thus, } V_{BE} = 0.7 + 0.025 \ln \frac{9.352}{1} = 0.756 \text{ V}$$

$$V_{BB} = 0.756 + I_{R2} R_2$$

$$= 0.756 + 0.648 \times 1.365$$

$$= 1.641 \text{ V}$$

This figure belongs to Problem 11.27.

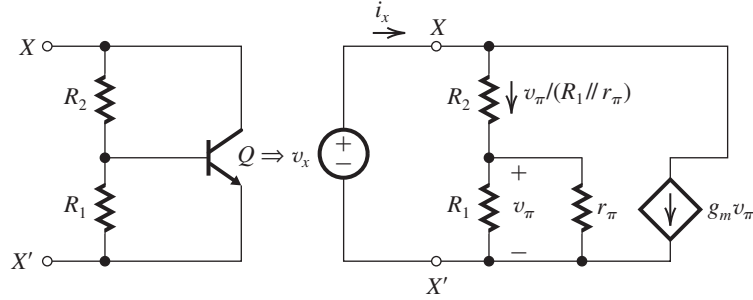


Figure 1

11.27 Figure 1 shows the V_{BE} multiplier together with its small-signal equivalent circuit prepared for determining the incremental terminal resistance r ,

$$r \equiv \frac{v_x}{i_x}$$

Now,

$$i_x = g_m v_\pi + \frac{v_\pi}{R_1 \parallel r_\pi} \quad (1)$$

$$v_x = v_\pi + \frac{v_\pi}{R_1 \parallel r_\pi} R_2 \quad (2)$$

Dividing (2) by (1) gives

$$\begin{aligned} r &= \frac{1 + R_2/(R_1 \parallel r_\pi)}{g_m + \frac{1}{R_1 \parallel r_\pi}} \\ &= \frac{R_2 + (R_1 \parallel r_\pi)}{1 + g_m(R_1 \parallel r_\pi)} \end{aligned}$$

For $R_1 = R_2 = 1.2 \text{ k}\Omega$, $I_C = 1 \text{ mA}$, and $\beta = 100$, we have


$$g_m = 40 \text{ mA/V}$$

$$r_\pi = \frac{100}{40} = 2.5 \text{ k}\Omega$$

Thus,

$$r = \frac{1.2 + (1.2 \parallel 2.5)}{1 + 40(1.2 \parallel 2.5)} = 60.2 \text{ }\Omega$$

11.28 (a) For $R_L = \infty$:

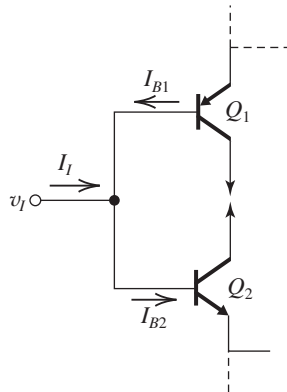

At $v_I = 0 \text{ V}$, we have

$$I_{B1} = I_{B2} = \frac{2.87}{200}$$

$$I_I = I_{B2} - I_{B1} = 0$$

At $v_I = +10 \text{ V}$, we have

$$I_{B1} = \frac{0.88}{200} \text{ mA} = 4.4 \text{ }\mu\text{A}$$

$$I_{B2} = \frac{4.87}{200} \text{ mA} = 24.4 \text{ }\mu\text{A}$$

$$I_I = I_{B2} - I_{B1} = 20 \text{ }\mu\text{A}$$

At $v_I = -10 \text{ V}$, we have

$$I_{B1} = \frac{4.87}{200} \text{ mA} = 24.4 \text{ }\mu\text{A}$$

$$I_{B2} = \frac{0.88}{200} \text{ mA} = 4.4 \text{ }\mu\text{A}$$

$$I_I = I_{B2} - I_{B1} = -20 \text{ }\mu\text{A}$$

(b) For $R_L = 100 \text{ }\Omega$:

At $v_I = 0 \text{ V}$, we have $I_I = 0$

At $v_I = +10 \text{ V}$, we have

$$I_{B1} = \frac{0.38}{200} = 1.9 \text{ }\mu\text{A}$$

$$I_{B2} = \frac{4.87}{200} = 24.4 \text{ }\mu\text{A}$$

$$I_I = I_{B2} - I_{B1} = 22.5 \text{ }\mu\text{A}$$

At $v_I = -10 \text{ V}$, we have $I_I = -22.5 \text{ }\mu\text{A}$

11.29 Circuit operating near $v_I = 0$ and is fed with a signal source having zero resistance.

The resistance looking as shown by the arrow X is

$$= R_1 \parallel r_{e1}$$


This resistance is reflected from base to the emitter of Q_3 as $(R_1 \parallel r_{e1})/(\beta_3 + 1)$.

The resistance seen by arrow Y , from the upper half of the circuit


$$= R_3 + r_{e3} + (R_1 \parallel r_{e1})/(\beta_3 + 1)$$

A similar resistance is seen by the arrow Z and both of these resistances (seen by arrows Y and arrow Z) are in parallel, therefore
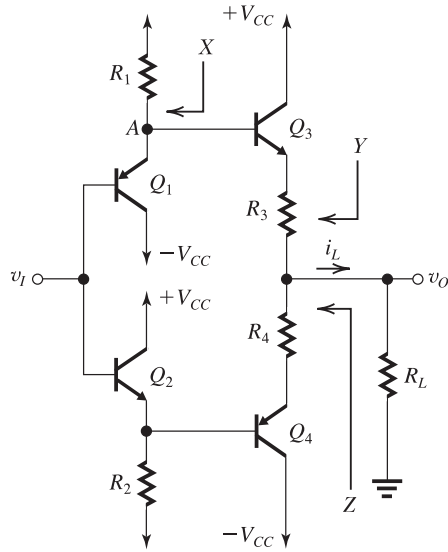
$$R_{\text{out}} = \frac{1}{2} [R_3 + r_{e3} + (R_1 \parallel r_{e1}) / (\beta_3 + 1)]$$



11.30

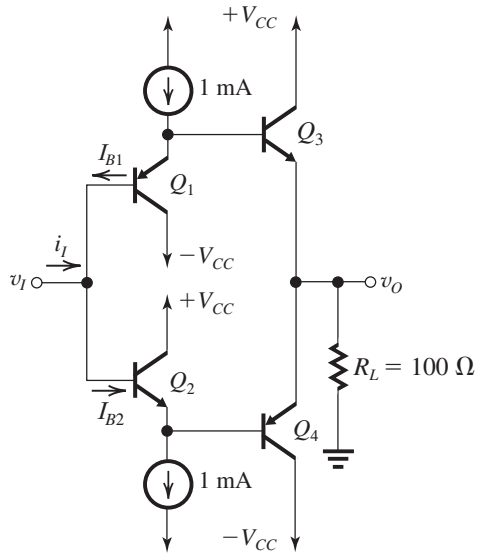

(a) $v_i = 0$ and transistors have $\beta = 100$.

$$v_o = 0 \text{ V}$$

$$I_Q = I_{E3} = I_{E4} = I_{E1} = I_{E2} \simeq 1 \text{ mA}$$

More precisely, $\frac{I_{E3}}{\beta + 1} + I_{E1} = 1 \text{ mA}$

thus,

$$I_Q \left(\frac{1}{(\beta + 1)} + 1 \right) = 1$$

$$\Rightarrow I_Q \simeq 0.99 \text{ mA}$$

Input bias current is zero because $I_{B1} = I_{B2}$.


(b) From the equivalent half circuit, we have

$$2R_{\text{in}} = (\beta_1 + 1) [r_{e1} + (\beta_3 + 1) (r_{e3} + 2R_L)]$$

$$r_{e1} = r_{e3} = \frac{V_T}{I_E} = \frac{25}{1} = 25 \Omega$$

$$2R_{\text{in}} = (100 + 1)[25 + (100 + 1)(25 + 2 \times 100)]$$
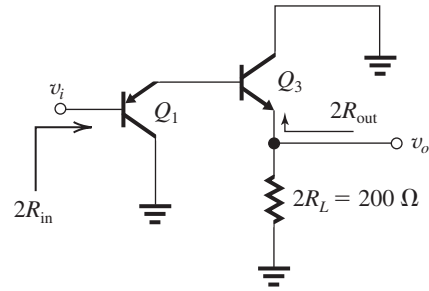
$$\Rightarrow R_{\text{in}} = 1.15 \text{ M}\Omega$$



$$A_v = \frac{v_o}{v_i} = \frac{2R_L}{2R_L + r_{e3} + \frac{r_{e1}}{\beta_3 + 1}}$$

$$= \frac{200}{200 + 25 + \frac{25}{101}}$$

$$\simeq 0.89 \text{ V/V}$$

$$2R_{\text{out}} = r_{e3} + \frac{r_{e1}}{\beta + 1}$$

$$= 25 + \frac{25}{101}$$

$$R_{\text{out}} = 12.6 \Omega$$

11.31 See figure on the next page.


At $v_i = 5 \text{ V}$, we have

$$V_{E1} = +5.7 \text{ V}$$

$$I_{R1} = \frac{V_{CC} - V_{E1}}{R_1} = \frac{10 - 5.7}{R_1} = \frac{4.3}{R_1}$$

To allow for $I_{B3} = 10 \text{ mA}$ if needed while reducing I_{E1} by no more than half, then I_{R1} must be $2 \times 10 = 20 \text{ mA}$. Thus,
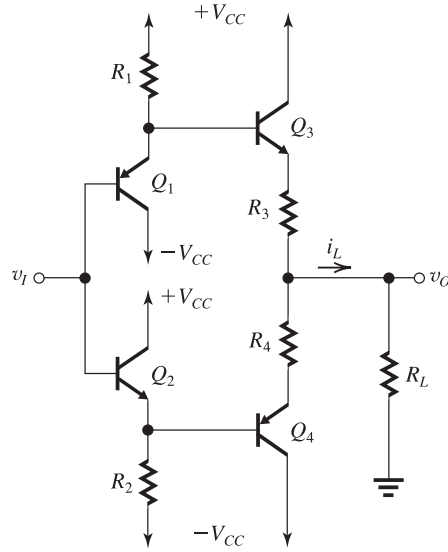
$$R_1 = \frac{V_{R1}}{I_{R1}} = \frac{4.3}{20} = 0.215 \text{ k}\Omega = 215 \Omega$$



Similarly,

$$R_2 = 0.215 \text{ k}\Omega = 215 \Omega$$

Next, we determine the values of R_3 and R_4 : At $v_I = 0$, assume $V_{BE1} = 0.7$. Then

$$V_{E1} = 0.7 \text{ V}$$

$$I_{R1} = \frac{10 - 0.7}{0.215} = 43.3 \text{ mA}$$

$$V_{BE1} = 0.7 + 0.025 \times \ln\left(\frac{43.3}{10}\right)$$

$$= 0.737 \text{ V}$$

$$V_{E1} = 0.737 \text{ V}$$

Meanwhile Q_3 will be conducting $I_Q = 40 \text{ mA}$.

Since $I_{S3} = 3I_{S1}$ then Q_3 has $V_{BE} = 0.7 \text{ V}$ at $I_C = 30 \text{ mA}$. At 40 mA ,

$$V_{BE3} = 0.7 + 0.025 \times \ln\left(\frac{40}{30}\right)$$

$$= 0.707 \text{ V}$$

For $v_O = 0$,

$$V_{E1} - V_{BE3} - I_{E3}R_3 = 0$$

$$0.737 - 0.707 - 40R_3 = 0$$

$$\Rightarrow R_3 = 0.75 \Omega$$

Similarly,

$$R_4 = 0.75 \Omega$$

$$R_{\text{out}} = \frac{1}{2} \left[R_3 + r_{e3} + \frac{R_1 \parallel r_{e1}}{\beta_3 + 1} \right]$$

where

$$r_{e3} = \frac{25 \text{ mV}}{40 \text{ mA}} = 0.625 \Omega$$

$$r_{e1} = \frac{25 \text{ mV}}{20 \text{ mA}} = 1.25 \Omega$$

$$R_{\text{out}} = \frac{1}{2} \left[0.75 + 0.625 + \frac{215 \parallel 1.25}{51} \right]$$

$$R_{\text{out}} = 0.7 \Omega$$

Next, consider the situation when

$$v_I = +1 \text{ V and } R_L = 2 \Omega$$

Let $v_O \simeq 1 \text{ V}$, then

$$i_L = \frac{1 \text{ V}}{2 \Omega} = 0.5 \text{ A} = 500 \text{ mA}$$

Now if we assume that $i_{E4} \simeq 0$, then

$$i_{E3} = i_L = 500 \text{ mA}$$

$$V_{BE3} = 0.7 + 0.025 \ln \frac{500}{30}$$

$$= 0.770 \text{ V}$$

$$i_{B3} = \frac{500}{51} \simeq 10 \text{ mA}$$

Assuming that $V_{BE1} \simeq 0.7 \text{ V}$, then

$$v_{E1} = 1 + 0.7 = 1.7 \text{ V}$$

$$i_{R1} = \frac{10 - 1.7}{0.215} = 38.6 \text{ mA}$$

$$i_{E1} = i_{R1} - i_{B2} = 38.6 - 10 = 28.6 \text{ mA}$$

$$V_{BE1} = 0.7 + 0.025 \ln \frac{28.6}{10}$$

$$= 0.726 \text{ V}$$

$$V_{E1} = 1.726 \text{ V}$$

$$i_L = \frac{V_{E1} - V_{BE3}}{R_3 + R_L}$$

$$= \frac{1.726 - 0.770}{0.75 + 2}$$

$$= 0.348 \text{ A}$$

$$v_O = i_L R_L$$

$$= 0.348 \times 2 = 0.695 \text{ V}$$

Let's check that i_{E4} is zero. The voltage at the base of Q_4 is

$$V_{B4} = 1 - V_{BE2}$$

$$\simeq 1 - 0.74 = 0.26 \text{ V}$$

The voltage across R_4 and V_{EB4} is

$$= v_O - 0.26 = 0.695 - 0.26 = 0.435 \text{ V}$$



which is sufficiently small to keep Q_4 cutoff, verifying our assumption that $i_{E4} \simeq 0$.

Let's now do more iterations to refine our estimate of v_O :

$$i_L = 0.35 \text{ A}$$

$$\begin{aligned}
 i_{B3} &= \frac{0.35}{51} \simeq 7 \text{ mA} \\
 i_{E1} &= \frac{10 - 1 - 0.726}{0.215} - 7 = 31.5 \text{ mA} \\
 V_{EB1} &= 0.7 + 0.025 \ln\left(\frac{31.5}{10}\right) \\
 &= 0.729 \text{ V} \\
 V_{E1} &= 1 + 0.729 = 1.729 \text{ V} \\
 i_{E3} &= i_L = 350 \text{ mA} \\
 V_{BE3} &= 0.7 + 0.025 \ln\left(\frac{350}{30}\right) \\
 &= 0.761 \text{ V} \\
 i_L &= \frac{V_{E1} - V_{BE3}}{R_3 + R_2} \\
 &= \frac{1.729 - 0.761}{0.75 + 2} = 0.352 \text{ A} \\
 v_O &= i_L R_L \\
 &= 0.352 \times 2 = 0.704 \text{ V}
 \end{aligned}$$

11.32

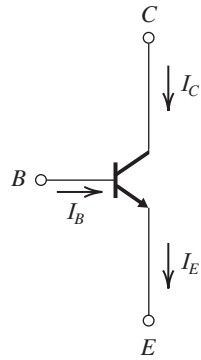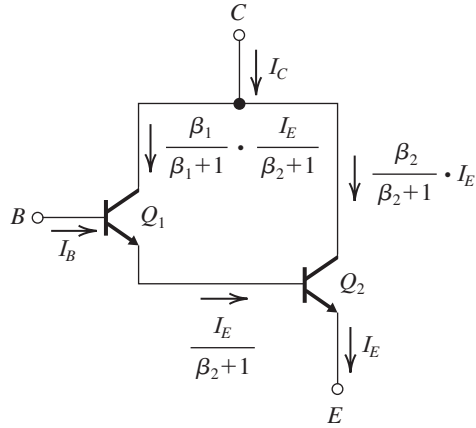

(a) For the composite transistor, we have

$$\beta = \frac{I_C}{I_B}$$

Refer to the diagram.

$$I_B = \frac{1}{\beta_1 + 1} \frac{I_E}{\beta_2 + 1}$$

$$I_C = \frac{\beta_1}{(\beta_1 + 1)(\beta_2 + 1)} I_E + \frac{\beta_2}{(\beta_2 + 1)} I_E$$

$$= \frac{\beta_1 + \beta_2(\beta_1 + 1)}{(\beta_1 + 1)(\beta_2 + 1)} \cdot I_E$$

For the composite transistor, β is given by

$$\beta = \frac{I_C}{I_B} = \frac{\frac{\beta_1 + \beta_2(\beta_1 + 1)}{(\beta_1 + 1)(\beta_2 + 1)} \times I_E}{\frac{1}{(\beta_1 + 1)(\beta_2 + 1)} \cdot I_E}$$

$$= \beta_1 + \beta_2(\beta_1 + 1)$$

$$\simeq \beta_1 \beta_2 \text{ since } \beta_1 \gg 1 \text{ and } \beta_2 \gg 1$$

(b) Refer to the diagram.

Operating current of Q_2

$$= I_{C2} = \frac{\beta_2}{\beta_2 + 1} I_E = \frac{\beta_2}{\beta_2 + 1} \times \frac{\beta + 1}{\beta} I_C$$

where $\beta = \beta_1 \beta_2$

$$\simeq I_C \text{ since } \beta_2 \gg 1 \text{ and } \beta \gg 1$$

Operating current of Q_1

$$= I_{C1} = \frac{\beta_1}{(\beta_1 + 1)(\beta_2 + 1)} I_E$$

$$= \frac{\beta_1}{(\beta_1 + 1)(\beta_2 + 1)} \cdot \frac{\beta + 1}{\beta} I_C$$

$$\simeq \frac{I_C}{\beta_2} \text{ since } \beta \gg 1, \beta_2 \gg 1 \text{ and } \beta_1 \gg 1.$$

(c) Again refer to the diagram and part (b).

$$V_{BE} = V_{BE2} + V_{BE1} = V_T \ln\left(\frac{I_{C2}}{I_S}\right) + V_T \ln\left(\frac{I_{C1}}{I_S}\right)$$

From part (b), $I_{C2} \simeq I_C$ and $I_{C1} \simeq \frac{I_C}{\beta_2}$

$$\therefore V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) + V_T \ln\left(\frac{1}{\beta_2} \frac{I_C}{I_S}\right)$$

$$= V_T \ln\left(\frac{I_C}{I_S}\right) + V_T \ln\left(\frac{I_C}{I_S}\right) + V_T \ln\left(\frac{1}{\beta_2}\right)$$

$$V_{BE} = 2V_T \ln\left(\frac{I_C}{I_S}\right) - V_T \ln(\beta_2)$$

$$(d) r_{\pi \text{eq}} = (\beta_1 + 1)[r_{\pi 1} + (\beta_2 + 1)r_{\pi 2}]$$

$$\text{Here, } r_{e2} = \frac{V_T}{I_{E2}} \simeq \frac{V_T}{I_{C2}} \simeq \frac{V_T}{I_C}$$

$$r_{e1} = \frac{V_T}{I_{E2}} \simeq \frac{V_T}{I_{C1}} \simeq \frac{V_T}{I_C/\beta_2} = \beta_2 r_{e2}$$

$$r_{\pi \text{eq}} \simeq (\beta_1 + 1) [\beta_2 r_{e2} + \beta_2 r_{e2}]$$

$$= 2(\beta_1 + 1) \beta_2 r_{e2}$$

$$\simeq 2\beta_1 \beta_2 r_{e2}$$

$$= 2\beta_1 \beta_2 \frac{V_T}{I_C}$$

(e) To find g_{meq} , apply a signal v_{be} and find the corresponding current i_c :

$$i_c = i_{c1} + i_{c2} = g_{m1}v_{be1} + g_{m2}v_{be2}$$

$$= g_{m1}v_{be} \frac{r_{e1}}{r_{e1} + (\beta_2 + 1)r_{e2}}$$

$$+ g_{m2} \frac{(\beta_2 + 1)r_{e2}}{r_{e1} + (\beta_2 + 1)r_{e2}} \cdot v_{be}$$

$$\simeq v_{be} \frac{1}{\beta_2 r_{e2} + (\beta_2 + 1)r_{e2}}$$

$$+ \frac{\beta_2}{\beta_2 r_{e2} + (\beta_2 + 1)r_{e2}} \cdot v_{be}$$

$$\because g_{m1} \simeq 1,$$

$$i_c \simeq v_{be} \frac{1}{2\beta_2 r_{e2}} + v_{be} \frac{\beta_2}{2\beta_2 r_{e2}}$$

$$\simeq v_{be} \frac{(\beta_2 + 1)}{2\beta_2 r_{e2}}$$

$$\simeq v_{be} \frac{1}{2r_{e2}}$$

$$g_{\text{meq}} = \frac{i_c}{v_{be}} = \frac{1}{2r_{e2}}$$

$$= \frac{1}{2} \frac{I_C}{V_T}$$

11.33 (a)

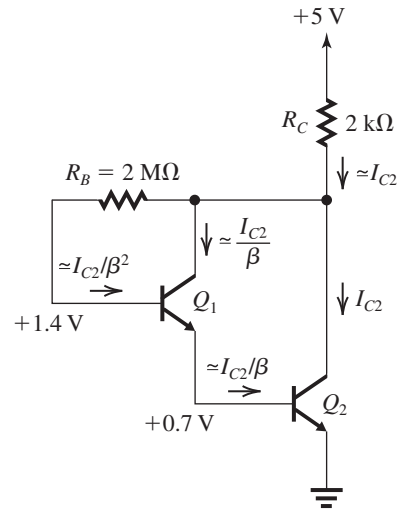


Figure 1

From Figure 1 we can write

$$5 = I_{C2}R_C + \frac{I_{C2}}{\beta^2}R_B + 1.4$$

$$\Rightarrow I_{C2} = \frac{5 - 1.4}{R_C + \frac{R_B}{\beta^2}}$$

$$= \frac{3.6}{2 + \frac{2000}{10,000}} = 1.64 \text{ mA}$$

$$I_{C1} \simeq \frac{I_{C2}}{\beta} = \frac{1.64}{100} = 0.0164 \text{ mA}$$

(b)

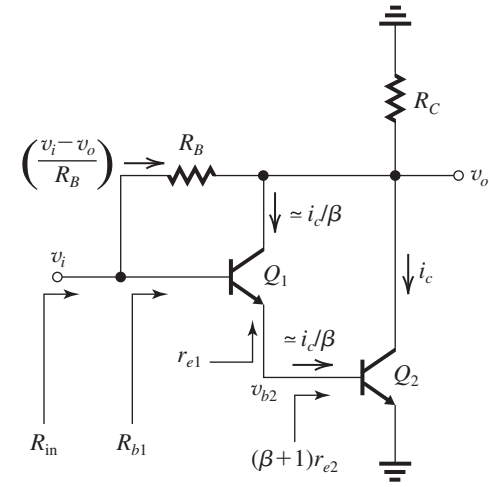


Figure 2

$$v_{b2} = v_i \frac{(\beta + 1)r_{e2}}{(\beta + 1)r_{e2} + r_{e1}}$$

where

$$r_{e2} = \frac{V_T}{I_{E2}} \simeq \frac{V_T}{I_{C2}} = \frac{25 \text{ mV}}{1.64 \text{ mA}} = 15.2 \Omega$$

$$r_{e1} = \frac{V_T}{I_{E1}} \simeq \frac{V_T}{I_{C1}} = \frac{25 \text{ mV}}{0.0164 \text{ mA}} = 1.52 \Omega$$

$$v_{b2} = v_i \frac{101 \times 15.2}{101 \times 15.2 + 1520} = 0.5v_i$$

$$i_c = g_{m2}v_{b2}$$

$$= g_{m2} \times 0.5v_i$$

where

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{1.64}{0.025} = 65.6 \text{ mA/V}$$

$$i_c = 65.6 \times 0.5v_i = 32.8v_i$$

Writing a node equation at the output provides

$$\frac{v_o}{R_C} + i_c + \frac{i_c}{\beta} + \frac{v_o - v_i}{R_B} = 0$$

Substituting $i_c = 32.8v_i$, we obtain

$$v_o \left(\frac{1}{R_C} + \frac{1}{R_B} \right) = -v_i \left[\left(1 + \frac{1}{\beta} \right) 32.8 - \frac{1}{R_B} \right]$$

$$A_v \equiv \frac{v_o}{v_i} = - \frac{\left(1 + \frac{1}{\beta} \right) 32.8 - \frac{1}{R_B}}{\frac{1}{R_C} + \frac{1}{R_B}}$$

$$= - \frac{1.01 \times 32.8 - (1/2000)}{\frac{1}{2} + \frac{1}{2000}}$$

$$= -66.2 \text{ V/V}$$

(c) $R_{b1} = (\beta + 1)[r_{e1} + (\beta + 1)r_{e2}]$

$$= 101[1.52 + 101 \times 0.0152]$$

$$= 318.7 \text{ k}\Omega$$

The component of R_{in} arising from R_B can be found as

$$R_{i2} = \frac{v_i}{(v_i - v_o)/R_B}$$


$$= \frac{R_B}{1 - (v_o/v_i)} = \frac{2000}{1 - (-66.2)} = 29.8 \text{ k}\Omega$$

Thus

$$R_{in} = R_{ib} \parallel R_{i2}$$

$$= 318.7 \parallel 29.8 = 27.2 \text{ k}\Omega$$

11.34 (a) DC Analysis:

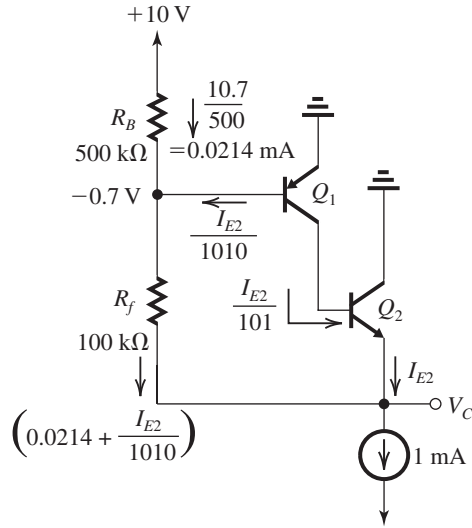

$$1 \text{ mA} = 0.0214 + \frac{I_{E2}}{1010} + I_{E2}$$

$$\Rightarrow I_{E2} = 0.978 \text{ mA}$$

$$I_{C2} = 0.99 \times 0.978 = 0.97 \text{ mA}$$

$$I_{C1} = \frac{0.978}{101} = 9.7 \mu\text{A}$$

$$V_C = -0.7 - 100 \left(0.0214 + \frac{0.978}{1010} \right)$$

$$= -2.94 \text{ V}$$

(b) Small-signal parameters:

$$g_{m1} = \frac{9.7 \times 10^{-6}}{25 \times 10^{-3}} = 0.388 \text{ mA/V}$$

$$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = 25.77 \text{ k}\Omega$$

$$r_{o1} = \frac{|V_A|}{I_{C1}} = \frac{100}{9.7 \mu\text{A}} = 10.31 \text{ M}\Omega$$

$$g_{m2} = \frac{0.97 \times 10^{-3}}{25 \times 10^{-3}} = 38.8 \text{ mA/V}$$

$$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = 2.58 \text{ k}\Omega$$

$$r_{o2} = |V_A| / I_{C2} = 103.1 \text{ k}\Omega$$

Node equation at b_2 :

$$g_{m1}v_{\pi 1} + \frac{v_{b2}}{r_{o1}} + \frac{v_{\pi 2}}{r_{\pi 2}} = 0$$

But $v_{b2} = v_o + v_{\pi 2}$, then

$$g_{m1}v_{\pi 1} + \frac{v_o + v_{\pi 2}}{r_{o1}} + \frac{v_{\pi 2}}{r_{\pi 2}} = 0$$

$$\Rightarrow v_{\pi 2} \left(\frac{1}{r_{\pi 2}} + \frac{1}{r_{o1}} \right) = - \left(\frac{v_o}{r_{o1}} + g_{m1}v_{\pi 1} \right)$$

$$\text{or, } v_{\pi 2} = - \frac{\frac{v_o}{r_{o1}} + g_{m1}v_{\pi 1}}{\frac{1}{r_{\pi 2}} + \frac{1}{r_{o1}}}$$

Node equation at output:

$$\frac{v_o}{r_{o2}} + \frac{v_o - v_{\pi 1}}{R_f} = g_{m2}v_{\pi 2} + \frac{1}{r_{\pi 2}}v_{\pi 2}$$

$$= \left(g_{m2} + \frac{1}{r_{\pi 2}} \right) v_{\pi 2}$$


$$= - \frac{\left(g_{m2} + \frac{1}{r_{\pi 2}} \right) \left[\frac{v_o}{r_{o1}} + g_{m1}v_{\pi 1} \right]}{\frac{1}{r_{\pi 2}} + \frac{1}{r_{o1}}}$$

Substituting $v_{\pi 1} = v_i$ and collecting terms, we obtain

$$v_o \left[\frac{1}{r_{o2}} + \frac{1}{R_f} + \frac{\left(g_{m2} + \frac{1}{r_{\pi 2}} \right)}{r_{o1} \left(\frac{1}{r_{\pi 2}} + \frac{1}{r_{o1}} \right)} \right]$$

$$= -v_i \left[\frac{g_{m1} \left(g_{m2} + \frac{1}{r_{\pi 2}} \right)}{\frac{1}{r_{\pi 2}} + \frac{1}{r_{o2}}} - \frac{1}{R_f} \right]$$

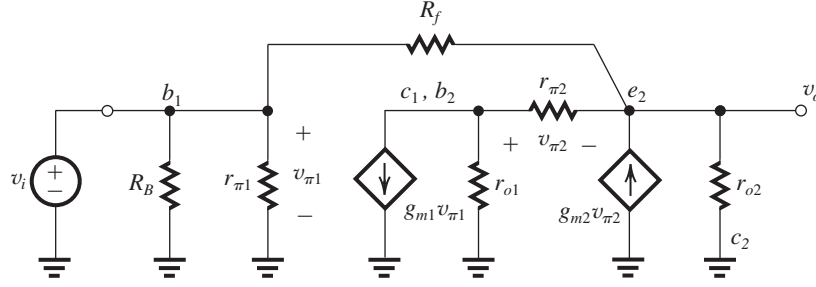This figure belongs to Exercise 11.34, part (b).



$$\frac{v_o}{v_i} = - \frac{\frac{g_{m1} \left(g_{m2} + \frac{1}{r_{\pi 2}} \right)}{\frac{1}{r_{\pi 2}} + \frac{1}{r_{o2}}} - \frac{1}{R_f}}{\frac{1}{r_{o2}} + \frac{1}{R_f} + \frac{\left(g_{m2} + \frac{1}{r_{\pi 2}} \right)}{r_{o1} \left(\frac{1}{r_{\pi 2}} + \frac{1}{r_{o1}} \right)}}$$

Since $r_{\pi 2} \ll r_{o1}$, we have

$$\frac{v_o}{v_i} \simeq - \frac{g_{m1} (g_{m2} r_{\pi 2} + 1) - \frac{1}{R_f}}{\frac{1}{r_{o2}} + \frac{1}{R_f} + \frac{1}{r_{o1}} (g_{m2} r_{\pi 2} + 1)}$$

$$= - \frac{g_{m1} (\beta_2 + 1) - \frac{1}{R_f}}{\left(\frac{1}{r_{o2}} + \frac{1}{R_f} \right) + \frac{1}{r_{o1}} (\beta_2 + 1)}$$

Since $\frac{1}{R_f} \ll g_{m1} (\beta_2 + 1)$, we have

$$\frac{v_o}{v_i} \simeq - \frac{g_{m1} (\beta_2 + 1)}{\left(\frac{1}{r_{o2}} + \frac{1}{R_f} \right) + \frac{1}{r_{o1}} (\beta_2 + 1)}$$

Substituting $\beta_2 = \beta_N$ and noting that $\beta_N \gg 1$, we obtain

$$\frac{v_o}{v_i} \simeq -g_{m1} \frac{1}{\frac{1}{\beta_N} \left(\frac{1}{r_{o2}} + \frac{1}{R_f} \right) + \frac{1}{r_{o1}}} = -g_{m1} [r_{o1} \parallel \beta_N (r_{o2} \parallel R_f)] \quad \text{Q.E.D.}$$

(c)

$$\frac{v_o}{v_i} = -0.388 [10.31 \times 10^3 \parallel 100 (103.1 \parallel 100)]$$

$$= -1320 \text{ V/V}$$

$$R_{in} = R_B \parallel r_{\pi 1} \left[\frac{v_i}{\left(\frac{v_i - v_o}{R_f} \right)} \right]$$

$$= 500 \parallel 25.77 \left[\frac{R_f}{1 - \frac{v_o}{v_i}} \right]$$

$$= 500 \parallel 25.77 \parallel \frac{100}{1 + 1320}$$

$$= 500 \parallel 25.77 \parallel 0.0757$$


$$= 75.5 \Omega$$

11.35 First consider the situation in the quiescent state and find V_{BB} .

$$I_{Q2} = I_{Q4} = 2 \text{ mA}$$

$$V_{BE2} = V_{BE4} = 0.7 + 0.025 \ln \left(\frac{2}{10} \right)$$

$$= 0.660 \text{ V}$$

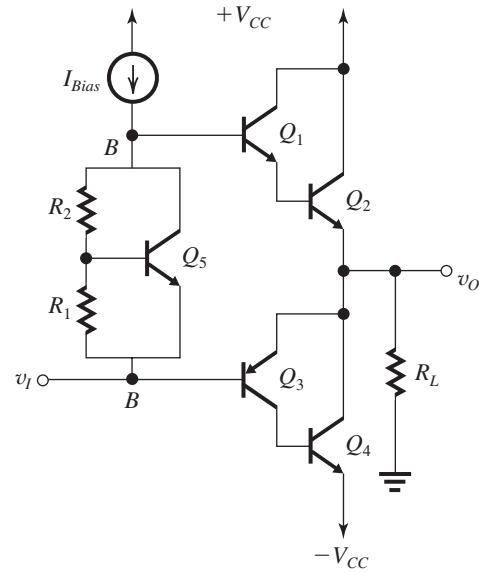

For Q_1 and Q_3 , we have

$$I_C = \frac{2}{\beta} = \frac{2}{100} = 0.02 \text{ mA}$$

$$V_{BE1} = |V_{BE3}| = 0.7 + 0.025 \ln \left(\frac{0.02}{1} \right)$$

$$= 0.602 \text{ V}$$

$$I_{B1} = \frac{0.02 \text{ mA}}{\beta} = \frac{0.02}{100} = 0.2 \mu\text{A}$$

$$I_{\text{Bias}} = 100 \times \text{Base current in } B_1$$

$$= 100 \times 0.2 = 20 \mu\text{A}$$

$$I_{R1,R2} = \frac{1}{10} \times 20 \mu\text{A} = 2 \mu\text{A}$$

$$\text{and } I_{C5} = 20 - 2 = 18 \mu\text{A}$$

$$V_{BE5} = 0.7 + 0.025 \ln\left(\frac{18 \mu}{1 \text{ m}}\right) \simeq 0.600 \text{ V}$$

$$V_{BB} = V_{BE1} + V_{BE2} + |V_{BE3}|$$

$$= 0.602 + 0.660 + 0.602$$

$$= 1.864 \text{ V}$$

$$R_1 + R_2 = \frac{1.864}{2 \mu\text{A}} = 932 \text{ k}\Omega$$

$$R_1 = \frac{0.600}{2 \mu\text{A}} = 300 \text{ k}\Omega$$

$$R_2 = 932 - 300 = 632 \text{ k}\Omega$$

Now find v_I for $v_O = 10 \text{ V}$ and $R_L = 1 \text{ k}\Omega$.

Q_2 is conducting most of the current and Q_4 conducting a negligible current.

$$\therefore I_{C2} \simeq I_L = \frac{10 \text{ V}}{1 \text{ k}\Omega} = 10 \text{ mA}$$

\therefore The current through each of Q_1 and Q_2 increases by a factor of $\frac{10}{2} = 5$

$$\text{Thus } V_{BE2} = 0.66 + 0.025 \ln 5 = 0.700 \text{ V}$$

$$V_{BE1} = 0.602 + 0.025 \ln 5 = 0.642 \text{ V}$$

$$\text{and } I_{B1} = 5 \times 0.2 \mu\text{A} = 1 \mu\text{A}$$

\therefore The current through the multiplier is $I_{\text{Bias}} - 1 = 20 - 1 = 19 \mu\text{A}$. Assuming most of the decrease occurs in I_{C5} , we obtain

$$\therefore I_{C5} = 18 - 1 = 17 \mu\text{A}$$

$$V_{BE5} = 0.7 + 0.025 \ln\left(\frac{17 \mu\text{A}}{1 \mu\text{A}}\right) = 0.598 \text{ V}$$

$\therefore V_{BB1}$, the voltage across the multiplier is

$$V_{BB} = 0.598 \times \frac{932}{300} = 1.858 \text{ V}$$

It follows that V_{EB3} becomes

$$V_{EB3} = 1.858 - 0.700 - 0.642 = 0.516 \text{ V}$$

i.e. V_{EB3} has decreased by $0.600 - 0.516 = 0.084 \text{ V}$

Correspondingly, I_{C3} will decrease by a factor of $e^{\frac{-0.084}{0.025}} = 0.035$.

$$\therefore I_{C4} \text{ becomes } 0.035 \times 2 = 0.07 \text{ mA}$$

This value is close to zero, no iteration required.

$$\therefore v_I = 10 + 0.7 + 0.642 - 1.858$$

$$v_I = 9.484 \text{ V}$$

Now find v_I for $v_O = -10 \text{ V}$ and $R_L = 1 \text{ k}\Omega$.

$$i_L = \frac{-10}{1 \text{ k}\Omega} = -10 \text{ mA}$$

Assume that current through Q_2 is almost zero.

$$\therefore I_{C4} \simeq 10 \text{ mA}$$

The current through Q_4 increases by a factor of 5 (relative to the quiescent value).

\therefore The current through Q_3 must also increase by the same factor. Thus

$$|V_{BE3}| = 0.602 + 0.025 \ln 5 = 0.642 \text{ V}$$

$|V_{BE3}|$ has increased by $0.642 - 0.602 = 0.04 \text{ V}$. Since Q_1 and Q_2 are almost cut off, all of the I_{Bias} now flows through the V_{BE} multiplier. That is an increase of 0.2μ . Assuming that most of the increase occurs in I_{C5} , V_{BE5} becomes

$$V_{BE5} = 0.7 + 0.025 \ln\left(\frac{18.2 \mu\text{A}}{1 \text{ mA}}\right) \simeq 0.600 \text{ V}$$

The voltage V_{BE5} remains almost constant, and the voltage across the multiplier will remain almost constant. Thus the increase in $|V_{EB3}|$ will result in an equal decrease in $|V_{BE1}| + |V_{BE2}|$, i.e.

$$V_{BE1} + V_{BE2} = 0.660 + 0.602 - 0.04$$

The current through each of Q_1 and Q_2 decreases by the same factor, let it be m ; then

$$0.025 \ln m + 0.025 \ln m = -0.04 \text{ V}$$

$$\Rightarrow m = 0.45$$

$$\text{Thus } I_{C2} = 0.45 \times 2 = 0.9 \text{ mA}$$

Now do iteration

$$I_{C4} = 10.9$$

$$I_{C4} \text{ has increased by a factor of } \frac{10.9}{2} = 5.45$$

$$\therefore |V_{BE3}| = 0.602 + 0.025 \ln 5.45$$

$$= 0.644$$

$$v_I = v_O + |V_{EB3}|$$

$$v_I \cong -10.644 \text{ V}$$

11.36 (a) Refer to the circuit in Fig. P11.36.

While D_1 is conducting, the voltage at the emitter of Q_3 is $(V_{CC1} - V_D)$. For Q_3 to turn on, the voltage at its base must be at least equal to $V_{CC1} = 35 \text{ V}$. This will occur when v_I reaches the value

$$v_I = V_{CC1} - V_{Z1} - V_{BB}$$

$$= 35 - 3.3 - 1.2 = 30.5 \text{ V}$$

This is the positive threshold at which Q_3 is turned on.

(b) The power dissipated in the circuit is given by Eq. (11.19):

$$P_D = \frac{2}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} - \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

For 95% of the time, $\hat{V}_o = 30$ V, $V_{CC} = 35$ V,

$$P_D = \frac{1}{R_L} \left[\frac{2}{\pi} \times 30 \times 35 - \frac{1}{2} \times 30^2 \right] \\ = \frac{218.5}{R_L}$$

For 5% of the time, $\hat{V}_o = 65$ V, $V_{CC} = 70$ V,

$$P_D = \frac{1}{R_L} \left[\frac{2}{\pi} \times 65 \times 70 - \frac{1}{2} \times 65^2 \right] \\ = \frac{784.1}{R_L}$$

Thus, the total power dissipation is

$$P_D = \frac{218.5}{R_L} \times 0.95 + \frac{784.1}{R_L} \times 0.05 \\ = \frac{246.8}{R_L} \quad (1)$$

This should be compared to the power dissipation of a class AB output stage operated from ± 70 V. Here,

P_D (for 95% of the time)

$$= \frac{1}{R_L} \left[\frac{2}{\pi} \times 30 \times 70 - \frac{1}{2} \times 30^2 \right] \\ = \frac{886.9}{R_L}$$

P_D (for 5% of the time)

$$= \frac{1}{R_L} \left[\frac{2}{\pi} \times 65 \times 70 - \frac{1}{2} \times 65^2 \right] \\ = \frac{784.1}{R_L}$$

$$\text{Total dissipation} = \frac{886.9}{R_L} \times 0.95 + \frac{784.1}{R_L} \times 0.05 \\ = \frac{881.8}{R_L} \quad (2)$$

The results in (1) and (2) indicate that using the Class G circuit in Fig. P11.36 results in a reduction in P_D by a factor of 3.6!

11.37 Refer to Exercise 11.11 and Fig. 11.21.

$$2 \times 10^{-3} = 10^{-14} e^{V_{BE}/V_T}$$

$$\Rightarrow V_{BE} = 0.650 \text{ V}$$

$$R_{E1} = \frac{0.650 \text{ V}}{100 \text{ mA}} = 6.5 \text{ } \Omega$$

From a normal peak output current of 75 mA, we get

$$V_{BE} = 6.5 \times 75 = 487.5 \text{ mV}$$

$$I_{C5} = 10^{-14} \times e^{487.5/25} = 2.9 \text{ } \mu\text{A}$$

11.38 Refer to Fig. P11.38.

$$2 \times 10^{-3} = 10^{-14} e^{V_{EB5}/V_T}$$

$$V_{EB5} = 0.025 \ln(2 \times 10^{11})$$

$$= 0.650 \text{ V}$$

$$R = \frac{0.650 \text{ V}}{100 \text{ mA}} = 6.5 \text{ } \Omega$$

For a normal peak output current of 75 mA, we have

$$V_{EB5} = 6.5 \times 75 = 487.5 \text{ mV}$$

$$I_{C5} = 10^{-14} \times e^{487.5/25}$$

$$= 2.9 \text{ } \mu\text{A}$$

11.39 Refer to Fig. 11.22.

At 125°C, we have

$$V_Z = 6.8 + (125 - 25) \times 2 = 7.0 \text{ V}$$

Since $I_{C2} = 200 \text{ } \mu\text{A}$, then

$$V_{BE1} = 0.7 + 0.025 \ln\left(\frac{200}{100}\right) - 2 \text{ mV} \times 100 \\ = 0.517 \text{ V}$$

Similarly, for Q_2 to conduct 200 μA , we need

$$V_{BE2} = 0.517 \text{ V}$$

Now, the voltage across R_1 and R_2 is

$$V_{(R1+R2)} = V_Z - V_{BE1} \\ = 7 - 0.517 = 6.483 \text{ V}$$

The voltage across R_2 is equal to V_{BE1} , thus

$$R_2 = \frac{0.517}{0.2 \text{ mA}} = 2.59 \text{ k}\Omega$$

The voltage across R_1 is given by $6.487 - 0.517 = 5.966 \text{ V}$. Thus,

$$R_1 = \frac{5.966 \text{ V}}{0.2 \text{ mA}} = 29.8 \text{ k}\Omega$$

Now, at 25°C, we have

$$V_Z = 6.8 \text{ V}$$

Assume $V_{BE1} = 0.7 \text{ V}$, then

$$V_{(R1+R2)} = 6.8 - 0.7 = 6.1 \text{ V}$$

$$I_{(R1+R2)} = \frac{6.1}{2.59 + 29.8} = 0.188 \text{ } \mu\text{A}$$

Thus

$$V_{BE1} = 0.7 + 0.025 \ln \frac{188}{100} = 0.716 \text{ V}$$

$$V_{(R_1+R_2)} = 6.8 - 0.716 = 6.084$$

$$\begin{aligned} V_{BE2} &= 6.084 \times \frac{R_2}{R_1 + R_2} \\ &= 6.084 \times \frac{2.59}{2.59 + 29.8} = 0.486 \text{ V} \end{aligned}$$

Thus,

$$I_{C2} = 100 e^{(486-700)/25} = 0.019 \text{ } \mu\text{A}$$

11.40 (a) Refer to the circuit in Fig. 11.23.

$$R_{\text{out}} = R_{on} \parallel R_{op}$$

where

$$R_{on} = \frac{1}{g_{mn}} \parallel r_{on} \simeq 1/g_{mn}$$

$$R_{op} = \frac{1}{g_{mp}} \parallel r_{op} \simeq 1/g_{mp}$$

$$R_{\text{out}} = R_{on} \parallel R_{op} \simeq \frac{1}{g_{mn}} \parallel \frac{1}{g_{mp}}$$

Thus,

$$R_{\text{out}} \simeq \frac{1}{g_{mn} + g_{mp}} \quad \text{Q.E.D.}$$

For matched devices, we have

$$g_{mn} = g_{mp} = g_m$$

$$R_{\text{out}} = \frac{1}{2g_m} \quad \text{Q.E.D.}$$

(b) $R_{\text{out}} = 20 \text{ } \Omega$

$$\frac{1}{2g_m} = 20$$

$$\Rightarrow g_m = \frac{1}{40} \text{ A/V} = 25 \text{ mA/V}$$

But,

$$g_m = k'(W/L)V_{OV}$$

$$25 = 200V_{OV}$$

$$\Rightarrow V_{OV} = \frac{25}{200} = 0.125 \text{ V}$$

$$V_{GG} = 2V_{GS}$$

$$= 2(|V_t| + |V_{OV}|)$$


$$= 2(0.5 + 0.125)$$

$$= 2 \times 0.625 = 1.25 \text{ V}$$

$$I_Q = \frac{1}{2}k'\left(\frac{W}{L}\right)V_{OV}^2$$

$$= \frac{1}{2} \times 200 \times 0.125^2 = 1.56 \text{ mA}$$

11.41

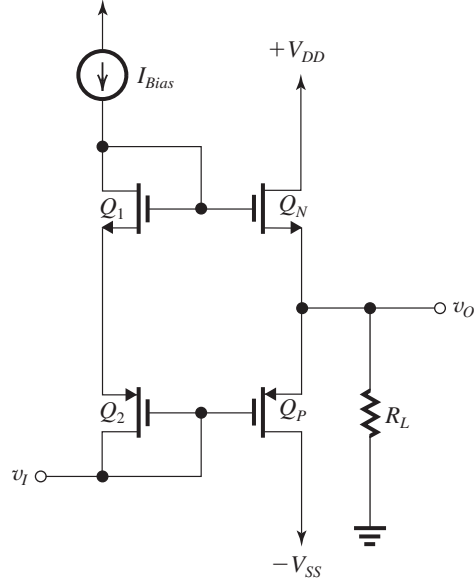

(a) Equation (11.43)

$$I_Q = I_{\text{Bias}} \frac{(W/L)_n}{(W/L)_1}$$

$$1 = 0.1 \frac{(W/L)_n}{(W/L)_1}$$

$$\frac{(W/L)_n}{(W/L)_1} = 10$$

$$Q_1: I_{\text{Bias}} = \frac{1}{2}k'_n\left(\frac{W}{L}\right)_1 V_{OV}^2$$

$$0.1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_1 \times (0.15)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = 35.6$$

$$Q_2: 0.1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_2 \times (0.15)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_2 = 88.9$$

$$Q_N: 1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_N \times (0.15)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_N = 356$$

$$Q_P: 1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_P \times (0.15)^2$$

$$\left(\frac{W}{L}\right)_P = 889$$

(b) From the circuit we get $v_I = v_O - V_{SGP}$

Since $v_O = 0$, we have

$$v_I = -V_{SGP}$$

$$V_{SGP} = |V_{OV}| + |V_t|$$

$$= 0.15 + 0.45$$

$$= 0.6 \text{ V}$$

$$\therefore v_I = -V_{SGP} = -0.6 \text{ V}$$

(c) Using Eq. (11.46), we obtain

$$v_{O\max} = V_{DD} - V_{OV}|_{\text{Bias}} - V_{GSN}$$

To find V_{GSN} , use the equations

$$i_{DN\max} = \frac{1}{2} k'_n \frac{W}{L} (V_{GSN} - V_t)^2$$


$$10 = \frac{1}{2} \times 0.250 \times 356 (V_{GSN} - V_t)^2$$

$$\Rightarrow V_{GSN} - V_t = 0.47 \text{ V}$$

$$V_{GSN} = V_t + 0.47 = 0.45 + 0.47 \simeq 0.92 \text{ V}$$

$$\therefore v_{O\max} = 2.5 - 0.2 - 0.92 = 1.38 \text{ V}$$

11.42

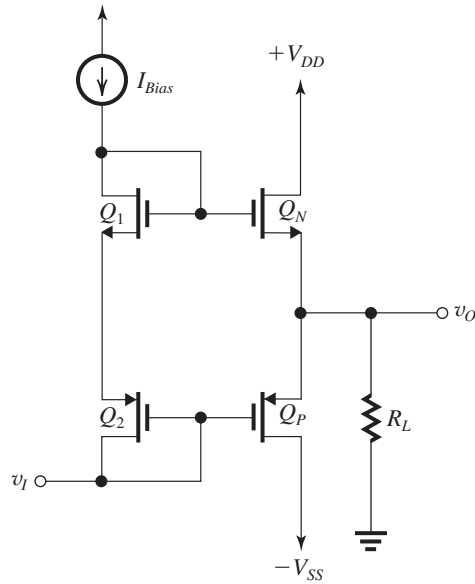

(a) under quiescent condition

$$\text{Voltage gain} = \frac{v_o}{v_i} = \frac{R_L}{R_L + R_{\text{out}}}$$

As shown in problem 11.40, for matched transistors we have

$$R_{\text{out}} = \frac{1}{2g_m}$$

Substituting for R_{out} above, we obtain for $\frac{v_o}{v_i}$

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + \frac{1}{2g_m}} \quad \text{Q.E.D.}$$

$$(b) \text{ Voltage gain} = 0.98 = \frac{R_L}{R_L + \frac{1}{2g_m}}$$

$$0.98 = \frac{1000}{1000 + \frac{1}{2g_m}}$$

$$\Rightarrow g_m = 24.5 \text{ mA/V}$$

For Q_1 , we have $I_{\text{Bias}} = I_D$.

$$\therefore 0.2 = \frac{1}{2} k_1 V_{OV}^2$$

$$0.2 = \frac{1}{2} \times 20 \times V_{OV}^2$$

$$\Rightarrow V_{OV} = 0.14 \text{ V}$$

For Q_N , we have

$$g_m = k_n V_{OV}$$

$$24.5 = k_n \times 0.14$$

$$k_n = 173 \text{ mA/V}^2$$

$$n = \frac{k_n}{k_1} = \frac{173}{20}$$

$$= 8.66$$

$$\text{and } I_Q = n I_{\text{bias}}$$

$$= 8.66 \times 0.2$$

$$= 1.73 \text{ mA}$$

11.43 Refer to Fig. 11.24. Consider the situation when Q_N is conducting the maximum current of 20 mA,

$$20 = \frac{1}{2} k_n v_{OVN}^2$$

$$= \frac{1}{2} \times 200 v_{OVN}^2$$

$$\Rightarrow v_{OVN} = 0.45 \text{ V}$$

Thus,

$$v_{O\min} = -V_{SS} + v_{OVN}$$

$$= -2.5 + 0.45 = -2.05 \text{ V}$$

Because Q_N and Q_P are matched, a similar situation pertains when Q_P is supplying maximum current, and

$$v_{O\max} = +2.05 \text{ V}$$

Thus, the output voltage swing realized is $\pm 2.05 \text{ V}$.

11.44 From Eq. (11.57), we obtain

$$R_{\text{out}} = 1/\mu(g_{mp} + g_{mn})$$

where

$$g_{mp} = g_{mn} = \frac{2I_Q}{|V_{OV}|} = \frac{2 \times 2}{0.2} = 20 \text{ mA/V}$$

$$R_{\text{out}} = \frac{1}{5(20 + 20)} = \frac{1}{200} \text{ k}\Omega = 5 \Omega$$

11.45 (a) From Eq. (11.68), we obtain

$$|\text{Gain error}| = \frac{1}{2\mu g_m R_L} \quad (1)$$

From Eq. (11.57), we get

$$R_{\text{out}} = \frac{1}{\mu(g_{mn} + g_{mp})}$$

For $g_{mn} = g_{mp} = g_m$, we have

$$R_{\text{out}} = \frac{1}{2\mu g_m} \quad (2)$$

Combining (1) and (2) yields

$$|\text{Gain error}| = \frac{R_{\text{out}}}{R_L} \quad \text{Q.E.D.}$$

(b) For $R_L = 100 \Omega$ and $|\text{Gain error}| = 3\%$,

$$R_{\text{out}} = 0.03 \times 100 = 3 \Omega$$

But,

$$R_{\text{out}} = \frac{1}{2\mu g_m}$$

$$3 = \frac{1}{2 \times 5 \times g_m}$$

$$\Rightarrow g_m = \frac{1}{30} = 33.3 \text{ mA/V}$$

Using

$$g_m = \frac{2I_Q}{V_{OV}}$$

we obtain

$$33.3 = \frac{2 \times 2.5}{V_{OV}}$$

$$\Rightarrow V_{OV} = \frac{5}{33.3} = 0.15 \text{ V}$$

11.46 i_{DP} and i_{DN} are given by Eqs. (11.61) and (11.62) as

$$i_{DP} = I_Q \left(1 - \mu \frac{v_O - v_I}{V_{OV}} \right)^2 \quad (1)$$

$$i_{DN} = I_Q \left(1 + \mu \frac{v_O - v_I}{V_{OV}} \right)^2 \quad (2)$$

Equation (1) shows that Q_P turns off and $i_{DP} = 0$ when

$$\mu \frac{v_O - v_I}{V_{OV}} = 1$$

Substituting this into Eq. (2) gives

$$i_{DN} = I_Q(1 + 1)^2 = 4I_Q$$

Since $i_L = -i_{DN}$, we have

$$v_O = i_L R_L = -4I_Q R_L \quad \text{Q.E.D.}$$

Similarly, Eq. (2) shows that Q_N turns off and $i_{DN} = 0$ when

$$\mu \frac{v_O - v_I}{V_{OV}} = -1$$

substituting this into Eq. (1) gives

$$i_{DP} = I_Q(1 + 1)^2 = 4I_Q$$

Since in this case $i_L = i_{DP}$, then

$$v_O = i_L R_L = 4I_Q R_L \quad \text{Q.E.D.}$$

Thus, one of the two transistors turns off when $|i_L|$ reaches $4I_Q$.

$$\mathbf{11.47} \text{ (a) } I_Q = \frac{1}{2} k' \frac{W}{L} V_{OV}^2$$

$$1.5 = \frac{1}{2} \times 0.1 \left(\frac{W}{L} \right)_P (0.15)^2$$

$$\Rightarrow \left(\frac{W}{L} \right)_P = 1333.3$$

$$\left(\frac{W}{L} \right)_N = \frac{(W/L)_P}{k'_n/k'_p}$$

$$\left(\frac{W}{L} \right)_N = \frac{1333.3}{2.5} = 533.3$$

$$\text{(b) } g_m = \frac{2I_Q}{V_{OV}} = \frac{2 \times 1.5}{0.15} = 20 \text{ mA/V}$$

$$R_{\text{out}} = \frac{1}{2\mu g_m} \text{ (where } g_{mn} = g_{mp} = g_m)$$

$$2.5 = \frac{1}{2\mu \times 20 \times 10^{-3}}$$

$$\Rightarrow \mu = 10 \text{ V/V}$$

$$\text{(c) Gain error} = -\frac{1}{2\mu g_m R_L}$$

$$= -\frac{1}{2 \times 10 \times 20 \times 10^{-3} \times 50} = -0.05$$

or -5%

(d) In the quiescent state the dc voltage at the output of each amplifier must be of the value that causes the current in Q_N and Q_P to be I_Q . Thus, for the Q_P amplifier the output voltage is

$$V_{DD} - V_{SG} = V_{DD} - |V_p| - |V_{OV}|$$

$$= 2.5 - 0.5 - 0.15 = 1.85 \text{ V}$$

$$\begin{aligned} -V_{SS} + V_{GS} &= -2.5 + 0.5 + 0.15 \\ &= -1.85 \text{ V} \end{aligned}$$
$$\mu \frac{v_O - v_I}{V_{OV}} = -1$$
$$i_{DP} = I_O(1 + 1)^2 = 4I_O$$
$$i_L = i_{DP}$$
$$i_L = 4I_Q$$
$$v_O = 4I_O R_L$$

$$= 4 \times 1.5 \times 10^{-3} \times 50 = 0.3 \text{ V}$$

(f) The situation at $v_O = v_{O\max}$ is illustrated in Fig. 1. Analysis of this circuit provides

$$i_{DP} = \frac{1}{2} \times k'_n \left(\frac{W}{L} \right)_n [2.5 - (v_{Omax} - 0.5) - 0.5]^2$$

$$\frac{v_{O\max}}{R_L} = \frac{1}{2} \times 0.25 \times 533.3(2.5 - v_{O\max})^2$$

$$\Rightarrow v_{O\max} = 1.77 \text{ V}$$

$$v_{O\min} = -1.77 \text{ V}$$
$$V_{B1} - V_{B4} = \left(1 + \frac{R_3}{R_4}\right)V_{BE6} + \left(1 + \frac{R_1}{R_2}\right)V_{BE5}$$
$$V_{GG} = (V_{B1} - V_{B4}) - (V_{BE1} + V_{BE2} + V_{EB3} + V_{EB4})$$
$$V_{GG} = \left(1 + \frac{R_3}{R_4}\right)V_{BE6} + \left(1 + \frac{R_1}{R_2}\right)V_{BE5}$$

$$-4V_{BE} \quad \text{Q.E.D.} \quad (1)$$

(b) From the circuit diagram we see that as the output transistors heat up, Q_6 also heats up. Thus in Eq. (1) only V_{BE6} changes with the temperature of the output stage, thus V_{GG} changes with temperature according to

$$\frac{\partial V_{GG}}{\partial T} = \left(1 + \frac{R_3}{R_4}\right) \frac{\partial V_{BE6}}{\partial T} \quad \text{Q.E.D.} \quad (2)$$

$$\frac{\partial V_{GG}}{\partial T} = \frac{\partial (V_{tN} + |V_{tP}|)}{\partial T}$$

$$= -3 - 3 = -6 \text{ mV}/^{\circ}\text{C} \quad (3)$$

$$\frac{\partial V_{GG}}{\partial T} = \left(1 + \frac{R_3}{R_4}\right) \frac{\partial V_{BE6}}{\partial T}$$

$$\begin{aligned} &= \left(1 + \frac{R_3}{R_4}\right) \times -2 \\ &= -2 \left(1 + \frac{R_3}{R_4}\right) \text{ mV}/^\circ\text{C} \end{aligned} \quad (4)$$

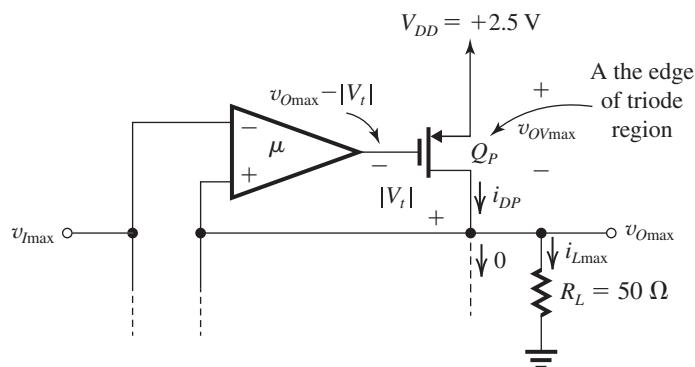


Figure 1

From Eqs. (3) and (4), we obtain

$$1 + \frac{R_3}{R_4} = 3$$

$$\Rightarrow \frac{R_3}{R_4} = 2$$

$$(d) I_{DN} = I_{DP} = 100 \text{ mA}$$

$$100 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_N V_{OVN}^2$$

$$100 = \frac{1}{2} \times 2 \times 10^3 \times V_{OVN}^2$$

$$\Rightarrow V_{OVN} = 0.316 \text{ V}$$

Similarly,

$$|V_{OVP}| = 0.316 \text{ V}$$

Thus,

$$V_{GSN} = |V_{GSP}| = 0.316 + 3 = 3.316 \text{ V}$$

and

$$V_{GG} = 2 \times 3.316 = 6.632 \text{ V}$$

To establish a quiescent current of 20 mA in the driver stage, we use

$$R = \frac{V_{GG}}{20} = \frac{6.632}{20} = 0.3316 \text{ k}\Omega$$

$$\simeq 332 \text{ }\Omega$$

$$V_{B1} - V_{B4} = V_{GG} + 4V_{BE}$$

$$= 6.632 + 4 \times 0.7 = 9.432 \text{ V}$$

Thus,

$$\left(1 + \frac{R_3}{R_4} \right) V_{BE6} + \left(1 + \frac{R_1}{R_2} \right) V_{BE5} = 9.432 \text{ V}$$

$$(1 + 2) \times 0.7 + \left(1 + \frac{R_1}{R_2} \right) \times 0.7 = 9.432$$

$$\Rightarrow \frac{R_1}{R_2} = 9.47$$

11.49 Refer to the circuit of Fig. 11.29.

Resistors R_2 and R_3 control the gain,

$$A_v = -\frac{2R_2}{R_3}$$

Resistor R_3 controls the gain alone. Resistor R_2 affects both the gain and the dc output level.

To see the later point, equate I_3 and I_4 from Eqs. (11.69) and (11.70) to obtain

$$\frac{V_S - 3V_{EB}}{R_1} = \frac{V_O - 2V_{EB}}{R_2}$$

$$\Rightarrow V_O = 2V_{EB} + \frac{R_2}{R_1} V_S - \frac{3R_2}{R_1} V_{EB}$$

$$= \frac{R_2}{R_1} V_S + \left(2 - \frac{3R_2}{R_1} \right) V_{EB}$$

$$\text{For } V_O \simeq \frac{2}{3} V_S, \text{ select } \frac{R_2}{R_1} = \frac{2}{3}$$

$$R_2 = \frac{2R_1}{3} = \frac{100}{3} = 33.3 \text{ k}\Omega$$

To keep the gain unchanged, we must change R_3 so that

$$\frac{2R_2}{R_3} = 50$$

$$R_3 = \frac{2 \times (100/3)}{50} = \frac{4}{3} = 1.33 \text{ k}\Omega$$

11.50 Refer to Fig. 11.29 with $V_S = 22 \text{ V}$.

$$V_{B1} \simeq 0$$

$$V_{E1} \simeq 0.7 \text{ V}$$

$$V_{E3} \simeq 1.4 \text{ V}$$

$$V_{C10} = 22 - 0.7 = 21.3 \text{ V}$$

$$I_{E3} = \frac{21.3 - 1.4}{50} \simeq 0.4 \text{ mA}$$

$$I_{E1} = I_{B3} = \frac{I_{E3}}{\beta_P + 1} = \frac{0.4}{21} = 19 \text{ }\mu\text{A}$$

$$I_{B1} = \frac{I_{E1}}{\beta_P + 1} = \frac{19}{21} = 0.9 \text{ }\mu\text{A}$$

$$V_{B1} = I_{B1} \times R_4 = 0.9 \times 10^{-3} \times 150 = 0.136 \text{ V}$$

We can use this value to obtain I_{E1} :

$$V_{E1} = 0.836 \text{ V}$$

$$V_{E3} = 1.536 \text{ V}$$

$$I_{E3} = \frac{21.3 - 1.536}{50} \simeq 0.4 \text{ mA}$$

(almost no change)

$$I_{E1} \simeq 19 \text{ }\mu\text{A}$$

$$I_{E4} = I_{E3} = 0.4 \text{ mA}$$

$$I_{E2} = I_{E1} = 19 \text{ }\mu\text{A}$$

$$I_{E5} \simeq I_{C3} = 0.4 \times \frac{20}{21} = 0.38 \text{ mA}$$

$$I_{E6} = I_{E5} = 0.38 \text{ mA}$$

$$I_{R1} = I_{R2} \simeq 0.4 \text{ mA}$$

$$V_O = V_{E4} + I_{R2} R_2$$

$$= V_{E3} + I_{R2} R_2$$

$$= 1.536 + 0.4 \times 25$$

$$= 11.54 \text{ V}$$

Consider next the effect of finite transistor β . For the case in Fig. 1, we have

$$V_S = 16 \text{ V}$$

The $V_S = 16$ V graph intersects the THD = 3% line at $P_L = 2.7$ W, which is the maximum possible load power. Thus,

$$\frac{(\hat{V}_o/\sqrt{2})^2}{R_I} = 2.7$$

$$\hat{V}_o = \sqrt{2.7 \times 8 \times 2} = 6.57 \text{ V}$$

which means that an approximately 13-V peak-to-peak sinusoid is needed.

$$i_{E1} = \frac{v_I}{R}$$

$$i_{C1} = \alpha_1 i_{E1} = \frac{\beta}{\beta + 1} \left(\frac{v_I}{R} \right)$$

$$i_{C4} = i_{C1} \frac{1}{1 + \frac{2}{\beta}}$$

Thus,

$$i_o = \frac{\beta}{\beta + 1} \frac{\beta}{\beta + 2} \frac{v_I}{R}$$

$$= \frac{100}{101} \times \frac{100}{102} \times \frac{v_I}{R}$$

$$\simeq 0.97 \frac{v_I}{R}$$

11.52 Figure 1 shows the currents in the circuit for the case where v_i is positive and assuming an op amp with very high gain (hence the 0 V between its two input terminals) and all β 's are very high. The result is that

$$i_O = \frac{v_I}{R}$$

If v_I is negative, the current through R reverses direction and is thus supplied by Q_2 and then mirrored to the output by the mirror $Q_5 - Q_6$, resulting in $i_O = v_I/R$ but reversed in direction.

11.53 Refer to Fig. 11.32.

$$\text{Gain} = 2K = 8$$

$K = 4$

$$\frac{R_4}{R_3} = K = 4$$

$$\Rightarrow R_4 = 40 \text{ k}\Omega$$

$$1 + \frac{R_2}{R_1} = 4$$

$$\frac{R_2}{R_1} = 3$$

$$\Rightarrow R_2 = 30 \text{ k}\Omega$$

This figure belongs to Problem 11.52.

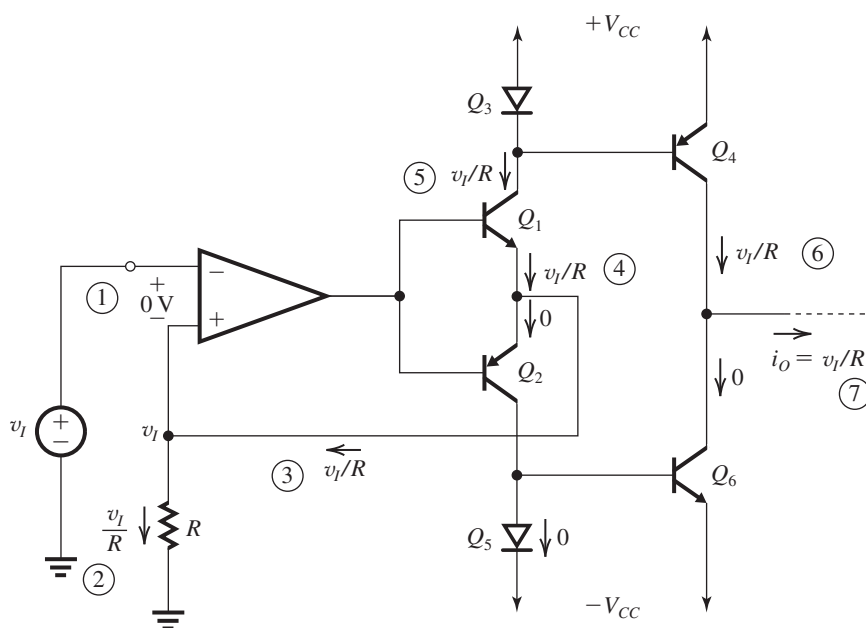


Figure 1

11.54 The analysis is shown in Fig. 1 (below), from which the gain is found as

$$\frac{v_O}{v_I} = 1 + \frac{R_2 + R_3}{R_1}$$

The largest sinusoid that can be provided across R_L will have a peak amplitude of $2 \times 13 = 26$ V. To ensure that the signals v_{O1} and v_{O2} are complementary, then

$$1 + \frac{R_2}{R_1} = \frac{R_3}{R_1}$$

Selecting $R_1 = 1$ k Ω , we obtain

$$1 + R_2 = R_3 \quad (1)$$

and to obtain a gain of 8 V/V we write

$$1 + \frac{R_2 + R_3}{R_1} = 8$$

$$1 + R_2 + R_3 = 8 \quad (2)$$

Solving (1) and (2) simultaneously gives

$$2(1 + R_2) = 8$$

$$\Rightarrow R_2 = 3 \text{ k}\Omega$$

$$R_3 = 4 \text{ k}\Omega$$

11.55 See figure on the next page.

11.56

$$\text{Average} = +10 \times 0.65 - 10 \times 0.35 = +3 \text{ V}$$

If duty cycle changed to 0.35, the average becomes

$$= +10 \times 0.35 - 10 \times 0.65 = -3 \text{ V}$$

11.57 (a) Maximum peak voltage across $R = V_{DD}$

Maximum power supplied to load

$$= \frac{(V_{DD}/\sqrt{2})^2}{R} = \frac{V_{DD}^2}{2R}$$

This figure belongs to Problem 11.54.

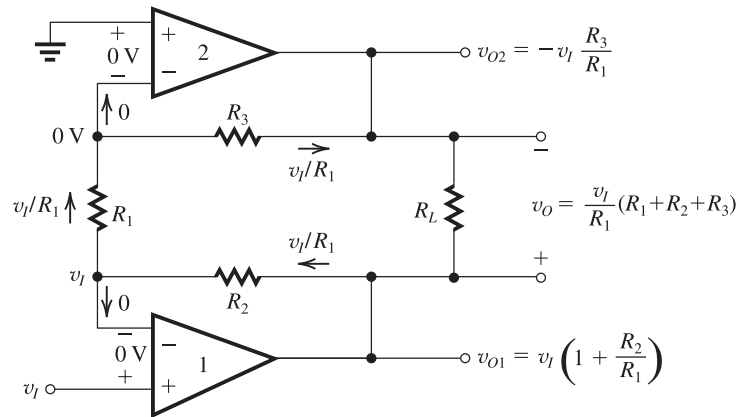


Figure 1

$$(b) \text{ Power loss} = 4f_s CV_{DD}^2$$

$$\eta = \frac{P_L}{P_L + P_{\text{loss}}} = \frac{V_{DD}^2/2R}{(V_{DD}^2/2R) + 4f_s CV_{DD}^2} = \frac{1}{1 + 8f_s CR}$$

For $f_s = 250$ kHz, $C = 1000$ pf and $R = 16$ Ω

$$\eta = \frac{1}{1 + 8 \times 250 \times 10^3 \times 1000 \times 10^{-12} \times 16} = 97\%$$

11.58

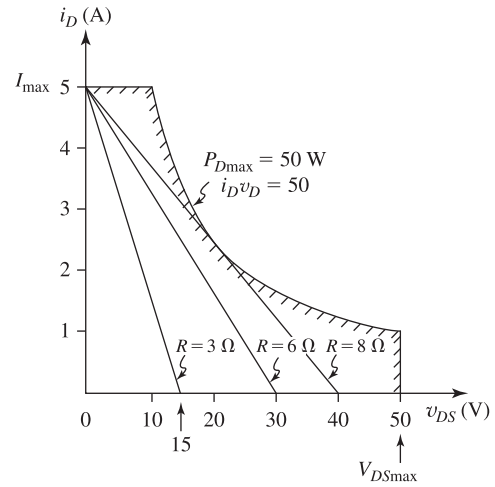



Figure 1

(a) Figure 1 shows the SOA boundaries.

(b) For the CS configuration in Fig. P11.58,

$$V_{DS} = V_{DD} - RI_D \quad (1)$$

This figure belongs to Problem 11.55.

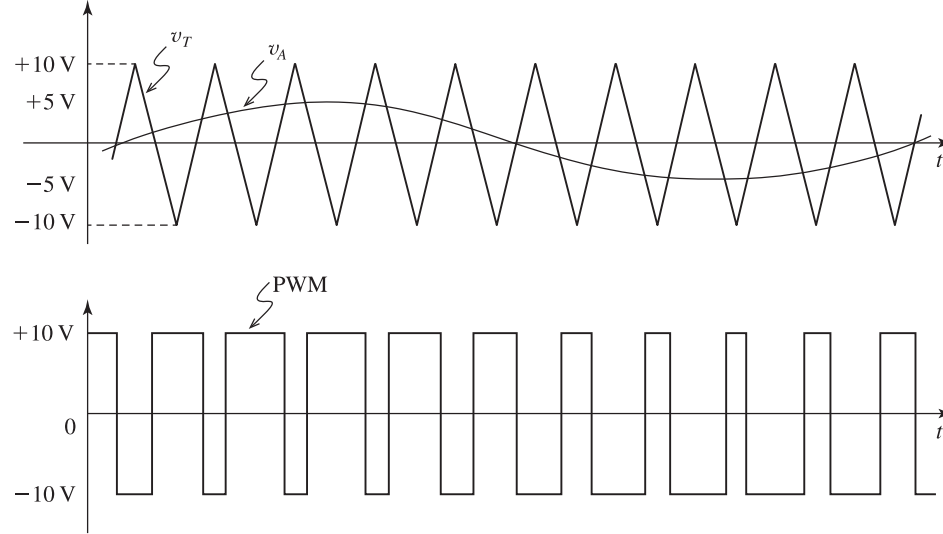

We see that maximum V_{DS} occurs when $I_D = 0$ and the resulting maximum V_{DS} is

$$V_{DS\max} = V_{DD}$$

Writing (1) in the alternative form

$$I_D = \frac{V_{DD} - V_{DS}}{R} \quad (2)$$

shows that maximum I_D is obtained when $V_{DS} = 0$ and the resulting maximum I_D is

$$I_{D\max} = \frac{V_{DD}}{R}$$

The power dissipation in the transistor is given by

$$\begin{aligned} P_D &= V_{DS} I_D \\ &= (V_{DD} - R I_D) I_D \end{aligned}$$

P_D will be maximum when

$$\frac{\partial P_D}{\partial I_D} = 0$$

that is,

$$V_{DD} - 2R I_D = 0$$

$$\Rightarrow R I_D = \frac{V_{DD}}{2}$$

or

$$V_{DS} = \frac{V_{DD}}{2}$$

The corresponding $P_{D\max}$ is

$$\begin{aligned} P_{D\max} &= V_{DS} I_D \\ &= \frac{V_{DD}}{2} \frac{V_{DD}}{2R} \\ &= \frac{V_{DD}^2}{4R} \end{aligned}$$

(c) For $V_{DD} = 40\text{ V}$, $v_{DS\max} = 40\text{ V}$. Now, since V_{DS} and I_D are related by the linear relationship in (1) or (2), the straight line representing this relationship on the $i_D - v_{DS}$ plane must pass by the point $v_{DS} = 40\text{ V}$ and $i_D = 0$. Now we are searching for the straight line with maximum slope that clears the hyperbola and intersects the vertical axis at 5 A or less. For this case, this straight line is the one joining the points (40, 0) and (0, 5). It is a tangent to the hyperbola at $v_{DS} = \frac{V_{DD}}{2} = 20\text{ V}$, which is the point of maximum power dissipation. For this straight line

$$R = \frac{40\text{ V}}{5\text{ A}} = 8\ \Omega$$

$$I_{D\max} = 5\text{ A}$$

$$P_{D\max} = \frac{V_{DD}^2}{4R} = \frac{40^2}{4 \times 8} = 50\text{ W}$$

(d) For $V_{DD} = 30\text{ V}$: Following a process similar to that in (c), we find

$$R = \frac{30\text{ V}}{5\text{ A}} = 6\ \Omega$$

$$I_{D\max} = 5\text{ A}$$

$$P_{D\max} = \frac{30^2}{4 \times 6} = 37.5\text{ W}$$

The locus of the operating point is shown in Fig. 1.

(e) For $V_{DD} = 15\text{ V}$, we have

$$R = \frac{15\text{ V}}{5\text{ A}} = 3\ \Omega$$

$$I_{D\max} = 5\text{ A}$$

$$P_{D\max} = \frac{15^2}{4 \times 3} = 18.75\text{ W}$$

The locus of the operating point is shown in Fig. 1.

$$\mathbf{11.59} \text{ Power rating} = \frac{130 - 30}{2.5} = 40 \text{ W}$$

$$I_{Cav} \leq \frac{40}{20} = 2.0 \text{ A}$$

$$\mathbf{11.60} \text{ (a) } \theta_{JA} = \frac{T_{J\max} - T_{A0}}{P_{D0}}$$

$$= \frac{100 - 25}{2} = 37.5^\circ\text{C/W}$$

(b) At $T_A = 50^\circ\text{C}$, we have

$$P_{D\max} = \frac{T_{J\max} - T_A}{\theta_{JA}}$$

$$= \frac{100 - 50}{37.5} = 1.33 \text{ W}$$

$$\text{(c) } T_J = 25^\circ + 37.5 \times 1 = 62.5^\circ\text{C}$$

$$\mathbf{11.61} \quad T_J \leq 50 + 3 \times 20 = 110^\circ\text{C}$$

$$V_{BE} = 800 - 2 \times (110 - 25) = 630 \text{ mV}$$

$$= 0.63 \text{ V}$$

$$\mathbf{11.62} \quad \theta_{JC} = \frac{T_J - T_C}{P_D} = \frac{180^\circ - 30^\circ}{50} = 3^\circ\text{C/W}$$

$$T_J - T_S = \theta_{JS} P_D$$

$$180^\circ - T_S = (\theta_{JC} + \theta_{CS}) P_D$$

$$\Rightarrow T_S = 180 - (3 + 0.6) \times 30 = 72^\circ$$

$$T_S - T_A = \theta_{SA} P_D$$

$$72 - 27 = \theta_{SA} \times 30$$

$$\Rightarrow \theta_{SA} = 1.5^\circ\text{C/W}$$

$$\text{Required heat-sink length} = \frac{6^\circ\text{C/W/cm}}{1.5^\circ\text{C/W}}$$

$$= 4 \text{ cm}$$

$$\mathbf{11.63} \quad T_C - T_A = \theta_{CA} P_D$$

$$= (\theta_{CS} + \theta_{SA}) P_D$$

$$\Rightarrow P_D = \frac{T_C - T_A}{\theta_{CS} + \theta_{SA}} = \frac{97 - 25}{0.5 + 0.1} = 120 \text{ W}$$

$$T_J - T_C = \theta_{JC} P_D$$

$$150 - 97 = \theta_{JC} \times 120$$

$$\Rightarrow \theta_{JC} = 0.44^\circ\text{C/W}$$