

# Wien-bridge oscillator


Student: Hong-Shuo Chen

Student ID: 0410001

Design the **Wien-bridge oscillator** (determine all Cs and Rs) to offer an oscillating frequency as close as possible to **10 kHz**, and use Hspice to verify the results. Use a non-perfect op designed by ourselves.
 
## Design

A Wien-bridge oscillator without amplitude stabilization



$$\omega_0 = 1/CR$$

$$R_2/R_1 = 2$$

In ideal

Select **R1 = 10k**

**R2 = 20k**

Select **R = 1k**

$$2\pi \cdot 1k = 1/(10k \cdot C)$$

$$C = 1/(2\pi \cdot 1k \cdot 10k)$$

**C = 15.9nF**

## Result and Discussion


$$R_1/R_2 = 2.08$$




```
***** Main Circuit *****
R1      Vinn    gnd          10k
R2      Vinn    vo           20.8k
***** Analysis *****
.op
.tran 10ns 10ms UIC
.probe tran v(vo)
```

When the loop gain is less than unity, the oscillations can not start.

$R1/R2 = 2.09$

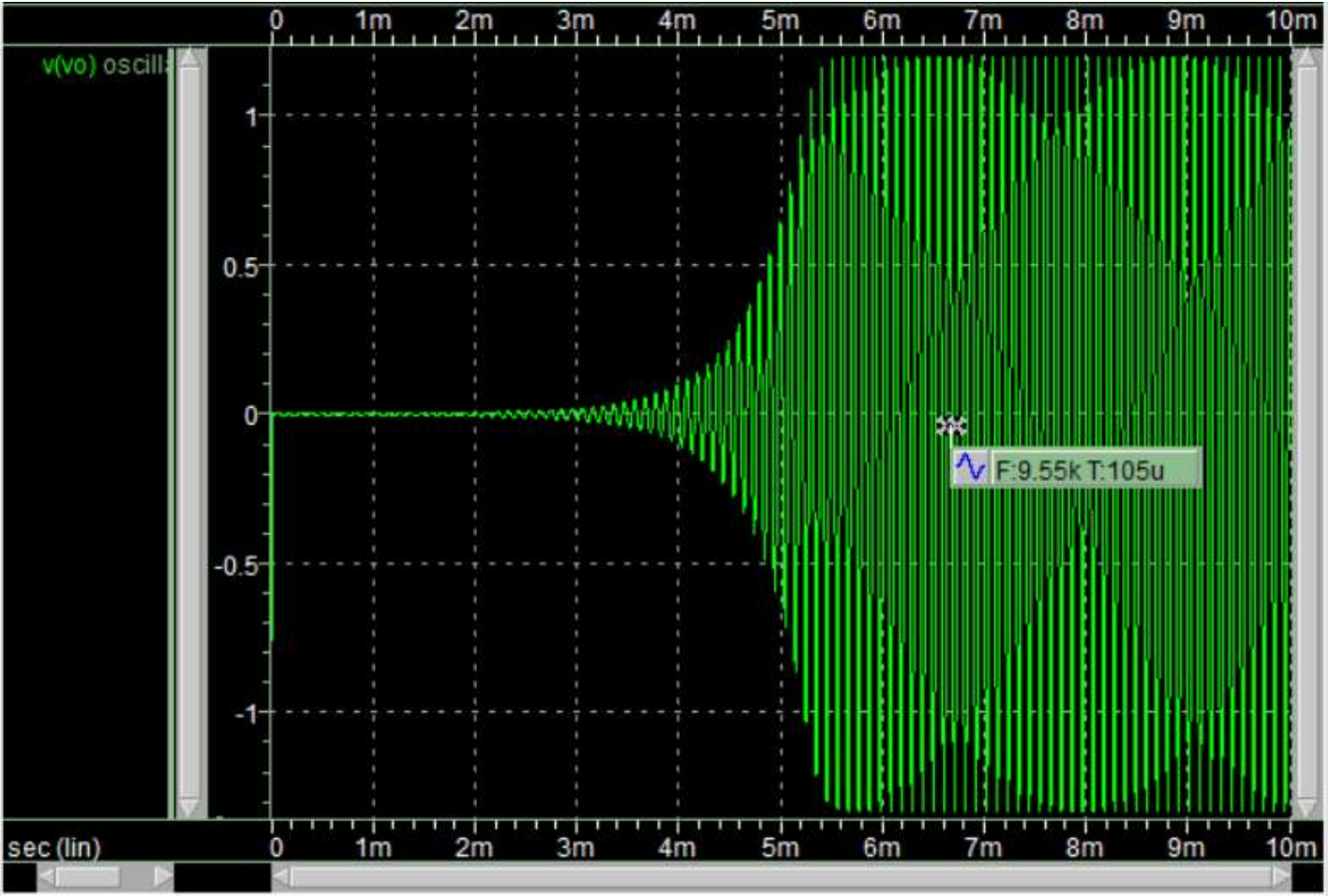

 



```

***** Main Circuit *****
R1      Vinn    gnd          10k
R2      Vinn    vo           20.9k
***** Analysis *****
.op
.tran 10ns 10ms UIC
.probe tran v(vo)

```

When the loop gain is greater than unity, the oscillations start.  
 Because the amplifier is not ideal, loop gain is slightly greater than unity, and it also causes the frequency slightly less than 10kHz.

$$R1/R2 = 2.3$$

  

```

***** Main Circuit *****
R1      Vinn    gnd          10k
R2      Vinn    vo           23k
***** Analysis *****
.op
.tran 10ns 10ms UIC
.probe tran v(vo)



```

As the loop gain increases, the circuits start oscillate earlier. However, the trade-off is that the frequency will decrease, and the wave form will be distorted. The amplitude of negative part sine wave will be greater than the amplitude of postive part the sine wave.


  
# Conclusion

Ater some adjustment  
I select  $R1/R2 = 2.1$ , which the distortion is not so large, and then adjust the C to let the frequency is equal to 10kHz.  
**C = 15.1nF**



```
***** Wien-bridge oscillator *****
***** Model/Lib *****
.lib 'cic018.1' TT
***** Options *****
.option post accurate method=gear
.option probe
.temp 27
.global Vdd Vss gnd
***** Source *****
Vdd          Vdd          gnd          DC=1.8
Vss          Vss          gnd          DC=-1.8
Iref         4            Vss          20uA

***** Main Circuit *****
*M      D      G      S      B
M1      3      Vinn    1      Vdd p_18 l=1u w=25u m=1
M2      2      Vinp    1      Vdd p_18 l=1u w=25u m=1
M3      3      3      Vss    Vss n_18 l=1u w=10u m=1
M4      2      3      Vss    Vss n_18 l=1u w=10u m=1
M5      1      4      Vdd    Vdd p_18 l=1u w=50u m=1
M6      vo     2      Vss    Vss n_18 l=1u w=50u m=1
M7      vo     4      Vdd    Vdd p_18 l=1u w=25u m=5
M8      4      4      Vdd    Vdd p_18 l=1u w=5u  m=1
Cc      2      vo     1.8p
*C1     vo     gnd     4p
R1      Vinn   gnd     10k
R2      Vinn   vo      21k
Cs      Vinp   5       15.1n
Rs      5      vo      1k
Cp      Vinp   gnd     15.1n
Rp      Vinp   gnd     1k

***** Analysis *****
.op
.tran 10ns 10ms UIC
.probe tran v(vo)

.end
```