

HW5

13.53

13.53 Bandpass with $f_0 = 2$ kHz, 3-dB bandwidth of 50 Hz, thus

$$Q = \frac{f_0}{BW} = \frac{2 \text{ kHz}}{50 \text{ Hz}} = 40$$

Refer to the circuit in Fig. 13.24(a). Using

$$C = 10 \text{ nF}$$

then

$$R = \frac{1}{\omega_0 C} = \frac{1}{2\pi \times 2 \times 10^3 \times 10 \times 10^{-9}} \\ = 7.96 \text{ k}\Omega$$

Select

$$R_1 = 10 \text{ k}\Omega$$

then

$$R_f = R_1 = 10 \text{ k}\Omega$$

Select

$$R_2 = 1 \text{ k}\Omega$$

then

$$R_3 = (2Q - 1)R_2 = (80 - 1) \times 1 = 79 \text{ k}\Omega$$

$$K = 2 - \frac{1}{Q} = 2 - \frac{1}{40} = 1.975$$

$$\text{Center-frequency gain} = KQ = 1.975 \times 40 = 79$$

13.56

13.56 Refer to Fig. 13.26 and Table 13.2. Using

$$C = 10 \text{ nF},$$

then

$$R = \frac{1}{\omega_0 C} = \frac{1}{10^5 \times 10 \times 10^{-9}} \\ = 1 \text{ k}\Omega$$

$$R_d = QR = 10 \times 1 = 10 \text{ k}\Omega$$

Select

$$r = 20 \text{ k}\Omega$$

$$R_1 = R_3 = \infty$$

If the dc gain is unity, then


$$1 = \text{HF gain} \times \frac{\omega_n^2}{\omega_0^2}$$

$$\Rightarrow \text{HF gain} = \left(\frac{10^5}{1.3 \times 10^5} \right)^2 \\ = 0.5917$$

$$C_1 = C \times \text{high-frequency gain}$$

$$= 10 \times 0.5917 = 5.92 \text{ nF}$$
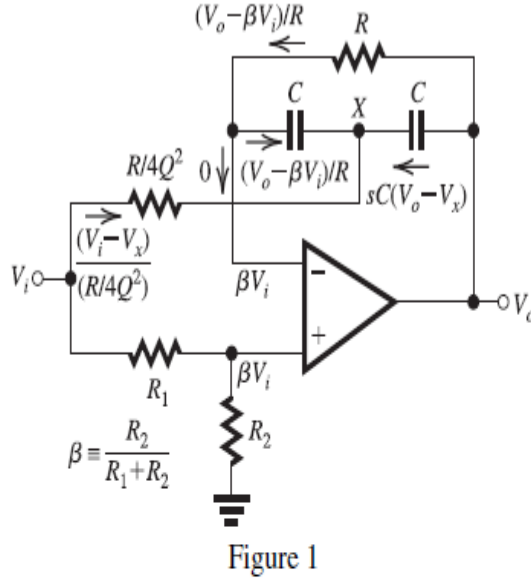
$$R_2 = R \frac{(\omega_0/\omega_n)^2}{\text{HF gain}} = 1 \text{ k}\Omega$$



The circuit is shown in Fig. 1. The voltage at node X is given by

$$V_x = \beta V_i - \frac{1}{sC} \frac{V_o - \beta V_i}{R}$$

$$= \beta V_i \left(1 + \frac{1}{sCR} \right) - \frac{V_o}{sCR}$$

Writing a node equation at X gives

$$\frac{V_o - \beta V_i}{R} + \frac{V_i - V_x}{R/4Q^2} + sC(V_o - V_x) = 0$$

Substituting for V_x from Eq. (1) and collecting terms gives

$$\frac{V_i}{V_x} = \frac{s^2 + s \frac{2}{CR} \left[1 + 2Q^2 \left(1 - \frac{1}{\beta} \right) \right] + \frac{4Q^2}{C^2 R^2}}{s^2 + s \frac{2}{CR} + \frac{4Q^2}{C^2 R^2}}$$

We observe that, as expected,

$$\omega_0 = \frac{2Q}{CR}$$

(a) To obtain an all-pass function, we set

$$\frac{2}{CR} \left[1 + 2Q^2 \left(1 - \frac{1}{\beta} \right) \right] = -\frac{2}{CR}$$

$$\Rightarrow \frac{1}{\beta} = 1 + \frac{1}{Q^2}$$

But,

$$\beta = \frac{R_2}{R_1 + R_2}$$

Thus,

$$(1) \quad \frac{R_2}{R_1} = Q^2$$

(b) To obtain a notch function, we set

$$\frac{2}{CR} \left[1 + 2Q^2 \left(1 - \frac{1}{\beta} \right) \right] = 0$$

$$\Rightarrow \frac{1}{\beta} = 1 + \frac{1}{2Q^2}$$

or, equivalently,

$$\frac{R_2}{R_1} = 2Q^2$$

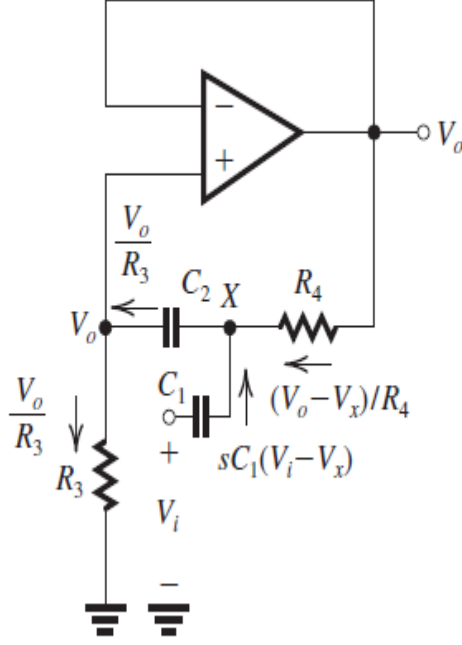


Figure 1

The analysis is shown in Fig. 1, below, left. The voltage at node X is given by

$$\begin{aligned} V_x &= V_o + \frac{V_o}{R_3} \frac{1}{sC_2} \\ &= V_o \left(1 + \frac{1}{sC_2 R_3} \right) \end{aligned} \quad (1)$$

A node equation at X provides

$$\begin{aligned} \frac{V_o - V_x}{R_4} + sC_1(V_i - V_x) &= \frac{V_o}{R_3} \\ V_o \left(\frac{1}{R_4} - \frac{1}{R_3} \right) + sC_1 V_i - V_x \left(\frac{1}{R_4} + sC_1 \right) &= 0 \end{aligned}$$

Substituting for V_x from Eq. (1) and collecting terms, we obtain

$$\frac{V_o}{V_i} = \frac{s^2}{s^2 + s \frac{1}{R_3} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) + \frac{1}{C_1 C_2 R_3 R_4}}$$

This is a high-pass function with a high-frequency gain of unity. To obtain a maximally flat response with $\omega_{3dB} = 10^4$ rad/s and using

$$C_1 = C_2 = C = 10 \text{ nF}$$

then

$$\omega_0 = \omega_{3dB} = 10^4 \text{ rad/s}$$

$$Q = \frac{1}{\sqrt{2}} = \omega_0 R_3 \left/ \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \right.$$

$$\frac{1}{\sqrt{2}} = 10^4 R_3 \left/ \left(\frac{2}{10 \times 10^{-9}} \right) \right.$$

$$\Rightarrow R_3 = \frac{1}{\sqrt{2}} \times \frac{2}{10^{-8}} \times 10^{-4} = 14.14 \text{ k}\Omega$$

$$\omega_0^2 = \frac{1}{C_1 C_2 R_3 R_4}$$

$$10^8 = \frac{1}{10^{-8} \times 10^{-8} \times 14.4 \times 10^3 \times R_4}$$

$$\Rightarrow R_4 = \frac{100}{14.14} \text{ k}\Omega = 7.07 \text{ k}\Omega$$

13.65

13.65

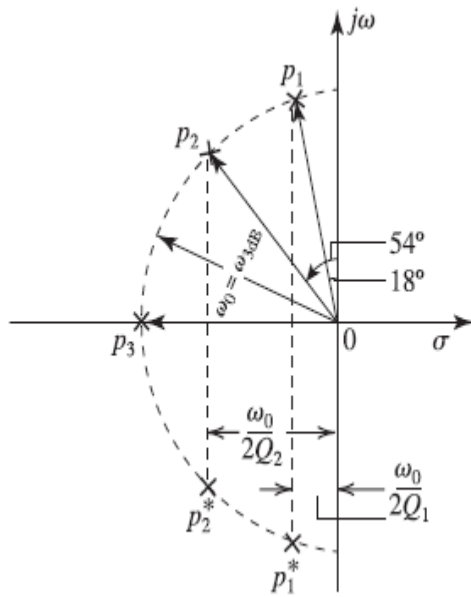


Figure 1

Figure 1 (see previous page) shows a graphical construct to determine the poles of the fifth order Butterworth filter. The pair of complex conjugate poles p_1 and p_1^* have a frequency

$$\omega_{01} = \omega_{3dB} = 2\pi \times 10^4 \text{ rad/s}$$

and a Q factor

$$Q_1 = \frac{1}{2 \sin 18^\circ} = 1.618$$

The pair of complex conjugate poles p_2 and p_2^* have

$$\omega_{02} = \omega_{3dB} = 2\pi \times 10^4 \text{ rad/s}$$

and a Q factor,

$$Q_2 = \frac{1}{2 \sin 54^\circ} = 0.618$$

The real-axis pole p_3 is at

$$s = -\omega_0 = -2\pi \times 10^4 \text{ rad/s}$$

The first second-order section can be realized using the circuit in Fig. 13.34(c). The design equations are (13.77)–(13.80).

$$R_1 = R_2 = R = 10 \text{ k}\Omega$$

$$C_4 = C$$

$$C_3 = C/4Q^2$$

Here, $Q = Q_1 = 1.618$, thus

$$C_3 = \frac{C}{4 \times 1.618^2} = 0.095C$$

$$CR = \frac{2Q}{\omega_0} = \frac{2 \times 1.618}{2\pi \times 10^4}$$

$$\Rightarrow C = \frac{2 \times 1.618}{2\pi \times 10^4 \times 10 \times 10^3} = 5.15 \text{ nF}$$

$$C_3 = 0.492 \text{ nF} = 492 \text{ pF}$$

$$C_4 = 5.15 \text{ nF}$$

The second second-order section also can be realized using the circuit in Fig. 13.34(c). Here,

$$R_1 = R_2 = R = 10 \text{ k}\Omega$$

$$C_4 = C$$

$$C_3 = \frac{C}{4Q^2}$$

where $Q = Q_2 = 0.618$. Thus

$$C_3 = \frac{C}{4 \times 0.618^2} = 0.655C$$

$$CR = \frac{2Q}{\omega_0} = \frac{2 \times 0.618}{2\pi \times 10^4}$$

$$\Rightarrow C = \frac{2 \times 0.618}{2\pi \times 10^4 \times 10^4} = 1.97 \text{ nF}$$

$$C_3 = 1.29 \text{ nF}$$

$$C_4 = 1.97 \text{ nF}$$


The first-order section can be realized using the circuit in Fig. 13.13(a) with

$$R_1 = R_2 = R = 10 \text{ k}\Omega$$

$$C = \frac{1}{\omega_0 R}$$

$$= \frac{1}{2\pi \times 10^4 \times 10^4} = 1.59 \text{ nF}$$

This figure belongs to Problem 13.65.

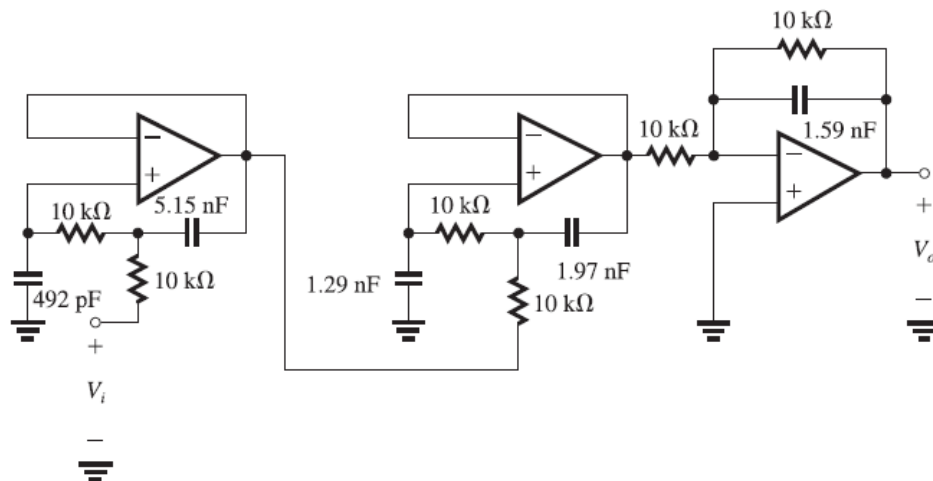

HW6

13.74

13.74 For the integrator in Fig. 13.36(b), we have

$$\frac{V_o}{V_1} = \frac{G_m}{sC}$$

$$\text{Unity-gain frequency} = \frac{G_m}{2\pi C}$$

Thus,

$$10 \times 10^6 = \frac{G_m}{2\pi \times 5 \times 10^{-12}}$$

$$\Rightarrow G_m = 0.314 \text{ mA/V}$$

13.76

13.76 Refer to the circuit in Fig. 13.36(c) and its transfer function in Eq. (13.91), namely

$$\frac{V_o}{V_i} = -\frac{G_{m1}}{sC + G_{m2}}$$

$$\text{Pole frequency} = \frac{G_{m2}}{2\pi C}$$

$$20 \times 10^6 = \frac{G_{m2}}{2\pi \times 2 \times 10^{-12}}$$

$$\Rightarrow G_{m2} = 0.251 \text{ mA/V}$$

$$|\text{DC gain}| = \frac{G_{m1}}{G_{m2}}$$

$$10 = \frac{G_{m1}}{G_{m2}}$$

$$\Rightarrow G_{m1} = 2.51 \text{ mA/V}$$

13.78

13.78 (a) Refer to the circuit in Fig. P13.78. The output current of the G_{m2} transconductor is $G_{m2}V_1$. Thus,

$$V_2 = \frac{G_{m2}}{sC} V_1$$

This is the input voltage to the negative transconductor G_{m1} . Thus the output current of G_{m1} , which is equal to I_1 , will be

$$\begin{aligned} I_1 &= G_{m1} V_2 \\ &= \frac{G_{m1} G_{m2}}{sC} V_1 \end{aligned}$$

$$Z_{in} \equiv \frac{V_1}{I_1} = s \frac{C}{G_{m1} G_{m2}}$$

which is that of an inductance L ,

$$L = \frac{C}{G_{m1} G_{m2}} \quad \text{Q.E.D.}$$

(b) To obtain an LCR resonator, we connected a capacitor C from node 1 to ground and a resistance R realized by the transconductor G_{m3} , as shown in Fig. 1 below.

(c) A fourth transconductor G_{m4} is used to feed a current $G_{m4}V_i$ to node 1, as shown in Fig. 1. The resulting circuit is identical to that in Fig. 13.37(b) except here $C_1 = C_2 = C$.

(d) With analogy to the identical circuit in Fig. 13.37(b), V_1/V_i will be a second-order bandpass filter with a transfer function given by Eq. (13.93), and V_2/V_i will be a second-order low-pass filter with a transfer function given by Eq. (13.94). Thus,

$$\frac{V_1}{V_i} = -\frac{s(G_{m4}/C)}{s^2 + s\frac{G_{m3}}{C_1} + \frac{G_{m1}G_{m2}}{C^2}}$$

and,

$$\frac{V_2}{V_i} = -\frac{G_{m2}G_{m4}/C^2}{s^2 + s\frac{G_{m2}}{C} + \frac{G_{m1}G_{m2}}{C^2}}$$

This figure belongs to Problem 13.78, part (b).

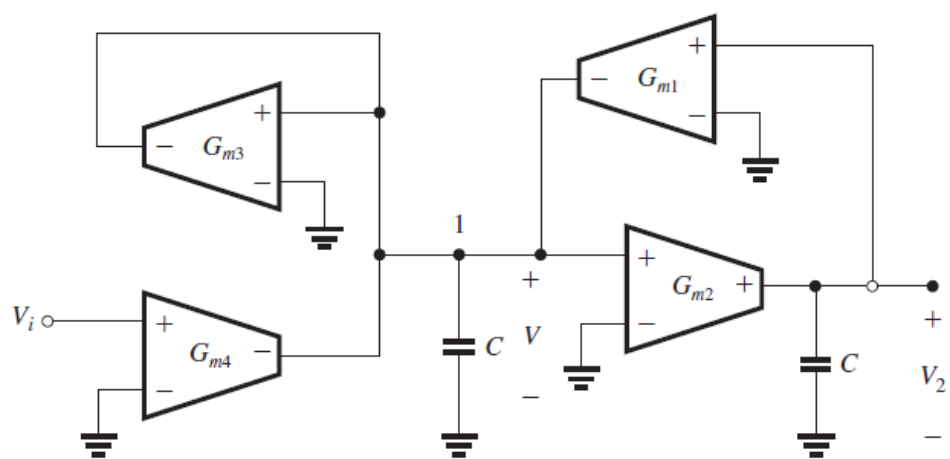


Figure 1

13.80

$$13.80 \quad f_0 = 25 \text{ MHz}, \quad Q = 5,$$

Center-frequency gain = 5

The design equations are given by (13.99), (13.100), and (13.101). Thus

$$G_m = \omega_0 C$$

where

$$C = C_1 = C_2 = 5 \text{ pF}$$

$$\begin{aligned} G_m &= 2\pi \times 25 \times 10^6 \times 5 \times 10^{-12} \\ &= 0.785 \text{ mA/V} \end{aligned}$$

Thus,

$$G_{m2} = G_m = 0.785 \text{ mA/V}$$

$$G_{m3} = \frac{G_m}{Q} = \frac{0.785}{5} = 0.157 \text{ mA/V}$$

$$\begin{aligned} G_{m4} &= \frac{G_m}{Q} |\text{Gain}| \\ &= \frac{0.785}{5} \times 5 = 0.785 \text{ mA/V} \end{aligned}$$

13.82

$$13.82 \quad R_{\text{eq}} = \frac{T_c}{C_1} = \frac{1}{f_c C_1} = \frac{1}{200 \times 10^3 C_1}$$

For $C_1 = 1 \text{ pF}$,

$$R_{\text{eq}} = \frac{1}{200 \times 10^3 \times 1 \times 10^{-12}} = 5 \text{ M}\Omega$$

For $C_1 = 5 \text{ pF}$,

$$R_{\text{eq}} = \frac{1}{200 \times 10^3 \times 5 \times 10^{-12}} = 1 \text{ M}\Omega$$

For $C_1 = 10 \text{ pF}$,

$$R_{\text{eq}} = \frac{1}{200 \times 10^3 \times 10 \times 10^{-12}} = 500 \text{ k}\Omega$$

13.84

$$\mathbf{13.84} \quad \omega_0 = \omega_{3dB} = 10^3 \text{ rad/s}$$

$$Q = 1/\sqrt{2} \text{ and DC gain} = 1$$

$$f_c = 100 \text{ kHz, } C_1 = C_2 = C = 5 \text{ pF}$$

From Eqs. (13.109) and (13.110),

$$C_3 = C_4 = \omega_0 T_c C$$

$$= 10^3 \times \frac{1}{100 \times 10^3} \times 5 \times 10^{-12}$$

$$= 0.05 \text{ pF}$$

From Eq. (13.112),

$$C_5 = \frac{C_4}{Q} = \frac{0.05}{1/\sqrt{2}} = 0.071 \text{ pF}$$

The dc gain of the low-pass circuit is

$$\text{DC gain} = \frac{C_6}{C_4}$$

For DC gain = 1,

$$C_6 = C_4 = 0.05 \text{ pF}$$