




HW8-Low Pass Filter

Professor: Paul C.-P. Chao

Low Pass Filter

- $V_{dd}=1.8V$

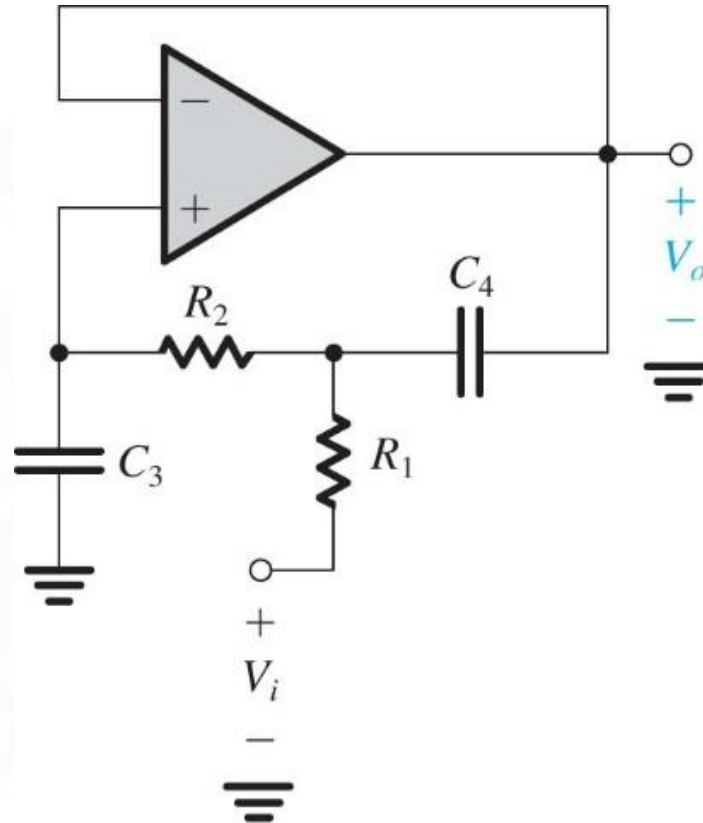

Generation of Equivalent Feedback Loops (Cont'd)

- If we apply the complementary transformation to the feedback loop in Fig. 13.34(a), we obtain the equivalent loop in Fig. 13.34(b). The new loop in Fig. 13.34(b) can be used to realize a **low-pass function** by injecting the input signal as shown in Fig. 13.34(c).


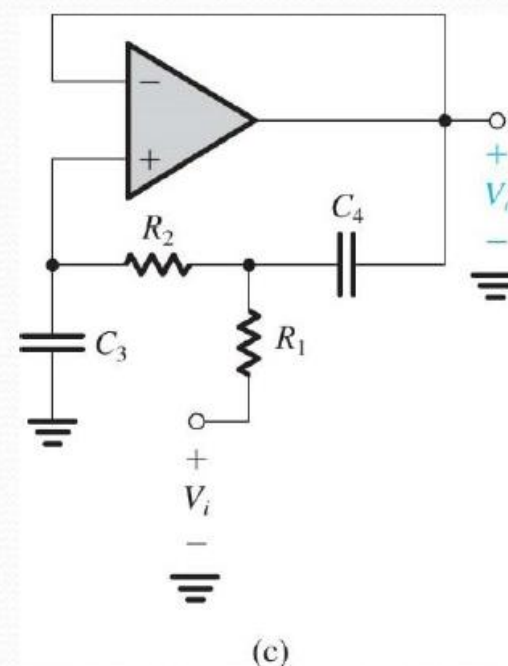
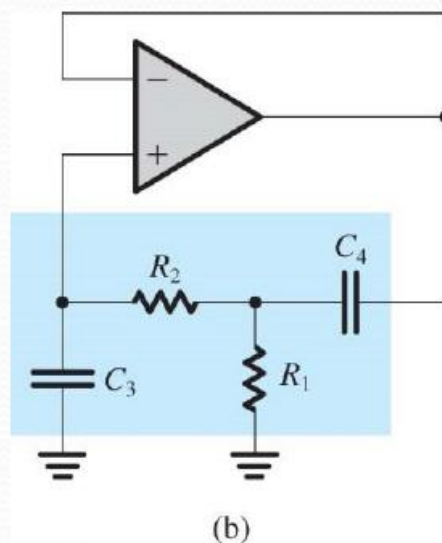
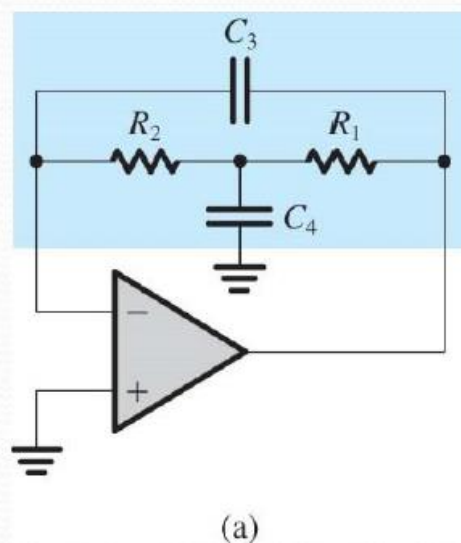



Figure 13.34 (a) Feedback loop obtained by placing the bridged-T network of Fig. 13.28(b) in the negative-feedback path of an op amp. (b) Equivalent feedback loop generated by applying the complementary transformation to the loop in (a). (c) A low-pass filter obtained by injecting V_i through R_1 into the loop in (b).

Synthesis of the Feedback Loop (Cont'd)

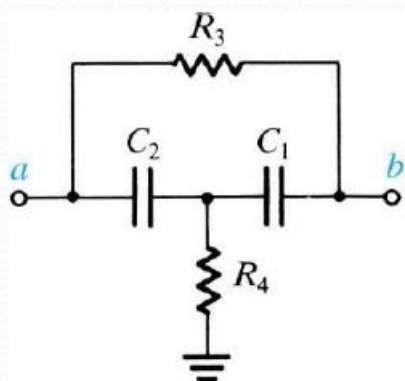- Aims to have **complex-conjugate** transmission zeros.
- The simplest such networks are the **bridged-T networks** shown in Fig. 13.28 together with their transfer functions $t(s)$ from b to a , with a open-circuited.



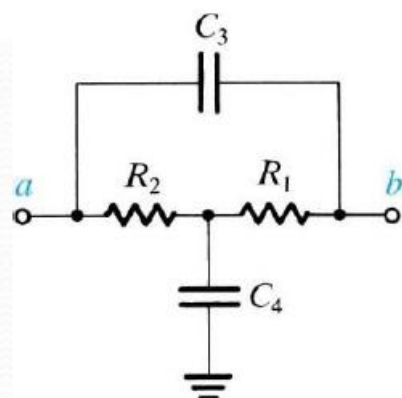
$$t(s) = \frac{s^2 + s\left(\frac{1}{C_1} + \frac{1}{C_2}\right)\frac{1}{R_3} + \frac{1}{C_1 C_2 R_3 R_4}}{s^2 + s\left(\frac{1}{C_1 R_3} + \frac{1}{C_2 R_3} + \frac{1}{C_1 R_4}\right) + \frac{1}{C_1 C_2 R_3 R_4}}$$



$$t(s) = \frac{s^2 + s\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\frac{1}{C_4} + \frac{1}{C_3 C_4 R_1 R_2}}{s^2 + s\left(\frac{1}{C_4 R_1} + \frac{1}{C_4 R_2} + \frac{1}{C_3 R_2}\right) + \frac{1}{C_3 C_4 R_1 R_2}}$$

(b)

Low Pass Filter

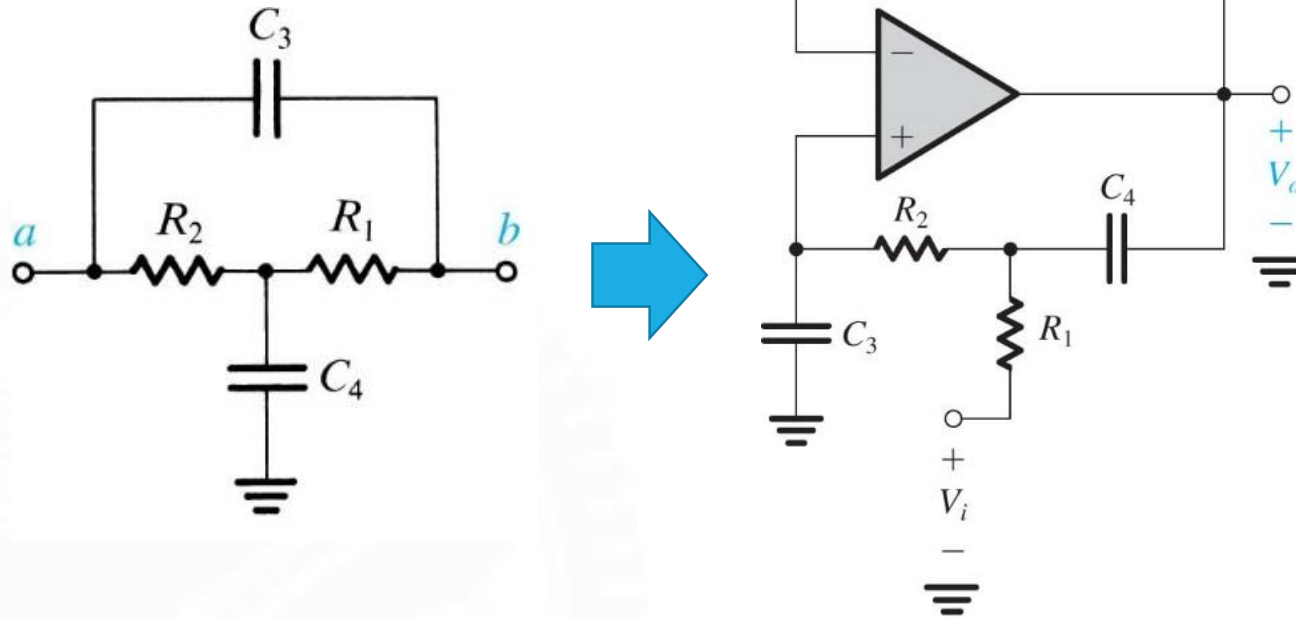

- Transfer function :

$$t(s) = \frac{s^2 + s\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\frac{1}{C_4} + \frac{1}{C_3 C_4 R_1 R_2}}{s^2 + s\left(\frac{1}{C_4 R_1} + \frac{1}{C_4 R_2} + \frac{1}{C_3 R_2}\right) + \frac{1}{C_3 C_4 R_1 R_2}}$$

Generation of Equivalent Feedback Loops(Cont'd)

- Application of the complementary transformation
- The design of the circuit in Fig. 13.33(b) is based on Eqs. (13.73) through (13.76): namely, $R_3 = R$, $R_4 = R/4Q^2$, $C_1 = C_2 = C$, $CR = 2Q/\omega_0$ and the value of C is arbitrarily chosen to be practically convenient --- a high-pass function.

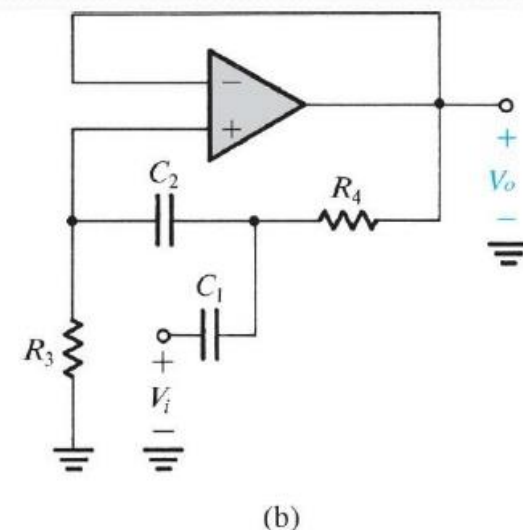
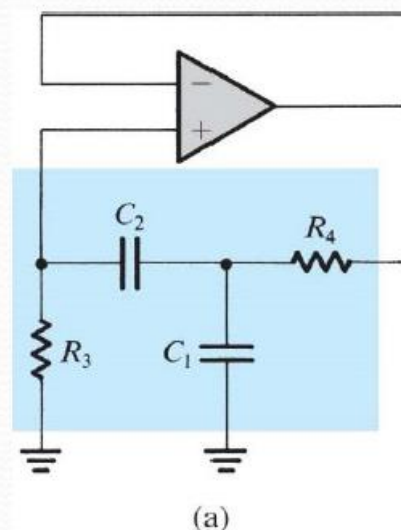
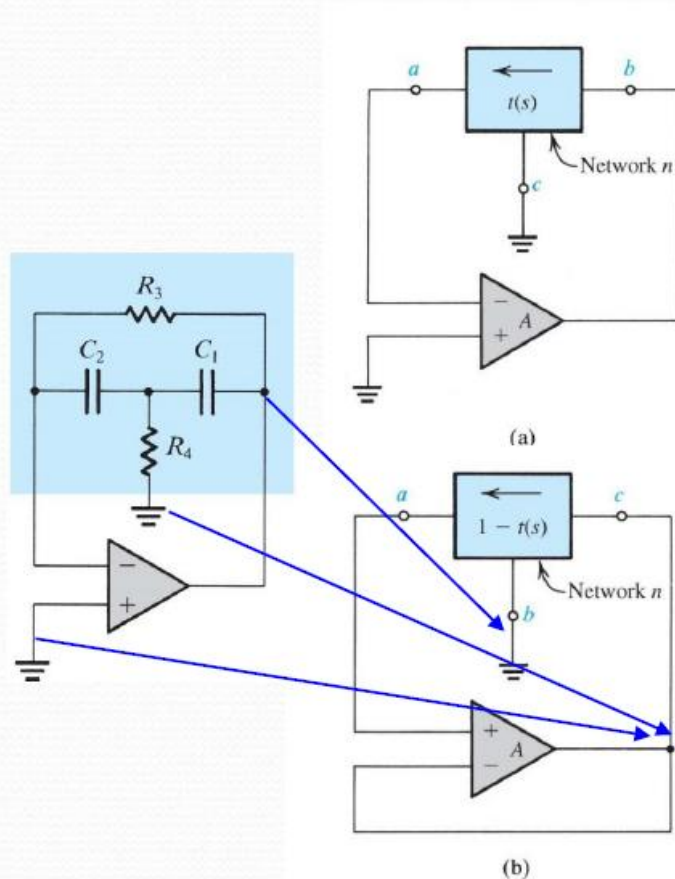


Figure 13.33 (a) Feedback loop obtained by applying the complementary transformation to the loop in Fig. 13.29. (b) Injecting the input signal through C_1 realizes the high-pass function. This is one of the **Sallenand-Key** family of circuits.

Generation of Equivalent Feedback Loops (Cont'd)

As another example, Fig. 13.34(a) shows the feedback loop generated by placing the two-port RC network of Fig. 13.28(b) in the negative-feedback path of an op amp. Using the expression for $t(s)$ given in Fig. 13.28(b), we can write for the active-filter poles

$$\omega_0 = 1/\sqrt{C_3 C_4 R_1 R_2} \quad (13.77)$$

$$Q = \left[\frac{\sqrt{C_3 C_4 R_1 R_2}}{C_4} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \right]^{-1} \quad (13.78)$$



(the only different result from the previous in page 75)

Normally the design of this circuit is based on selecting $R_1 = R_2 = R$, $C_4 = C$, and $C_3 = C/m$. When substituted in Eqs. (13.77) and (13.78), these yield

$$m = 4Q^2 \quad (13.79)$$


$$CR = 2Q/\omega_0 \quad (13.80)$$

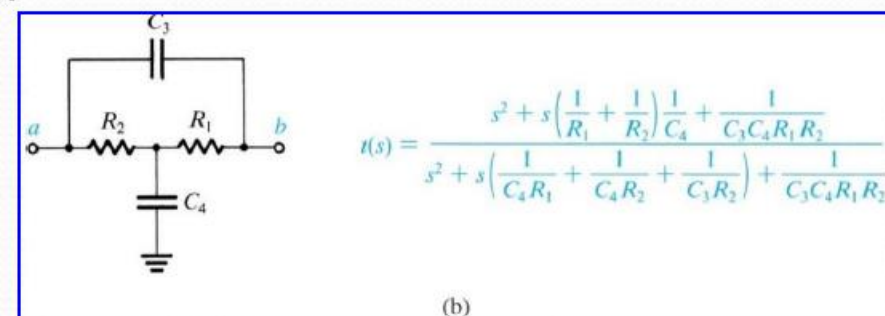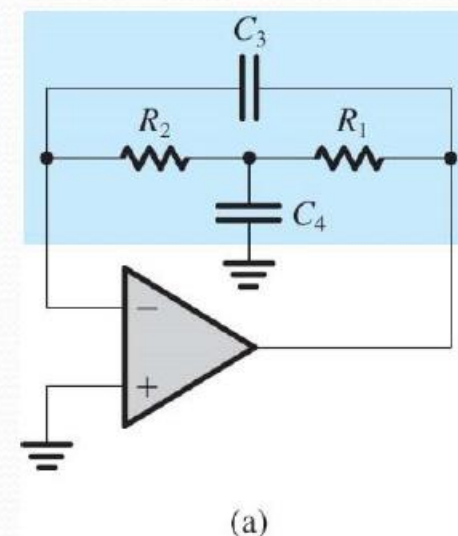with the remaining degree of freedom (the value of C or R) left to the designer to choose.





Two stage opamp

- $V_{dd}=1.8V$, $V_{in+}=V_{in-}=0.9V$

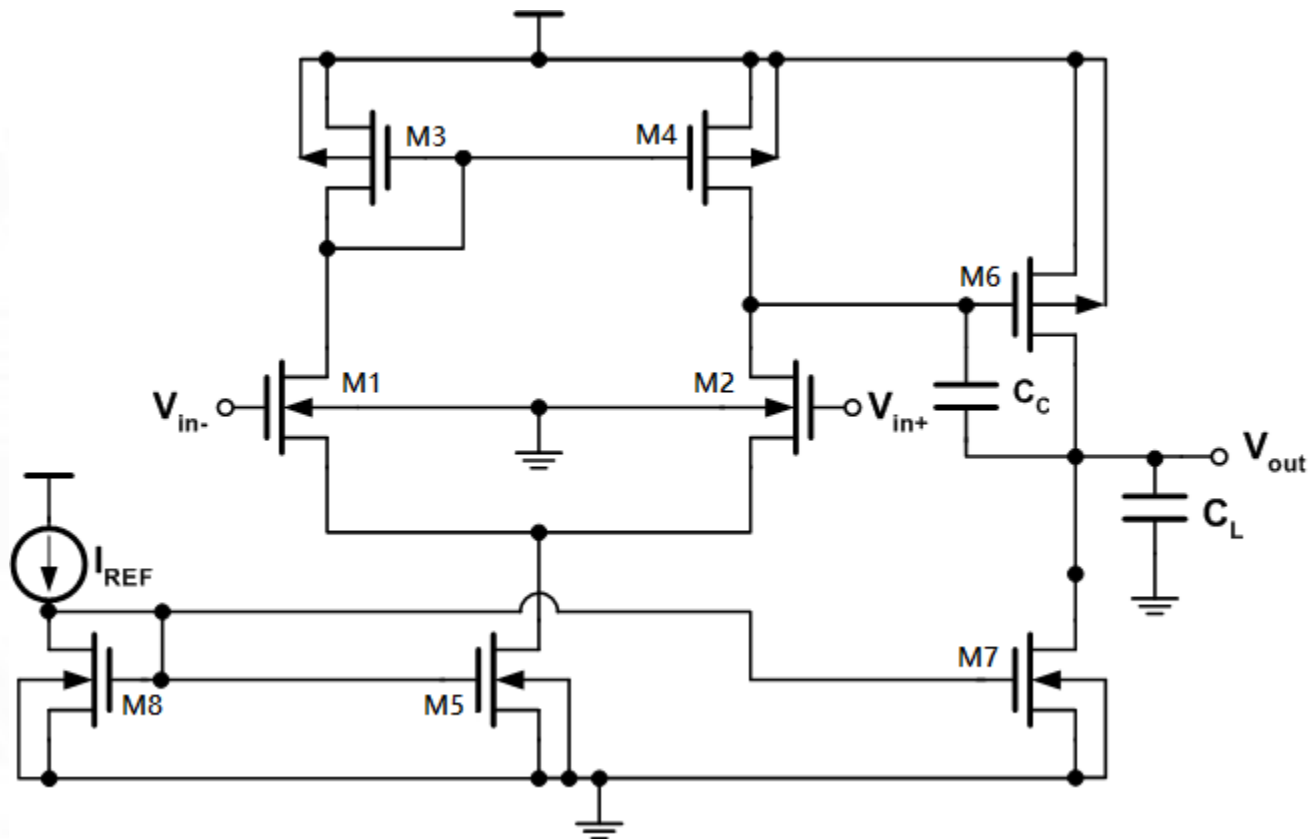

Simulation Result

- Frequency response

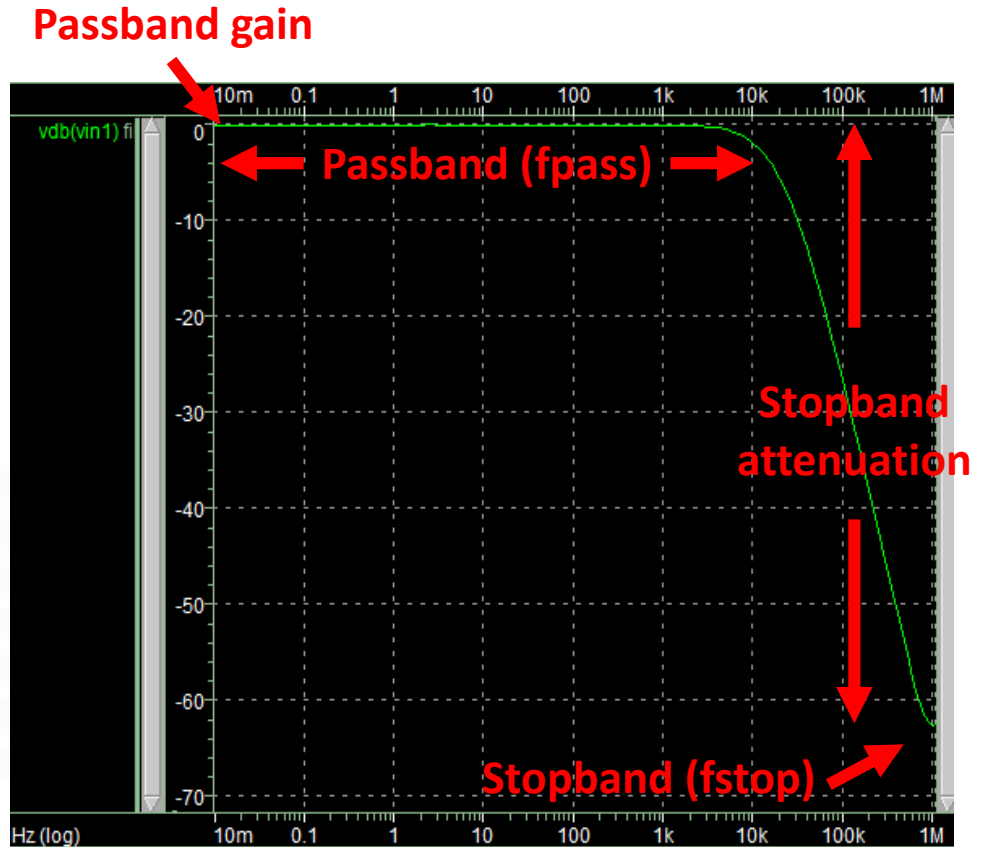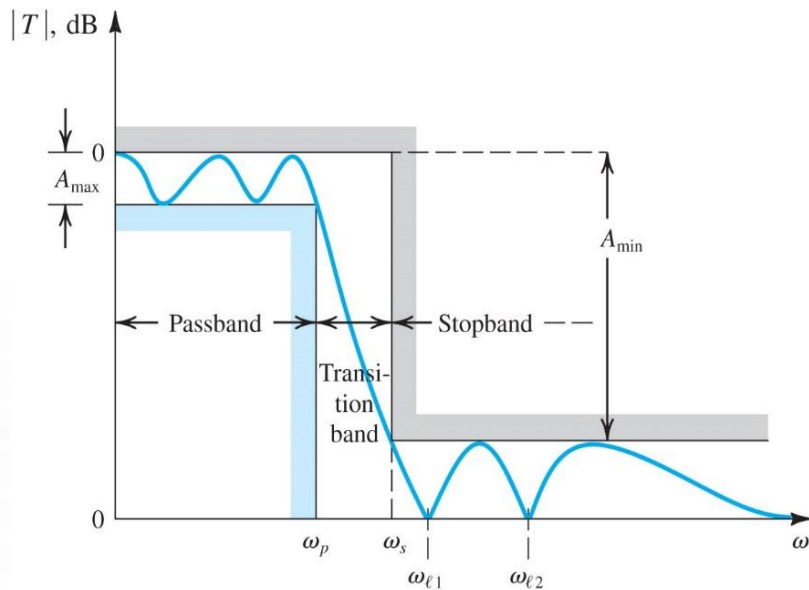


Simulation Result

- Transient analysis


Input → 1kHz



Input → 10kHz

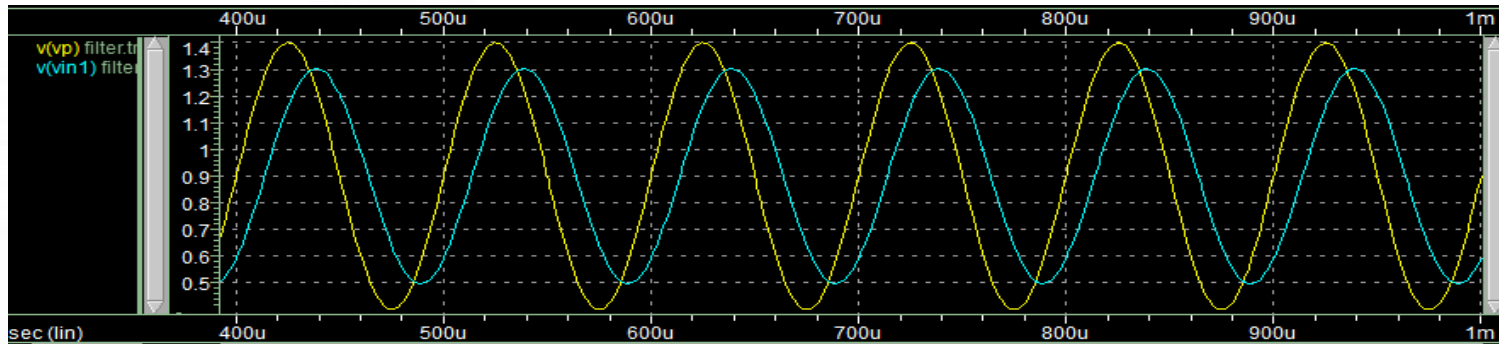

Input → 100kHz

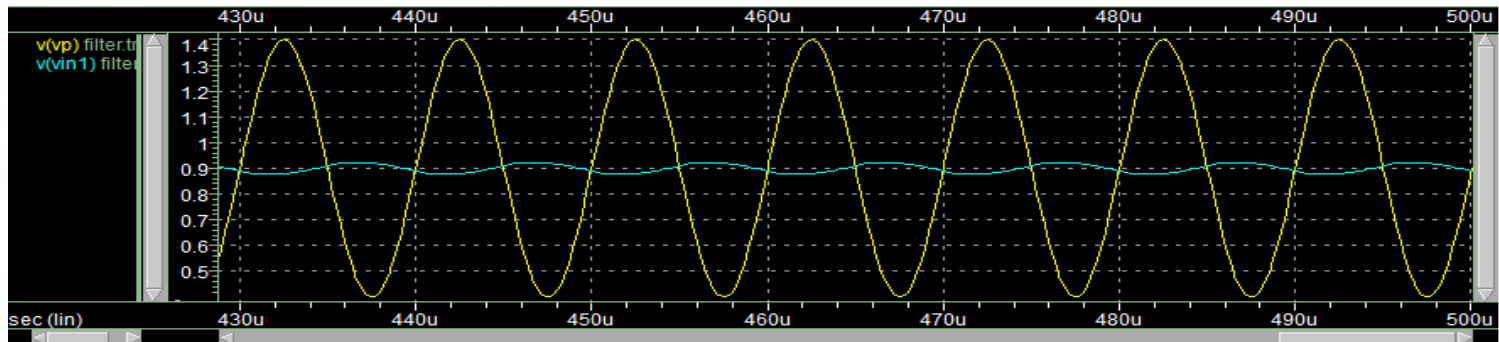



Design Specification

Parameter	Value
Power supply VDD	1.8V
Passband (fpass)	0-10kHz
Passband gain	0dB
Stopband (fstop)	100kHz
Stopband attenuation	40dB

- 作業上傳到E3, 繳交以下檔案, 檔名: hw8_學號
 - 報告 (.pdf) (ex:hw8_0560030.pdf)
 - 每個規格需符合, 並附上模擬結果圖
 - AC analysis (output frequency response)
 - Transient analysis (with 1kHz, 10kHz, 100kHz of 1Vpp sine wave input)
 - 解釋設計方法
 - Spice file (.sp) (ex:hw8_0560030.sp)
- Deadline: 12/25
- 12/25以後繳交作業, 遲交一個禮拜分數-10%, 兩個禮拜-20%, 以此類推分數



END
